

MAY 2008

AUS\$ 12.90 - NZ\$ 15.50 - SAR 84.95 - US\$ 9.95

£ 3.90

**FREE E-BOOK**  
**15 Elektor Blockbusters**  
**www.elektor.com/ebook**

# elektor

electronics worldwide

## M16C Display Computer GRAPHIC TALENT

**DigiButler** – assembly, test & software

**paX** – voltage amp & input buffer

**USB Programmer** – AVR Prog for ATM18

## THE PC TAKES CONTROL Measurement Software

.. 2-WIRE LCD .. REFLOW CONTROL .. EASYPIC5 .. POWER AMP PROTECTION .. FLOW



# NEW Jaycar Catalogue OUT NOW order on-line at [www.jaycarelectronics.co.uk/catalogue](http://www.jaycarelectronics.co.uk/catalogue)

## AV Project Kits

### Theremin Synthesiser Kit

KC-5295 £14.75 + postage & packing

The Theremin is a strange musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Theremin. By moving your hand between the antenna and the metal plate, you can create unusual sound effects. Kit includes a machined, silkscreened, and pre-drilled case, circuit board, all electronic components with clear English instructions.

- Required 9VDC wall adapter (Maplin #GS74R £6.99)



### "The Champ" Audio Amplifier

KC-5152 £1.95 + postage & packing

This tiny module uses the LM386 audio IC, and will deliver 0.5W into 8 ohms from a 9 volt supply making it ideal for all those basic audio projects. It features variable gain, will happily run from 4-12VDC and is smaller than a 9 volt battery, allowing it to fit into the tightest of spaces.

- PCB and all electronic components included



Be one of the first to get our brand new colour catalogue. It's bursting with over 800 new products, all with PDS pricing and in full colour.



### IR Remote Extender MKII Kit

KC-5432 £7.25 + postage & packing

Operate your DVD player or digital decoder using its remote control from another room. It picks up the signal from the remote control and sends it via a 2-wire cable to an infrared LED located close to the device. This improved model features fast data transfer, capable of transmitting pay TV digital remote control signals using the Pace 400 series decoder. Kit supplied with case, screen printed front panel, PCB with overlay and all electronic components.

- Requires 9VDC power (Maplin #GS74R £6.99) and 2-wire cable



## Starter Projects & Tools

### Short Circuits Book and Parts

KJ-8502 £11.95 + postage & packing

This full colour 96-page book has over 100 drawings and diagrams. The projects are fun to build and relevant to the electronics scene in the new millennium. Included with the book, you get the baseboard, plenty of spring terminals and ALL the components required to build every project in the book, INCLUDING the bonus projects. Book measures 205 x 275mm



### Battery Zapper Kit MK II

KC-5427 £29.00 + postage & packing

This kit attacks a common cause of failure in wet lead acid cell batteries: sulphation. The circuit produces short bursts of high-level energy to reverse the damaging sulphation effect. This improved unit features a battery health checker with LED indicator, new circuit protection against badly sulphated batteries, test points for a DMM and connection for a battery charger. Kit includes case with screen-printed lid, PCB with overlay and all electronic components with clear English instructions.

- Suitable for 6, 12 and 24V batteries



NEW  
IMPROVED  
VERSION!

### LED Water Level Indicator MKII Kit

KC-5449 £10.25 + postage & packing

This simple circuit illuminates a string of LEDs to quickly indicate the water level in a rainwater tank. The more LEDs that illuminate, the higher the water level. The input signal is provided by ten sensors located in the water tank and connected to the indicator unit via light duty figure-8 cable. Kit supplied with PCB with overlay, machined case with screen printed lid and all electronic components. Requires 12-18V AC or DC, 500mA plugpack.



## Precision Tools Ideal for PCB work!

Both pliers and side cutters are made from quality tool steel and have soft padded handles that are spring loaded for comfortable long-term use. Both are excellent for PCB work.

### 6" Long Nose Pliers

TH-1887 £3.00 + postage & packing

Precision, slim line long nose pliers that are ideal for working in confined areas. They have serrated jaws so you can get a firm grip on the item you're holding.



### 5" Angled Side Cutters

TH-1897 £3.00 + postage & packing

Ideal for fine PCB work, these cutters will easily cut leads flush with the board's surface.



### Low Cost DMM

QM-1500 £2.25 + postage & packing

This full featured Digital Multimeter is perfect for the home handyman or young experimenter and will give years of reliable service. It features a huge 10A DC current range as well as diode and transistor testing functions. Also measures AC & DC volts and resistance. At this price you should buy two!



### How To Order

- ORDER ON-LINE
- ALL PRICING IN POUND STERLING
- MINIMUM ORDER ONLY £10

### Post and Packing Charges

Order Value	Cost	Order Value	Cost
£10 - £49.99	£5	£200 - £499.99	£30
£50 - £99.99	£10	£500+	£40
£100 - £199.99	£20		

Max weight 12lb (5kg). Heavier parcels POA. Minimum order £10.

Note: Products are despatched from Australia, so local customs duty and taxes may apply.

How to order:

Phone: Call Australian Eastern Standard Time Mon-Fri on 0800 032 7241. Fax: +61 2 8832 3118

Email: [techstore@jaycarelectronics.co.uk](mailto:techstore@jaycarelectronics.co.uk)

Post: PO Box 107, Rydalmere NSW 2116 Australia  
Expect 10-14 days for air parcel delivery

Check out the Jaycar range in your FREE Catalogue - logon to

[www.jaycarelectronics.co.uk/elektor](http://www.jaycarelectronics.co.uk/elektor)

or check out the range at

[www.jaycarelectronics.co.uk](http://www.jaycarelectronics.co.uk)

**0800 032 7241**

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only)


For those who want to write:

PO Box 107, Rydalmere NSW 2116 Sydney AUSTRALIA

**Jaycar**  
Electronics

# BitScope PC Oscilloscopes & Analyzers
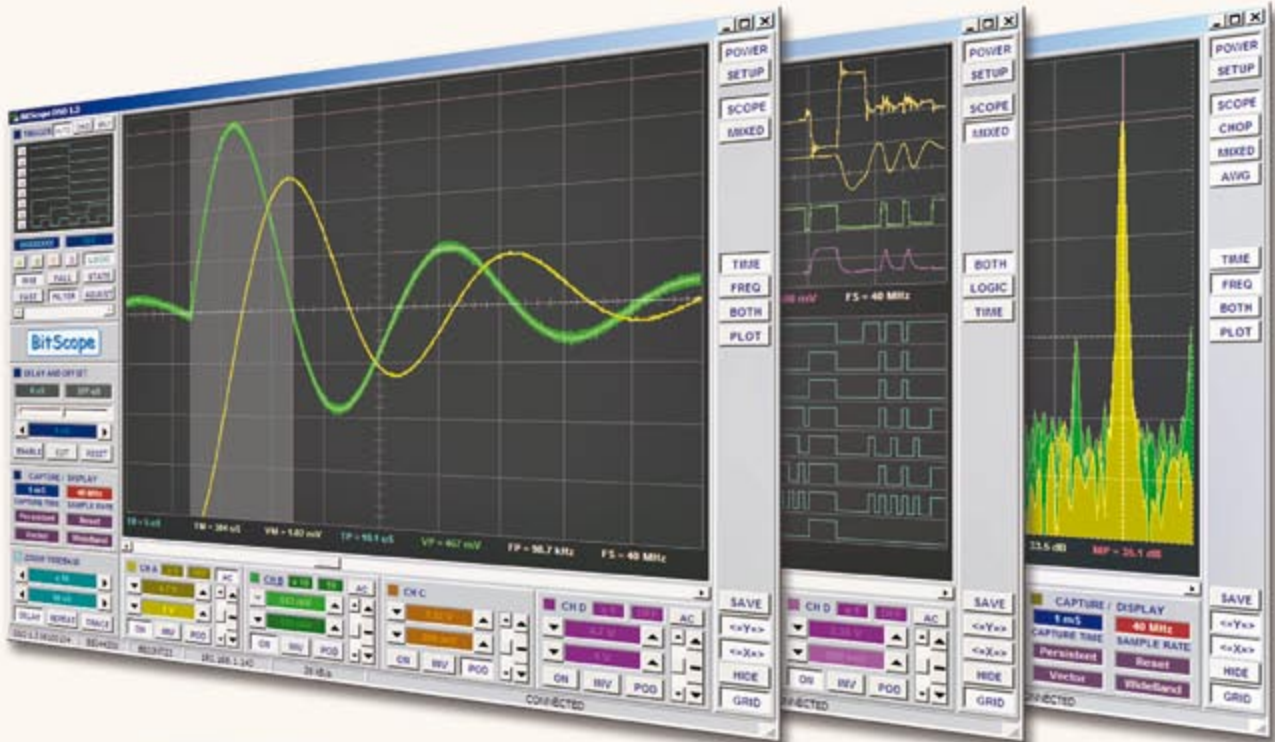
## DSO Test Instrument Software for BitScope Mixed Signal Oscilloscopes



4 Channel BitScope



2 Channel BitScope



Pocket Analyzer

### Digital Storage Oscilloscope

- ✓ Up to 4 analog channels using industry standard probes or POD connected analog inputs.

### Mixed Signal Oscilloscope

- ✓ Capture and display up to 4 analog and 8 logic channels with sophisticated cross-triggers.

### Spectrum Analyzer

- ✓ Integrated real-time spectrum analyzer for each analog channel with concurrent waveform display.

### Logic Analyzer

- ✓ 8 logic, External Trigger and special purpose inputs to capture digital signals down to 25nS.

### Data Recorder

- ✓ Record anything DSO can capture. Supports live data replay and display export.

### Networking

- ✓ Flexible network connectivity supporting multi-scope operation, remote monitoring and data acquisition.

### Data Export

- ✓ Export data with DSO using portable CSV files or use libraries to build custom BitScope solutions.

## BitScope DSO Software for Windows and Linux

BitScope DSO is fast and intuitive multi-channel test and measurement software for your PC or notebook. Whether it's a digital scope, spectrum analyzer, mixed signal scope, logic analyzer, waveform generator or data recorder, BitScope DSO supports them all.

Capture deep buffer one-shots or display waveforms live just like an analog scope. Comprehensive test instrument integration means you can view the same data in different ways simultaneously at the click of a button.

DSO may even be used stand-alone to share data with colleagues, students or customers. Waveforms may be exported as portable image files or live captures replayed on other PCs as if a BitScope was locally connected.

BitScope DSO supports all current BitScope models, auto-configures when it connects and can manage multiple BitScopes concurrently. No manual setup is normally required. Data export is available for use with third party software tools and BitScope's networked data acquisition capabilities are fully supported.



[www.bitscope.com](http://www.bitscope.com)

## More than just a mag

Most of you will associate 'Elektor' with the printed magazine that's been on circulation in newsstands, bookshops and in electronics retail stores since December 1974. In fact you are reading issue # 377 right now — on paper, and we intend to print quite a few more editions for you to enjoy. However over the past few years Elektor has developed a number of activities that do not involve paper anymore, although we consider them part and parcel of our publishing activities in general. Some of these activities may be unknown to you so I'll mention a few. To start with, there are our PCBs, CDs, books, special issues, kits and modules. Elektor PCBs have been on sale since issue #1 but kits and modules are relatively recent additions. We started selling them to help those individual readers 'dying' to build our more ambitious projects but were either unable to source the components or shamefully ignored by component suppliers moving towards the professional domain with the inherent, awful P&P quotes. Our first 'module' was the legendary GBDSO. Some of our recent kits, like DigiButler (page 26) and last month's Elektor Internet Radio are 'hybrids' in that they contain a PCB that has the SMD components pre-mounted. From reader feedback we learned that many of you still enjoy soldering through-hole parts, hence these are supplied separately with the kit for an hour or so of wielding the old soldering iron (low-power, mind you).


Elektor is also expanding its 'e-events' portfolio by staging workshops and seminars. Our partners are field leading companies and individuals. Examples include valve workshops and MultiSim10 from (and by) National Instruments EWB. Both were highly successful and got high grades from attendants. Another 'e-events' activity you may have seen announced is the Elektor-hosted study trip to China.

We have created an Elektor channel on YouTube, provisionally at [www.youtube.com/elektorim](http://www.youtube.com/elektorim). We have discovered that short films, however primitively made, on our techno stuff are a great way of pulling in not only newcomers of the MTV generation but also those now in retirement and having discovered Elektor again through successful Googling.

Jan Buiting  
Editor


# Display Computer

# 18

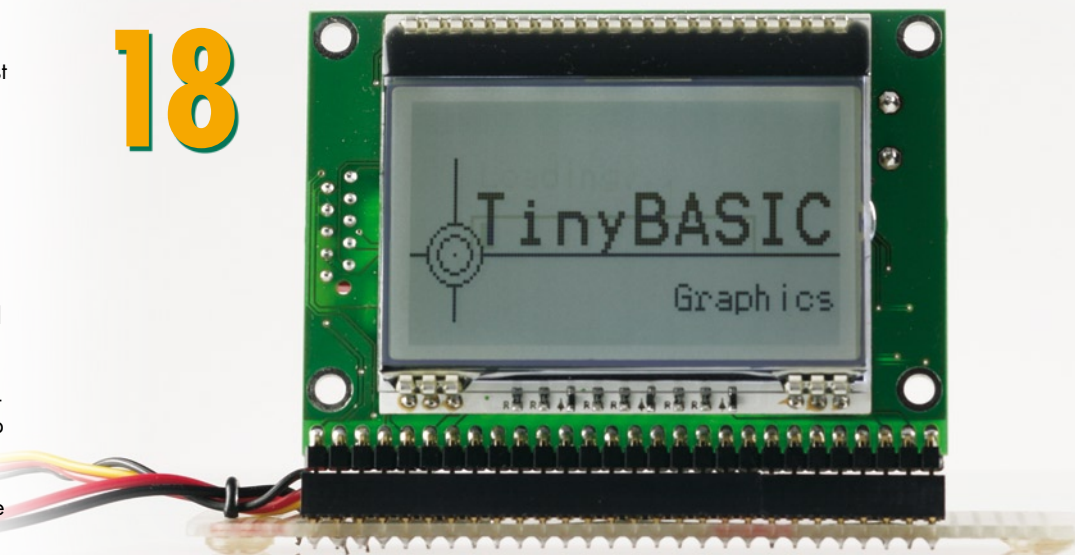


Programming a graphic display is distinctly more difficult than programming a text display. Our mini microcontroller board features a new display-on-glass module and a high-performance Renesas M16C microcontroller. The board is available fully assembled, and the microcontroller is pre-loaded with a TinyBasic interpreter to simplify the development of graphics applications – even for novices.

## 38 Elektor AVRProg

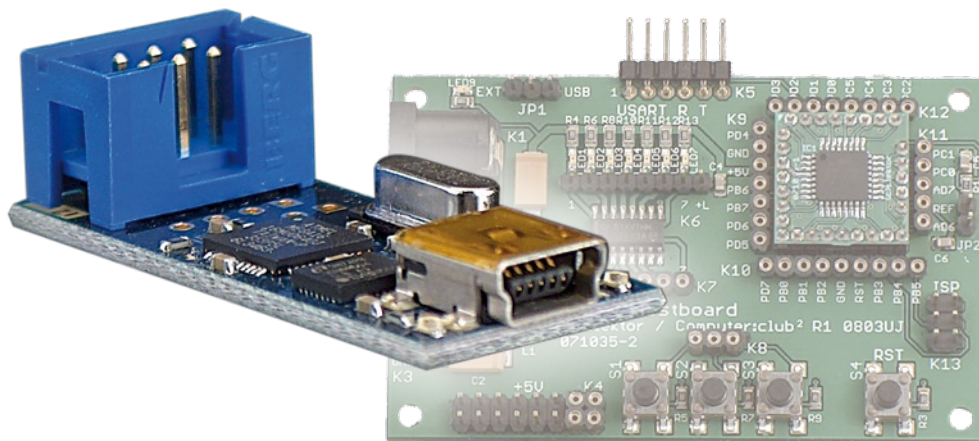

Two events triggered the conception of this AVR programmer: the feedback received on USBprog from Elektor, October 2007 and a series of articles started last month around our ATM18 project. The outcome is a plug-and-play AVRISP mk2-compatible USB programmer for AVR controllers!

## 58 Tiny Counter

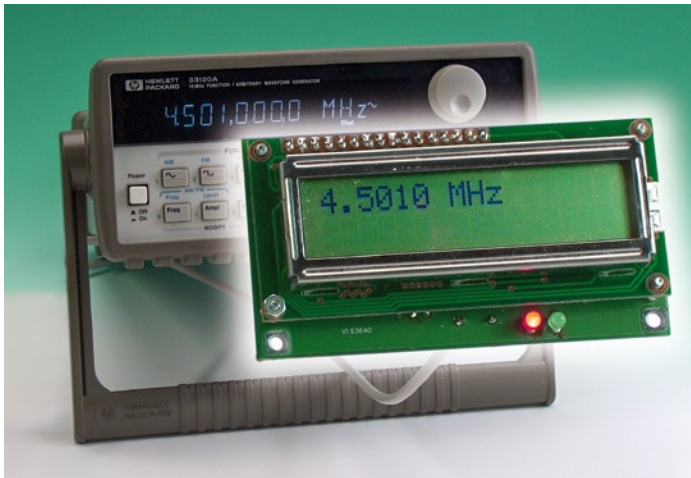


The tiny frequency counter module described here consists essentially of just an ATtiny2313 microcontroller and an LCD panel. The microcontroller is clocked at 20 MHz, and so the counter module can be used at frequencies of up to 5 MHz without the need for a prescaler.

## Free E-book


**15 top articles from Elektor  
bundled in a single pdf file**

details on page 12

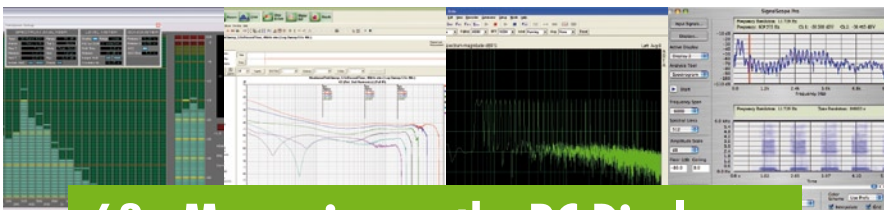
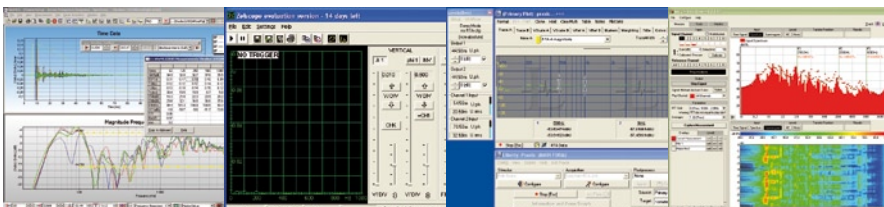
## 62 Measuring on the PC Display

In addition to its audio uses the soundcard can also be used for measuring purposes. But which software is the most appropriate? In this article we help you get oriented by giving you an overview of what can be found out there.



## projects

- 18** Display Computer
- 26** DigiButler (2)
- 32** Two-wire LCD
- 38** Elektor AVRProg
- 42** Soldering with Reflow Control
- 44** paX: a Power Amplifier with Error Correction
- 50** Protection System for Power Amplifiers
- 58** Tiny Counter
- 70** E-Blocks: Flowcode Interrupts
- 74** Design Tips: An SPI-networked microcontroller Symmetrical square wave

## technology

- 62** Measuring on the PC Display

## info & market

- 6** Colophon
- 8** Mailbox
- 12** Elektor E-book
- 14** News & New Products
- 56** Review: MikroElektronika EasyPIC5 Development System
- 80** Elektor SHOP
- 84** Sneak Preview

## infotainment

- 76** Hexadoku
- 77** Retronics: 'Alibi-Nota' telephone answering machine (1972)

# elektor international media

Elektor International Media provides a multimedia and interactive platform for everyone interested in electronics.

From professionals passionate about their work to enthusiasts with professional ambitions.

From beginner to diehard, from student to lecturer. Information, education, inspiration and entertainment.

Analogue and digital; practical and theoretical; software and hardware.

**English**  
**German**  
**Dutch**  
**French**  
**Chinese**

**Greek**  
**Spanish**  
**Swedish**  
**Finnish**

Volume 34, Number 377, May 2008

ISSN 1757-0875

*Elektor Electronics aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.*

**Publishers:** Elektor International Media, Regus Brentford,  
1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447 [www.elektor.com](http://www.elektor.com)

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription.

Elektor is published 11 times a year with a double issue for July & August.

*Elektor is also published in French, Spanish, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.*

**International Editor:**  
Wisse Hettinga ([w.hettinga@elektor.nl](mailto:w.hettinga@elektor.nl))

**Editor:** Jan Buiting ([editor@elektor.com](mailto:editor@elektor.com))

**International editorial staff:** Harry Baggen, Thijs Beckers,  
Ernst Krempelsauer, Jens Nickel, Guy Raedersdorf.

**Design staff:** Antoine Authier (Head),  
Ton Giesberts, Luc Lemmens, Jan Visser, Christian Vossen

**Editorial secretariat:** Hedwig Hennekens ([secretariaat@elektor.nl](mailto:secretariaat@elektor.nl))

**Graphic design / DTP:** Giel Dols, Mart Schroijen

**Managing Director / Publisher:** Paul Snakkers

**Marketing:** Carlo van Nistelrooy

**Customer Services:** Anouska van Ginkel

**Subscriptions:** Elektor International Media,  
Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England.  
Tel. (+44) 208 261 4509, fax: (+44) 208 261 4447  
Internet: [www.elektor.com](http://www.elektor.com)

# FPGA Course on CD-ROM

➔ Modern technology for everyone

**NEW!**



FPGAs have established a firm position in the modern electronics designer's toolkit. Until recently, these 'super components' were practically reserved for specialists in high-tech companies. That's all changed now, also because of the Elektor FPGA module. The combination of the module and the prototyping board is the perfect introduction to FPGAs. The nine lessons on the courseware CD-ROM are a step by step guide to the world of Field Programmable Gate Array technology. Subjects covered include not just digital logic and bus systems but also building an FPGA webserver, a 4-channel multimeter and a USB controller. The CD also contains PCB layout files in pdf format, a Quartus manual, project software and various supplementary instructions.

ISBN 978-90-5381-225-9 • £14.50 • US\$ 29.00

**elektor**  
SHOP

**Free of charge with  
FPGA product bundle!**  
[www.elektor.com/fpgacombi](http://www.elektor.com/fpgacombi)

**Order quickly and safe through [www.elektor.com/shop](http://www.elektor.com/shop)  
or use the Order Form near the end of the magazine**

Email: [subscriptions@elektor.com](mailto:subscriptions@elektor.com)  
Rates and terms are given on the Subscription Order Form

Head Office: Elektor International Media b.v.  
P.O. Box 11 NL-6114-ZG Susteren The Netherlands  
Telephone: (+31) 46 4389444, Fax: (+31) 46 4370161

Distribution: Seymour, 2 East Poultry Street, London EC1A, England  
Telephone: +44 207 429 4073

UK Advertising: Huson International Media, Cambridge House,  
Gogmore Lane, Chertsey, Surrey KT16 9AP, England.  
Telephone: +44 1932 564999, Fax: +44 1932 564998

Email: [p.brady@husonmedia.com](mailto:p.brady@husonmedia.com)  
Internet: [www.husonmedia.com](http://www.husonmedia.com)  
Advertising rates and terms available on request.

International Advertising: Frank van de Raadt, address as Head Office  
Email: [advertenties@elektor.nl](mailto:advertenties@elektor.nl)  
Advertising rates and terms available on request.

**Copyright Notice**  
The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Segment. b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning on recording, in whole or in part without

prior written permission from the Publishers. Such written permission must also be obtained before any part of this publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publishers to alter the text and design, and to use the contents in other Segment publications and activities. The Publishers cannot guarantee to return any material submitted to them.

**Disclaimer**  
Prices and descriptions of publication-related items subject to change.  
Errors and omissions excluded.

© Elektor International Media B.V. 2008

Printed in the Netherlands

## Compact Fluorescent lamps

Dear Editor — I liked the article on CF lamps in the January 2008 issue. It gives an insight into the requirements for operation of these miniature fluorescent lamps, but despite the attempts of various governments to inflict these units on the populous, there is still some resistance to their general use. There are many reasons for this. In Britain at least, the cost is relatively high compared to the humble incandescent lamp, although prices have dropped in the last few years. One issue with all CFLs is to know the colour emitted by them. The warm-up time can be a problem in some applications, especially in outdoor units having a short on time such as in IR detector controlled fittings at doorways. In cold weather these can take a few minutes to give a useful light, and by then, the detector is ready to switch off again.

I have used the standard BC fitting replacements for several years now, but current building regulations in the UK demand at least a certain number of low energy fittings in every new build or extension. These must be of a type that cannot accept a standard incandescent bulb as a replacement, effectively ruling out the GLS replacement lamps now becoming widely available here. We are therefore faced with fluorescent fittings, Bi-pin types or square 4D fittings.

Unfortunately, the lamp unit manufacturers have been slow to provide suitable units that are acceptable to the home user. Most of the fittings available that will only accept a non-incandescent type lamp tend to have a somewhat industrial look to them, necessitated by the requirement of providing a ballast of some kind and a place to keep said ballast away from danger. That has to include dissipation of heat in a safe manner, isolation from prying fingers and safety in failure either of lamp or ballast.

There are pendant drops made that will only accept a bi-pin lamp, but they do not readily take a standard shade as the fitting is larger than the old bayonet holder.

Then there is the lamp equivalent problem. How does one relate 18 W = 100 W and pictures of several light bulbs on the packet with the real world? In truth I have seen 5-W CFL lamps that claim to be equivalent to 30 W candle lamps, and yes they are bright, but the light produced has an eerie greenish tinge presumably due to a lack of red in the spectrum produced. By the same token, some CFLs give a stark blue-white light, and these are very bright to the point of being painful, but the quality of the light seems strange. The shadows are harsh and yet the corners of the room seem to be in darkness, despite or perhaps owing to the intensity of

the light elsewhere in the room.

It must be said that the more recent spiral and the multi loop lamps are a better colour match to tungsten lamps than they were, although perhaps efficiency has been sacrificed for colour temperature. I modified a fitting to take a 16 W 4D lamp from 2x60 W golf ball bulbs, and for some reason ordered a cool white lamp. It is very bright, but using a 2700° lamp in the same place gives a dismal, gloomy light. It is still 16 watts, but how many incandescent lamps should it have on the pack? It is all a matter of perception.

No-one seems to quote lumen output from GLS lamps (standard household bulbs). These vary enormously dependant on the construction of the filament and the coatings on the lamp in any case. A 60 W rough service lamp has a tough relatively cold filament that gives a yellow light, whilst the mushroom lamps so popular in the 1960s were fragile beyond belief and burned at a high temperature with a coiled coil filament. This gave a very white light compared to its predecessors.

Comparing wattage ratings between GLS, quartz-halogen, CFL, 'normal' fluorescent and other discharge lamps is a bit like comparing fruit, vegetables and bread. It is meaningless without colour temperature and total light output being compared.

It would be far more helpful to insist on comparison of lumens per circuit watt, which would also include losses in the ballast. One almost unknown loss outside of the electrical fraternity is that suffered in standard iron cored ballasts used for standard fluorescent lamps with switch starters. These can add 15% or more to the tube rating, thus a traditional 40 W 4-foot (1200 mm) fitting actually used a total circuit power of nearer 50 watts, and whilst the efficiency was far above that of a tungsten lamp, only recently have HF ballasts become the norm in traditional 'long' fittings.


I recently installed some new lamps in my garage, the tubes being rated at 58 W and the whole fittings claiming to be 59 W. The power factor is also close to 1 and so these are sui-


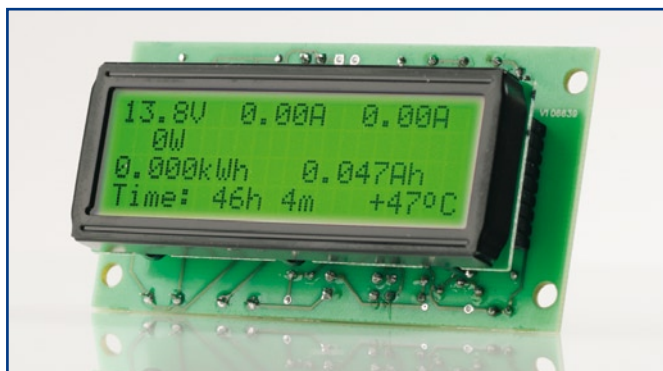
### Power meter revisited

The author of the article on the versatile DC power meter, Oliver Micac, has generated an updated version of the software for the meter. The new version makes it possible to use the meter with 60-mV DIN shunts.

The new firmware is available on the website under the original article (look for item number 070559-11 under



'Versatile DC Power Peter' in the January 2008 issue).

### Not a Summer Circuit

Okay — it's not a circuit; it's not even electronic but I think your readers might be interested in my Logic Goats. <http://www.flying-pig.co.uk/pagesv/logicgoat.html> Logic Goats are paper models

table for industrial use as well. They are soft-start, thus reducing inrush currents and have flicker-free start. The mains pollution emitted is low and they also offer possibly longer lamp life. This must be a step forward, but at the cost penalty of about twice that of a switch start unit. Contract electricians will not supply these until they are forced by legislation to use them. For me the cost penalty is not an issue for four units, but if I was supplying four thousand to a site, then offering the switch-start units would make the costing look better to the client.

Unfortunately the lamps are still a five foot long glass tube mounted on a metal box screwed to the ceiling, and we are back to the industrial look again.

What comes next? LEDs are looking promising. They are brighter by the week it seems and can be acceptable for some areas, but once more we are back to perceptions again. The GU10/GZ10 240 V dichroic type halogen lamp can now be replaced with a CFL version or an LED version. The original tends to be either 35 or 50 watts and produces a typical tungsten light with about 30° spread. The CFL version is too big for most fittings and woefully dim but only rated at 7 or 9 watts. The lack of a realistic reflector makes the light output seem poor. The LED version is an incredibly bright, bluish-white but only offers about a 5° beam. White LEDs tend to have a limited life as well. They are really blue LEDs with

a phosphor coating inside, and like fluorescent tubes, rely on this for their final colour. The light output diminishes fairly rapidly and after a year or so, a new white LED is dazzlingly bright compared to one that has been in use for the past 12 months.

All fluorescent lamps, compact or otherwise, use mercury vapour as the principle radiating component in the tube. When a current is passed through the tube the mercury vapour emits a high concentration of UV light. This is sometimes visible if the ends of the tube are not fully coated with phosphor powder, a blue glow can be seen inside the tube itself. The

UV excites the phosphors that coat the tube, and cause it to glow. The colour temperature of the light emitted depends on the phosphor mix used, and can be a range of colours from daylight through to red or blue or even UV.

The great efficiency associated with standard fluorescent lamps came from the fact that the light was emitted over an exceptionally large surface compared to a filament lamp. This gave softer shadows, less glare and a greater distribution of light over a given area. The humble tungsten filament lamp, like its predecessor the candle, was effectively a point source. With the CFL we are back to a point source (relatively speaking) so it has to be intensely bright to give a reasonable light output, as do HID lamps. Similar reasoning applies to LEDs as well. Unfortunately this tends to give them a characteristic starkness and glare. Here we go again!

The energy debate will continue no doubt, but what is the environmental effect of the CFL now poised to replace the incandescent lamp? Disposal of large quantities of dead units may be an issue, as they all contain mercury and some exotic phosphors, typically rare earth and metallic phosphor salts. The cathodes (the heater bit that glows in a switch-start fitting) are made from tungsten wire coated with barium, strontium and calcium salts, and are similar in design to an electronic valve (tube) cathode, being designed for optimum thermionic emission at low temperatures. If these things ever do replace the simple GLS lamp, even at five times the life span there will be a lot of undesirable rubbish being dumped into the ground, and no doubt even more regulation will be needed to ensure that the lamps are re-cycled in a safe manner. This cost could be inflicted on the retailer or the manufacturer, putting up the price and making their use less attractive.

There is also the question of energy required to actually make, package and distribute these lamps. They may use one fifth of the energy in their life time, but how much energy is expended making each one in comparison to its more humble cousin? The glass envelope is far more complex than a single bulb, and the electronics for the CFL ballast inevitably has to be made and built. Despite the maker's claims, the life of the CFL can be depressingly short, especially in the very compact designs that have a cooking hot ballast in the centre of the spiral fitting.

Are we in danger of moving the energy consumption and pollution generation from the end user to the manufacturing and disposal process, or like the electric car, from our cities to the power stations?

**Andrew Denham (UK)**

of working logic gates but in goat form — you can see a Youtube video of them in action here: [www.youtube.com/watch?v=vu3o6JNclRQ](http://www.youtube.com/watch?v=vu3o6JNclRQ)  
Best wishes

**Rob Ives (Flying Pig)**

*In a word, brilliant! Everyone, put down your soldering irons and get out your scissors and cardboard.*



### The 'Dekatron' decimal counter valve (1)

Dear Sir — your magazine used to be good, unfortunately it swerves time and again to high-tech subjects. What good are FPGAs and microcontrollers to me when I can't get any use from them? To be able to follow your construction projects you need an academic degree and vast amounts of 'pocket money' to buy special

parts and programming tools. That used to be different, and better, in the past.

For example, in your March 2008 issue you present the Dekatron counter valve with a schematic. Where, please, should normal people go to obtain, at a reasonable price, such parts declared obsolete decades ago? Kind of utopian, no? I am not so affluent as to spend my hard earned cash

on this grot. Not my cup of tea and I am cancelling my subscription.

**G. Kratzin (Germany)**

*A bemusing response indicating that Mr Kratzin has missed the point about our Retronics articles entirely, see the footer printed with every instalment.*

### Anti-Standby Switch — a sequel on safety

Dear Editor —on your green standby switch project (January 2008, Ed.), a current transformer MUST always work into a very low impedance load. It is extremely dangerous to not have a low-value load resistor across the secondary, across which a small ac voltage is developed. So dangerous that some commercial current transformer manufacturers install the load resistor within the transformer module. Without such a load, under transient and high current events several thousand volts can be developed across the secondary as it tries to drive its secondary current into a non-existent load.

Without a load a CT looks like a voltage step-up transformer multiplying the 240VAC mains input being pushed through it. Only the saturation of the core limits the energy.

The secondary winding, load resistor and PCB must be rated for the divided down primary load current. For example if the primary is rated for 13 Amps and there is a 1:10 turns ratio then the secondary must be designed for a steady state current of 1.3 Amps and a peak current of say 5 Amps (typical domestic 0.2 second fault current is 50 Amps). Obviously with a low impedance load and suitable conductors the power dissipation is very small.

**(name withheld at request of correspondent)**

*The designer, Thomas Scherer, replies*

Dear Jan — I thank the correspondent for being so concerned about security issues. But in my eyes he is too concerned about this and misses the point in some way. Specifically, the rule he mentions is no law of nature. In fact this is pure theory which doesn't match the real circumstances. Especially transients may happen with every inductive load, with coils and ordinary transformers too. This is nothing special. But they do not occur at the high energy levels he mentions. Therefore this never is as dangerous as you believe — otherwise a big part of commercially produced electronic devices would be dangerous. What he has not considered really is the amount of energy a pulse can have which is provided by this little current transformer. Like you said: this energy is limited by the core of this transformer and therefore is not insignificant. Second, there is no 'no load' condition. Connected to the secondary coil of the current transformer is found a 10-k resistor in series with a 100-nF capacitor which has nearly zero ohms for transients. A transient pulse of 1 kV peak should produce a current of 0.1 A which equals a peak power of about 100 W (for some  $\mu$ s). This little transformer is never able to produce such a peak power. And if you still believe in your theory: I measured the voltages which occur at the secondary windings of the current transformer during shutting off currents of 10 A on the primary side. The result is that the maximum measured pulse peaks do not reach 20 V. Is this dangerous? Not even for the following opamp, I believe, because the voltage at the 100-nF capacitor never exceeds 1 V.

Lastly the correspondent is completely wrong in thinking that the parts at the secondary winding of the current transformer need to withstand 5 A peaks. This really really never will happen. This is a practical case of impossibility ;-) So I am really sure the PCB is totally

safe and nobody can be killed but your theory of unsafety....

**Dr. Thomas Scherer**

### The original correspondent replies

Dear Jan — as your contributor Thomas points out it is all a matter of coupling. The CTs I was working with were designed to accurately measure (to within a percent or so) the primary current (typically 300 A) and in that application had many thousands of secondary turns to scale the primary current down to an electronics-friendly few milliamps using a substantial core. I have seen capacitors and ICs explode off the board when a load of 1 ohm was inadvertently omitted and in once case a senior engineer was thrown the length of the test bay when a technician



perhaps deliberately removed the working load.

In this application the CT is mostly sensing any significant primary current. I do not fully accept that the capacitor is a load since its contribution would be out of phase. The transient I am concerned about is the switch-on surge of the connected appliance, which with modern switch mode power supplies can sometimes be as much as 50 A for the first cycle.

So-called power factor corrected PSUs sometimes have a lower in-rush current. Providing the core saturates at the odd amp or so the energy fed into the secondary is relatively

small. Even so the 10 k resistor becomes a safety item, should this fail, downstream electronics would probably be damaged.

At one time we considered putting voltage limiters across the CT secondary but our Safety Committee could not resolve a satisfactory fail-to-safe mechanism and concluded that the reliability of a quality ohmic load was such that it far less likely to fail than the protection components proposed to protect the system should it fail. Every component was subject to such analysis which sometimes took weeks and sometimes needed experiments on live systems with induced failures.

Perhaps Elektor should publish a follow-up advising readers only to use the specified core and winding specification and not to substitute a genuine current transformer which is likely to have a very significantly higher coupling efficiency. Current transformers are very weird components that few readers are likely to have had experience of. Although I never had a shock or caused others to have a shock off them, what I have seen has made me very wary of such an innocent looking device!

## MailBox Terms

- Publication of reader's correspondence is at the discretion of the Editor.
  - Viewpoints expressed by correspondents are not necessarily those of the Editor or Publisher.
  - Correspondence may be translated or edited for length, clarity and style.
- When replying to Mailbox correspondence, please quote Issue number.
- Please send your MailBox correspondence to:

editor@elektor.com or  
Elektor, The Editor,  
1000 Great West Road,  
Brentford TW8 9HH, England.

## EasyPIC5 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



Following tradition of its predecessor EasyPIC4 as one of the best PIC development systems on the market, EasyPIC5 has more new features for the same price. The system supports 8-, 14, 18, 20, 28 and 40 pin PIC microcontrollers (it comes with a PIC16F877A). **USB 2.0** on-board programmer with **mikroICD** (In-Circuit Debugger) enables very efficient debugging and faster prototype development. Examples in **C**, **BASIC** and **Pascal** language are provided with the board. **Touch screen** controller with connector is available on-board.

## LV24-33 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



System supports 64, 80 and 100 pins **PIC24F/24H/dsPIC33F** microcontrollers (it comes with PIC24FJ96GA010 - PIC24 16-bit Microcontroller, 96 KB Flash Memory, 8 KB RAM in 100 Pin Package). Examples in **BASIC**, **PASCAL** and **C** are included with(in) the system. You can choose between USB and External Power supply. **LV 24-33** has many features that make your development easy. **USB 2.0** on-board programmer with **mikroICD** (In-Circuit Debugger) enables very efficient debugging and faster prototype development.

## PICPLC16B Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



**PICPLC16B** is a system designed for controlling industrial systems and machines. 16 inputs with **optocouplers** and 16 **relays** (up to 10A) can satisfy many industrial needs. The ultra fast **mikroICD** (In-circuit Debugger) enables very efficient debugging and faster prototype development. Features : **RS485**, **RS232**, **Serial Ethernet**, **USB 2.0** on-board programmer and **mikroICD** (In-Circuit Debugger) on-board.

## EasyAVR5 Development Board

with on-board USB 2.0 programmer



The system supports **8, 14, 20, 28 and 40 pin** microcontrollers (it comes with ATMEGA16). Each jumper, element and pin is clearly marked on the board. It is possible to test the most of industrial needs on the system: temperature controllers, counters, timers etc. **EasyAVR5** is an easy-to-use Atmel AVR development system. On-board **USB 2.0** programmer makes your development easy. Examples in **BASIC** and **Pascal** language are provided with the board.

## EasyPSoc3 Development Board

with on-board USB 2.0 programmer



The system supports **8, 20, 28 and 48 pin** microcontrollers (it comes with CY8C27843). Each jumper, element and pin is clearly marked on the board. **EasyPSoc3** is an easy-to-use PSoC development system. On-board **USB 2.0** programmer provides fast and easy in-system programming.

## Uni-DS 3 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer



The system supports **PIC, dsPIC, AVR, 8051, PSoC, ARM** and **PSoc** microcontrollers with a large number of peripherals. In order to continue working with different chip in the same development environment, you just need to switch a card. **UNI-DS3** has many features that make your development easy. You can choose between **USB** or **External Power** supply. Each MCU card has its own **USB 2.0** programmer!

## EasydsPIC4 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



The system supports **18, 28 and 40 pin** microcontrollers (it comes with dsPIC30F4013 general purpose microcontroller with internal 12-bit ADC). **EasydsPIC4** has many features that make your development easy. Many of these already made examples in **C**, **BASIC** and **PASCAL** language guarantee successful use of the system. Ultra fast **USB 2.0** on-board programmer and **mikroICD** (In-circuit Debugger) enables very efficient debugging and faster prototype developing.

## EasyARM Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer



**EasyARM** board comes with Philips LPC2214 microcontroller. Each jumper, element and pin is clearly marked on the board. It is possible to test most of industrial needs on the system: temperature controllers, counters, timers etc. **EasyARM** has many features making your development easy. One of them is on-board **USB 2.0** programmer with automatic switch between 'run' and 'programming' mode. Examples in **C** language are provided with the board.

## BIGAVR Development Board

with on-board USB 2.0 programmer



The system supports 64-pin and 100-pin AVR microcontrollers (it is delivered with ATMEGA128 working at 10MHz). Many already made examples guarantee successful use of the system. **BIGAVR** is easy to use Atmel AVR development system. **BIGAVR** has many features that makes your development easy. You can choose between **USB** or **External Power** supply. **BIGAVR** also supports Character LCD as well as Graphic LCD.

## Easy8051B Development Board

with on-board USB 2.0 programmer



System is compatible with **14, 16, 20, 28 and 40 pin** microcontrollers (it comes with AT89S8253). Also there are **PLCC44** and **PLCC32** sockets for 32 and 44 pin microcontrollers. **USB 2.0 Programmer** is supplied from the system and the programming can be done without taking the microcontroller out.

## LV 18FJ Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



System supports 64, 80 and 100 pin **PIC18FxxJxx** microcontrollers (it comes with PIC18F87J60 - PIC18 Microcontroller with an integrated 10Mbps Ethernet communications peripheral, 80 Pin Package). **LV 18FJ** is easy to use Microchip PIC18FxxJxx development system. **USB 2.0** on-board programmer with **mikroICD** (In-Circuit Debugger) enables very efficient debugging and faster prototype development. Examples in **C**, **BASIC** and **Pascal** language are provided with the board.

## dsPICPRO 3 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



The system supports dsPIC microcontrollers in 64 and 80 pins packages. It is delivered with dsPIC30F6014A microcontroller. **dsPICPRO3** development system is a full-featured development board for the Microchip dsPIC MCU. dsPICPRO3 board allows microcontroller to be interfaced with external circuits and a broad range of peripheral devices. This development board has an on-board **USB 2.0** programmer and integrated connectors for MMC/SD memory cards, 2 x RS232 port, RS485, CAN, on-board ENC28J60 Ethernet Controller, DAC etc...

## BIGPIC5 Development Board

Complete Hardware and Software solution with on-board USB 2.0 programmer and mikroICD



System supports the latest (**64**) and **80-pin** PIC microcontrollers (it is delivered with PIC18F8520). Many of these already made examples in **C**, **BASIC** and **Pascal** language guarantee successful use of the system. **Touch screen** controller with connector is available on-board. This development board has an on-board ultra fast on-board **USB 2.0** programmer, **mikroICD** (In-circuit Debugger) and integrated connectors for MMC/SD memory cards, 2 x RS232 port, RS485, CAN, on-board RTC, PS/2 connector, DAC etc...

## mikroElektronika Compilers

Pascal, Basic and C Compilers for various microcontrollers



Supporting an impressive range of microcontrollers, an easy-to-use IDE, hundreds of ready-to-use functions and many integrated tools makes MikroElektronika compilers one of the best choices on the market today. Besides mikroICD, mikroElektronika compilers offer a statistical module, simulator, bitmap generator for graphic displays, 7-segment display conversion tool, ASCII table, HTML code export, communication tools for SD/MMC, UDP (Ethernet) and USB, EEPROM editor, programming mode management, etc.

Each compiler has many routines and examples such as EEPROM, FLASH and MMC, reading/writing SD and CF cards, writing character and graphics on LCDs, manipulation of push-buttons, 4x4 keyboard and PS/2 keyboard input, generation of signals and sounds, character string manipulation, mathematical calculations, I2C, SPI, RS232, CAN, USB, RS485 and OneWire communications, Manchester coding management, logical and numerical conversion, PWM signals, interrupts, etc. The CD-ROM contains many already-written and tested programs to use with our development boards.

mikroElektronika manufactures competitive development systems. We deliver our products across the globe and our satisfied customers are the best guarantee of our first-rate service. The company is an official consultant on the PIC microcontrollers and the third party partner of Microchip company. We are also an official consultant and third party partner of Cypress Semiconductors since 2002 and official consultant of Philips Electronics company as well. All our products are RoHS compliant.

<http://www.mikroe.com/en/distributors/>

Find your distributor: UK, USA, Germany, Japan, France, Greece, Turkey, Italy, Slovenia, Croatia, Macedonia, Pakistan, Malaysia, Austria, Taiwan, Lebanon, Syria, Egypt, Portugal, India, Thailand, Taiwan, Czech and Slovak Republic.



**CAN-1 Board** - Interface CAN via MCP2551.

**CANSPI Board** - Make CAN network with SPI interface.

**RS485 Board** - Connect devices into RS-485 network

**Serial Ethernet** - Make ethernet network with SPI interface (ENC28J60).

**IrDA2 Board** - IrDA2 serve as wireless RS232 communication between two MCU's.



**CF Board** - Easy way to use Compact flash in your design.

**MMC/SD Board** - Easy way to use MMC and SD cards in your design.

**EEPROM Board** - Serial EEPROM board via I2C interface.

**RTC Board** - PCF8583 RTC with battery backup.



**ADC Board** - 12-bit analog-to-digital converter (ADC) with 4 inputs.

**DAC Board** - 12-bit digital-to-analog converter (DAC) with SPI.

**Keypad 4x4 Board** - Add keypad to your application.

**Accel. Board** - Accel. is an electronic device that measures acceleration forces.

**PICFlash** with mikroICD support



**PICFlash programmer** - an ultra fast USB 2.0 programmer for the PIC microcontrollers. Continuing its tradition as one of the fastest PIC programmer on the market, a new PICFlash with mikroICD now supports more PIC MCUs giving developer a wider choice of PIC MCU for further prototype development. **mikroICD** debugger enables you to execute mikroC / mikroPascal / mikroBasic programs on the host PIC microcontroller and view variable values, Special Function Registers (SFR), memory and EEPROM while the program is running.

- All of our products are shipped in special protective boxes.

- On-line secure ordering provides fast and safe way of buying our products.

Please visit our website for more info <http://www.mikroe.com>

SOFTWARE AND HARDWARE SOLUTIONS FOR EMBEDDED WORLD

**Free book!**  
get it at [www.elektor.com/ebook](http://www.elektor.com/ebook)


# 15 Elektor Blockbusters

## Free e-book for all Elektor readers




Each month Elektor magazine is packed with fine articles and challenging projects. Our archive going back to the mid-1970s, you can well imagine the immense repository of articles published in your favourite electronics magazine. Especially for all faithful Elektor readers we selected top-ranking articles from our recent issues and compiled them into the free e-book title '15 Elektor Blockbusters'. Visit the Elektor website today and download this collector's item — it's exclusive and all free!

Elektor likes to do a little extra for its readers, like a CAD software CD-ROM or the 24-page 'tinker-away' i-TRIXX supplement in the centre of the December issue. Our subscribers enjoy the additional luxury of receiving, via the address carrier, advice on exclusive offers and discounts that together can add up to considerable savings. Now, we add a free e-book for all readers: '15 Elektor Blockbusters' — an exclusive collection of top ranking articles from recent Elektor issues.


Getting your copy of the e-book is easy, fire up your Internet browser and go to [www.elektor.com/ebook](http://www.elektor.com/ebook). As a registered user of the Elektor website you are just one click away from '15 Elektor Blockbusters'. No problem if you are not yet a registered user of our website. After a few easy steps you will receive your personal login data and then '15 Elektor Blockbusters' is also available to you for downloading.

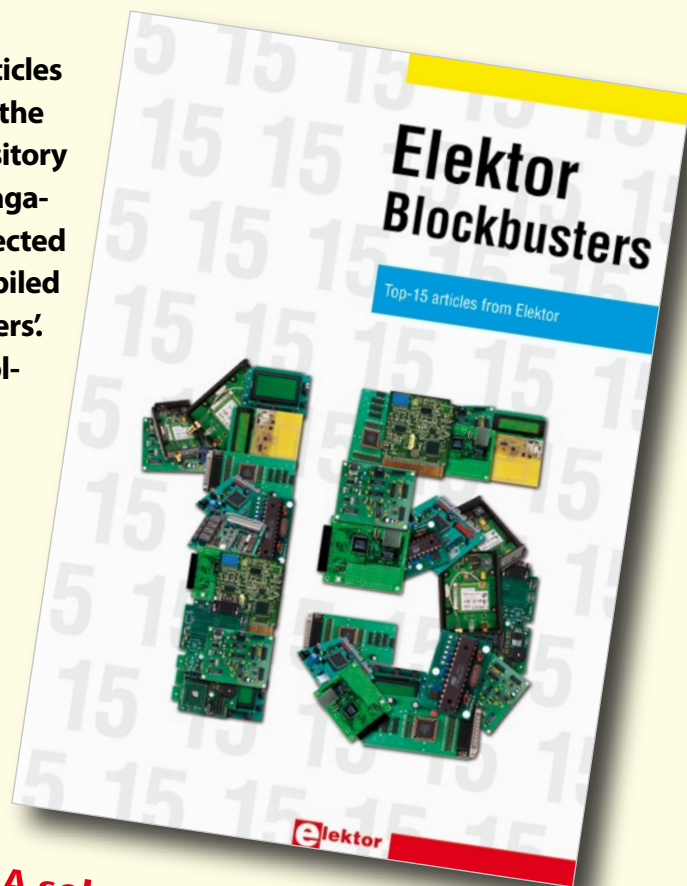

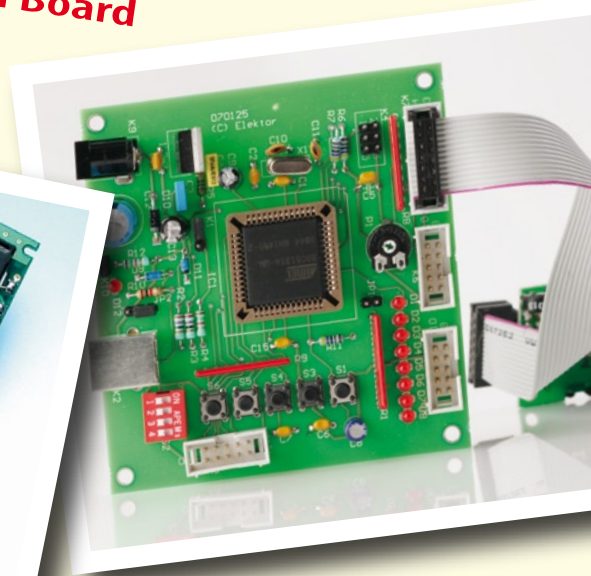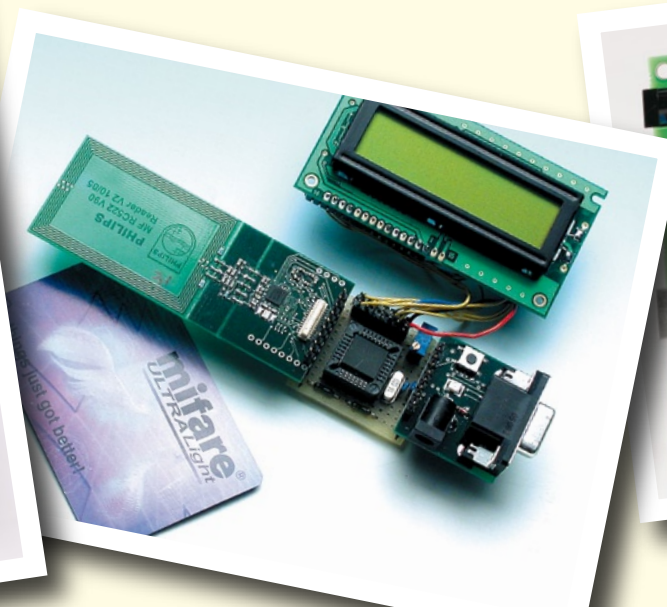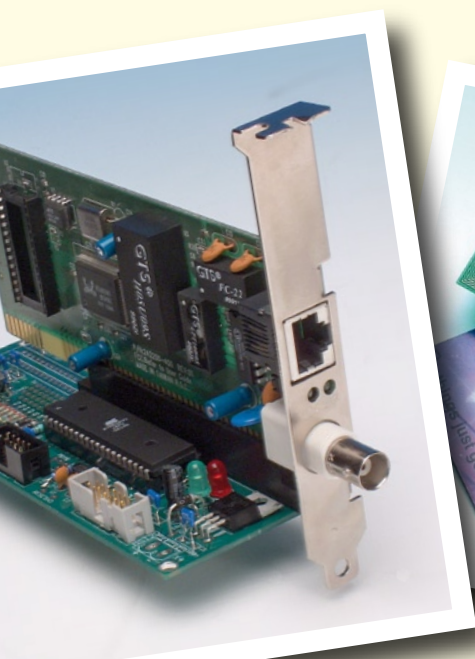- A selection from the contents**
- **Elektor RFID Reader**
  - **Software Defined Radio**
  - **Micro Webserver**
  - **USB Flash Board**


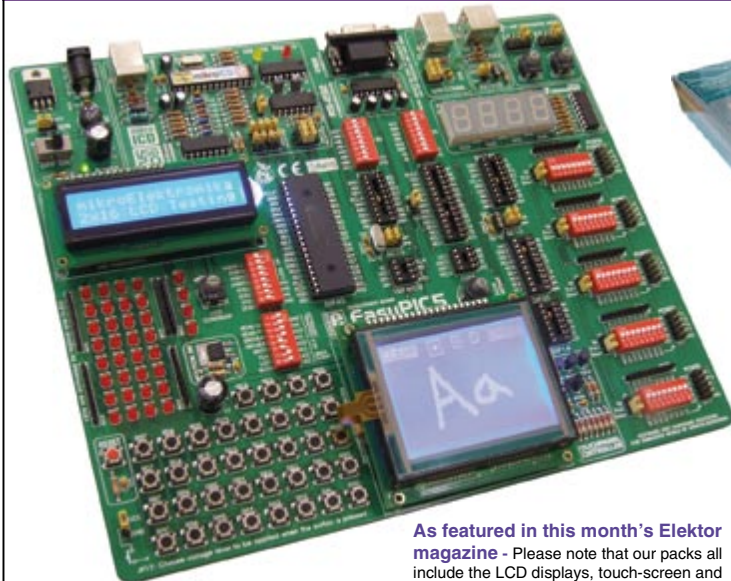
## EasyPIC5 Starter Packs—everything needed to learn about and develop with PIC microcontrollers from only £99



Four starter packs available, all of which include the EasyPIC5 development board, USB power/programming lead, blue backlit 16x2 character and 128x64 graphic LCDs, touch-screen overlay for GLCD, RS-232 lead, PIC16F877A 40-pin microcontroller and DS1820 temperature sensor plus manuals and software.

### EasyPIC5 Starter Pack - £99

Our EasyPIC5 Starter Pack is ideal for those wishing to learn about and program using assembly language or other makes of compiler. The pack contains the EasyPIC5 board, all required leads, character and graphic LCDs, touch-screen, PIC16F877A MCU and DS1820 temperature sensor. Exclusive to Paltronix, the pack also includes a getting started guide, tutorials and example programs—ideal for newcomers to microcontrollers.

### EasyPIC5 BASIC Starter Pack - £149

### EasyPIC5 C Starter Pack - £189

### EasyPIC5 Pascal Starter Pack - £149

Get off to the best start with the EasyPIC5 and save money with one of our compiler starter packs, which include the contents of the above EasyPIC5 Starter Pack plus a full version of MikroElektronika's mikroBASIC, mikroC or mikroPascal PIC compilers. These user-friendly compilers feature in-circuit debugging when used with the EasyPIC5 and also provide library routines to support all the EasyPIC5's built-in I/O devices and optional add-on boards.

**As featured in this month's Elektor magazine** - Please note that our packs all include the LCD displays, touch-screen and DS1820 temperature sensor.

MikroElektronika's EasyPIC5 development system simply must be the most versatile and best value PIC development system on the market. The board supports Flash-programmable devices in the PIC10F, 12F, 16F and 18F families in 8, 14, 18, 20, 28 and 40-pin packages and features a fast built-in USB2.0-based programmer. Also on the board are a useful range of I/O devices such as LEDs, pushbutton switches, potentiometers, RS-232 interface, USB and PS/2 connectors and provision for the easy fitting of character and graphic LCDs, touch-screen and DS1820 temperature sensor (all of which are supplied in our starter packs). Clearly labelled DIP-switches and jumpers allow any I/O devices not being used to be disabled and all of the PIC's I/O lines are available on IDC headers for easy expansion using MikroElektronika's extensive range of add-on boards or for connection to your own circuits. Detailed documentation and example programs and our own getting started guide and tutorial make the EasyPIC5 ideal for beginners and experienced users alike.

### UNI-DS3 Universal Development System



Work with various MCUs using one development board with the **UNI-DS3**. Currently supporting PIC, dsPIC, AVR, 8051, ARM and PSoC devices, the UNI-DS3 has a wide range of I/O features from £109 including main board and one plug-on MCU card.

We stock all MikroElektronika development and add-on boards and PIC, dsPIC/16-bit PIC, AVR and 8051 compilers.

### dsPICPRO3 Development System



The new **dsPICPRO3** is a development system for the dsPIC with advanced I/O and communications devices including RS-232, RS-485, CAN, Ethernet, real-time clock, SD card reader and displays. Starter packs priced from £149.

We stock a large range of similar development systems for PIC, dsPIC, AVR, 8051, ARM and PSoC microcontrollers.

### PICPLC16B Control System



The **PICPLC16B** makes an ideal platform for developing and implementing control and automation applications. This PIC microcontroller-based board has 16 relay outputs, 16 opto-isolated inputs plus RS-232, RS-485 and Ethernet interfaces for £99.

A wide range of microcontroller and PC-based control boards and add-ons are also available.

### PoScope Multi-Function Instrument



The **PoScope** features a 16-channel logic analyser with I2C, SPI, 1-wire and UART serial bus decoding, dual-channel oscilloscope, pattern generator, spectrum analyser, chart recorder and square-wave/PWM generator in one low-cost instrument for £79.

We also stock a range of probes and test leads suitable for use with the PoScope as well as money-saving bundles.

### LAP-16128U Logic Analyser



The **LAP-16128U** from ZeroPlus is a powerful 16-channel 200MHz logic analyser with UART, I2C and SPI protocol decoding priced from £195. Further protocol decoding options available including 1-wire, Microwire, CAN, LIN, PS/2 and USB.

We can supply all ZeroPlus logic analysers and advanced protocol decoding options.

### Leaper-48 Universal Device Programmer



The **Leaper-48** is a USB-based universal device programmer supporting an extensive range of memories, programmable logic devices, microcontrollers and digital signal processors at a low price of £295. Please see our website for full list of supported devices.

We also stock Leap device programmers for EPROM/EEPROM/Flash EPROM, 8051 and PIC.

### Robo-PICA Robot Experiment Pack



Start experimenting with robotics with the **Robo-PICA** robot experiment pack. Contains everything required to build various PIC microcontroller-based robot projects and carry out a large range of fun experiments for £89.

Similar robot kits stocked based on 68HC11, 8051, AVR and BASIC Stamp plus large range of accessories.

### NX-51 V2 Microcontroller Trainer



Designed specifically for teaching 8051 microcontroller interfacing and programming, the **NX-51 V2** incorporates a useful range of I/O devices and comes complete with detailed example programs for £99.

Other training systems available for microcontroller and electronics teaching.

### IDL Series Circuit Labs



The **IDL-400** Logic Trainer, **IDL-600** Analogue Lab and **IDL-800** Digital Lab all feature a large solderless breadboard, built-in DC power supplies, switches, displays and useful logic gates or test features and are priced from just £179.

We have a large range of prototyping products from breadboards to advanced digital and analogue circuit labs.

Please see our website at [www.paltronix.com](http://www.paltronix.com) for further details of these and other products  
We stock components, control systems, development tools, educational products, prototyping aids and test equipment

Paltronix Limited, Unit 3 Dolphin Lane, 35 High Street, Southampton, SO14 2DF | Tel: 0845 226 9451 | Fax: 0845 226 9452 | Email: [sales@paltronix.com](mailto:sales@paltronix.com)  
Secure on-line ordering. Major credit and debit cards accepted. Prices exclude delivery and VAT.

## USB Digitisers & Digital Multimeter

National Instruments has announced the release of the NI USB-5132/5133 digitisers and the NI USB-4065 6½-digit digital multimeter (DMM). These small, lightweight instruments feature bus-powered and plug-and-play operation, which makes them ideal for portable, benchtop and OEM applications. They are also shipped with NI LabVIEW SignalExpress LE, an interactive measurement workbench for quickly acquiring, analysing and presenting data, with no programming required.

The USB-5132/5133 50 MS/s and 100 MS/s digitisers offer two simultaneously sampled channels with 8-bit resolution. These USB digitisers feature 10 input ranges from 40 mV to 40 V and programmable DC offset, and come standard with 4 MB/



ch of onboard memory for measurements requiring extended data captures. The USB-4065 DMM offers 6½ digits of resolution at up to 10 readings per second and up to 4 MB/

ch of onboard memory for measurements requiring extended data captures. The USB-4065 DMM offers 6½ digits of resolution at up to 10 readings per second and up to 3,000 readings per second at lower resolutions. With  $\pm 300$  V of isola-

tion, current measurements up to 3 A and 2- or 4-wire resistance measurements, the USB-4065 offers a complete multimeter solution for portable 6½-digit measurement needs.

Each of these instruments includes its own soft front panel, which provides an interactive, familiar interface to get up and running quickly. For data logging applications, engineers can easily combine the USB-5132/5133 digitisers or the USB-4065 6½-digit DMM with LabVIEW SignalExpress measurement software. Together, this intuitive software and the bus-powered architecture of these new instruments are extending the ease-of-use and performance of portable measurements.

[www.ni.com/modularinstruments/usb](http://www.ni.com/modularinstruments/usb)

(080073-VII)

## Verotec strengthens direct sales route and technical support

Verotec, the successor company to Vero Electronics and APW, announce that a new online shop will be launched on March 1st 2008. Well-known APW / VERO products such as KM6-II Subracks & Front Panels, Diplomat, LBX & Verotec Cases, Fan Trays, 19" rack cases and many others can now be purchased either directly or through the new on-line shop. Selected sizes from all ranges are also available from the leading pan-European catalogue distributors

Farnell and RS Components.

Verotec standard products are available direct on short lead times with many popular items being available ex-stock. Customisation is a very common requirement for all types of sub rack and enclosure; Verotec's experienced technical support team are available to advise on the best product for any particular application and to provide quotations for custom versions. The intrinsic experience,

knowledge base, tooling and production equipment availability normally means that Verotec is able to offer the most competitive price and lowest time to market for any standard enclosure configured to meet the project needs.

For 50 years, the name VERO has been synonymous with high quality electronics packaging. The majority of Verotec employees are ex VERO and APW; they have extensive knowledge and experience

of the design, engineering, manufacturing and customisation of all the products. The traditionally high quality, fit and finish associated with the VERO name is being maintained and bettered; in-house technical and commercial departments provide support on all aspects of the product range.

[www.verotecshop.co.uk](http://www.verotecshop.co.uk)

(080087-IX)

## PS-900 soldering system

OK International has introduced the PS-900 Soldering System. Controlled and powered by SmartHeat® Technology, the PS-900 provides users with exceptional capability to solder high thermal demand applications including lead-free solders, multi-layer boards, and large mass components.

The PS-900 is a fixed temperature system that varies power to match the thermal demand of the device being soldered. SmartHeat® Technology provides an exceptionally fast response when under load while eliminating the potential for thermal overshoot. The result is a high quality solder joint formed at safe, controlled temperatures.

The PS-900 has a compact footprint power supply in a rugged,

lightweight cast aluminum housing. The system includes an ergonomic soldering handpiece, an Auto-sleep Workstand for the soldering iron, and a temperature resistant tip removal pad.

Over 30 tip geometries are available in dimensions as small as 0.4 mm (.016") to 5 mm (.197"). This range of tips allows users to perform a wide variety of applications including single point soldering of through-hole and SMD leads, drag soldering SMD leads, touch-up and pad clean-up. All PS-900 tips employ the use of high plating thickness. This feature protects the tip from flux attack, therefore, prolonging tip life and lowering operating costs.

The Auto-Sleep workstand, which




is unique to OK International, automatically reduces the tip temperature during idle periods, providing increased tip life. Moreover, with SmartHeat® Technology, the PS-900 does not require calibration.

This eliminates costly down-time typically associated with conventional soldering systems.

<http://www.okinternational.com>

(080073-IX)
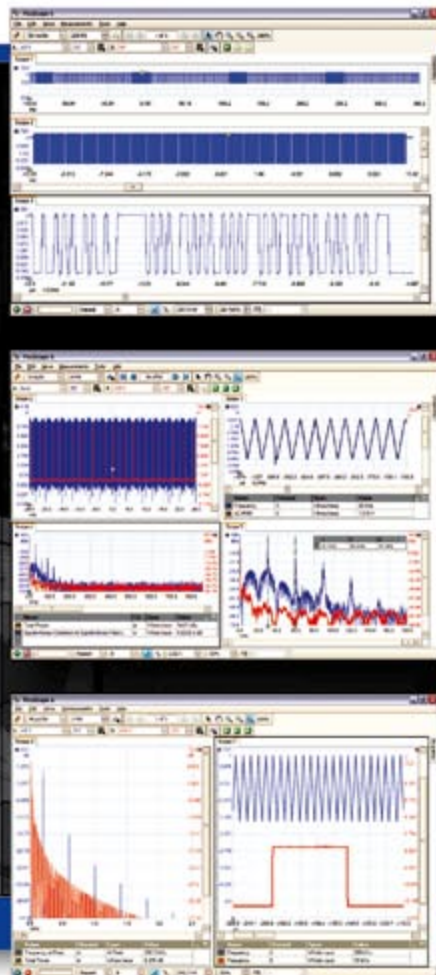
# USB Connected High Speed PC Oscilloscopes



5000 SERIES

## PicoScope 5000 Series The No Compromise PC Oscilloscopes

With class-leading bandwidth, sampling rate, memory depth and an array of advanced high-end features, the PicoScope 5000 PC Oscilloscopes give you the features and performance you need without any compromise.

**250 MHz bandwidth**  
**1 GS/s real-time sample rate**  
**128 megasample record length**

### Advanced Triggers

In addition to the standard triggers the PicoScope 5000 series comes as standard with pulse width, window, dropout, delay, and logic level triggering.

**250 MHz Spectrum Analyser**  
**High-speed USB 2.0 Connection**

**Automatic Measurements**

**Arbitrary Waveform Generator**

Define your own waveforms or select from 8 predefined signals with the 12 bit, 125 MS/s arbitrary waveform generator.

### Waveform Playback Tool

PicoScope software now allows you to go back, review, and analyse up to 1000 captures within its waveform playback tool.

**pico**  
Technology

3000 SERIES

The PicoScope 3000 Series of oscilloscopes from Pico Technology includes general purpose and high resolution models: With 12 bit resolution and 1% accuracy, the 10MHz PicoScope 3424 is able to detect changes as small as 0.024% (244ppm) – making it the ideal 4-channel oscilloscope for analog design and analysis. The higher speed 8 bit models in the PicoScope 3000 series feature sampling rates up to 200MS/s and up to 1 MS/s record lengths for general purpose and portable applications.



2000 SERIES

The PicoScope 2000 series oscilloscopes offer single and dual channel units that offer highly portable/low cost solutions to general purpose testing. The award winning 25MHz handheld PicoScope 2105 fits comfortably into the palm of your hand yet still includes the powerful features found in larger oscilloscopes.



VISIT

**[www.picotech.com/scope468](http://www.picotech.com/scope468)**

to check out our full line of PC-based instruments or call **01480 396 395** for information and a product catalogue

## Remembering Sir Arthur C. Clarke

**source: ITU News**

Science fiction writer and visionary Sir Arthur C. Clarke died on 19 March 2008 in Colombo, Sri Lanka, at the age of 90. He was born on 16 December 1917 in Minehead, Somerset in the United Kingdom and moved to Sri Lanka; then called Ceylon, in 1956.

The international telecommunication community will remember Sir Arthur for making popular the concept of using the geostationary orbit for communications. In October 1945, Clarke published in the British magazine *Wireless World* a technical paper entitled „Extra-terrestrial Relays — Can Rocket Stations Give World-wide Radio Coverage?“ The paper established the feasibility of artificial satellites as relay stations for Earth-based communications. Clarke predicted that one day communications around the world would be possible via a network of three geostationary satellites spaced at equal intervals around the Earth's equator.

Nearly two decades later, in 1964, Syncom 3 became the

first geostationary satellite to finally fulfil Clarke's prediction. Later that year, Syncom 3 was used to relay television coverage of


ons of people around the globe. In 1954, Clarke had also proposed using satellites in meteorology. Today, we cannot imagine predicting

*Village*, published in 1992, Clarke wrote: „Sometimes I'm afraid that you people down on Earth take the space stations for granted, forgetting the skill and science and courage that went to make them. How, often do you stop to think that all your long-distance phone calls, and most of your TV programmes are routed through one or the other of the satellites? And how often do you give any credit to the meteorologists for the fact that weather forecasts are no longer the joke they were to our grandfathers, but are dead accurate ninety-nine percent of the time?“

Clarke wrote more than 80 books involving science, and science fiction. His short story *The Sentinel* served as the basis for Stanley Kubrick's 1968 film *2001: A Space Odyssey*. His other famous works include *The Exploration of Space*, *The Promise of Space*, *The Fountains of Paradise*, his semi-autobiographical novel *Glide Path*, and *Childhood's End*. Before his death, Clarke had just reviewed the manuscript of his latest novel, *The Last Theorem*.

(080144-IX)

Photo by BILLYE CUTCHEEN

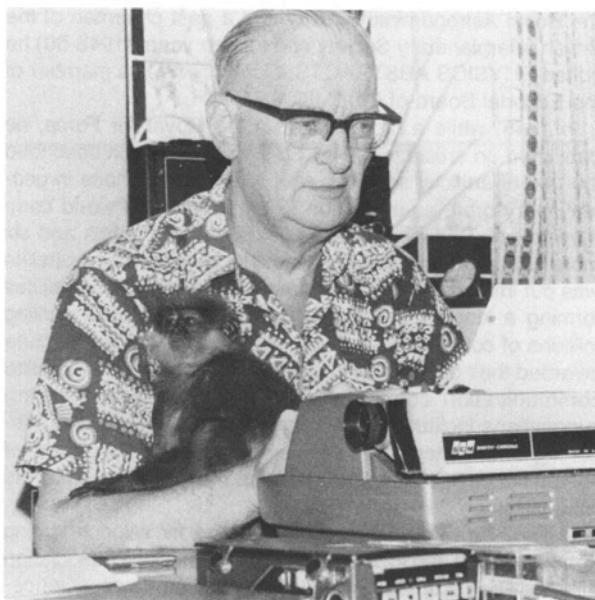

Clarke and friend.

the Summer Olympic Games in Tokyo to the United States — the first television transmission over the Pacific Ocean. Now, there are hundreds of satellites in orbit and providing communications to milli-


the weather without using dedicated meteorological satellites.

Looking back on these developments, in his book *How the World Was One — Beyond the Global*
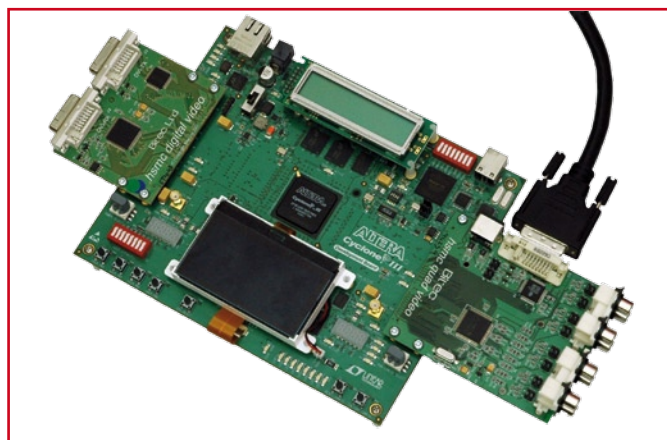
## Altera & Bitec: next-generation video system development

Altera and Bitec Ltd. jointly announced the availability of a video development kit that enables designers to rapidly develop and prototype high-performance, cost-sensitive video applications. At the heart of the kit are Altera's Cyclone® III FPGAs, which are an ideal video processing platform given the device's large parallel processing capabilities with up to 288 multipliers, 4-Mbit embedded memory blocks, and low power consumption. The kit supports multiple video I/O formats, allowing video application developers to quickly develop, debug, and prototype designs using their lab video signals and displays.

The video development kit features a Cyclone III development board with two high-speed Mezzanine Connector (HSMC)-based video



interface daughtercards developed by Bitec. The kit supports composite, S-video, DVI and RGB video and contains:

- Cyclone III EP3C120F780 development board
- Quad-Video HSMC daughter-

card (8 composite or 4 S-Video inputs)

- DVI HSMC daughtercard and DVI cable
- Quartus® II Web Edition software
- Access to Altera® OpenCore

Plus evaluation intellectual property (IP) megafunctions including the Video and Image Processing (VIP) Suite


- A CD-ROM with a video mosaic reference design developed by Bitec

The Cyclone III FPGA-based video development kit is currently available exclusively through Bitec. Interested customers can find additional information about the kit and general technology at the websites below.

[www.bitec.ltd.uk/ciii\\_video\\_dev\\_kit.html](http://www.bitec.ltd.uk/ciii_video_dev_kit.html)  
[www.altera.com/devkits](http://www.altera.com/devkits)  
[www.altera.com/products/ip/dsp/image\\_video\\_processing/m-alt-vipsuite.html](http://www.altera.com/products/ip/dsp/image_video_processing/m-alt-vipsuite.html)

(080144-VI)

# More Efficient 3-Phase Motor Control

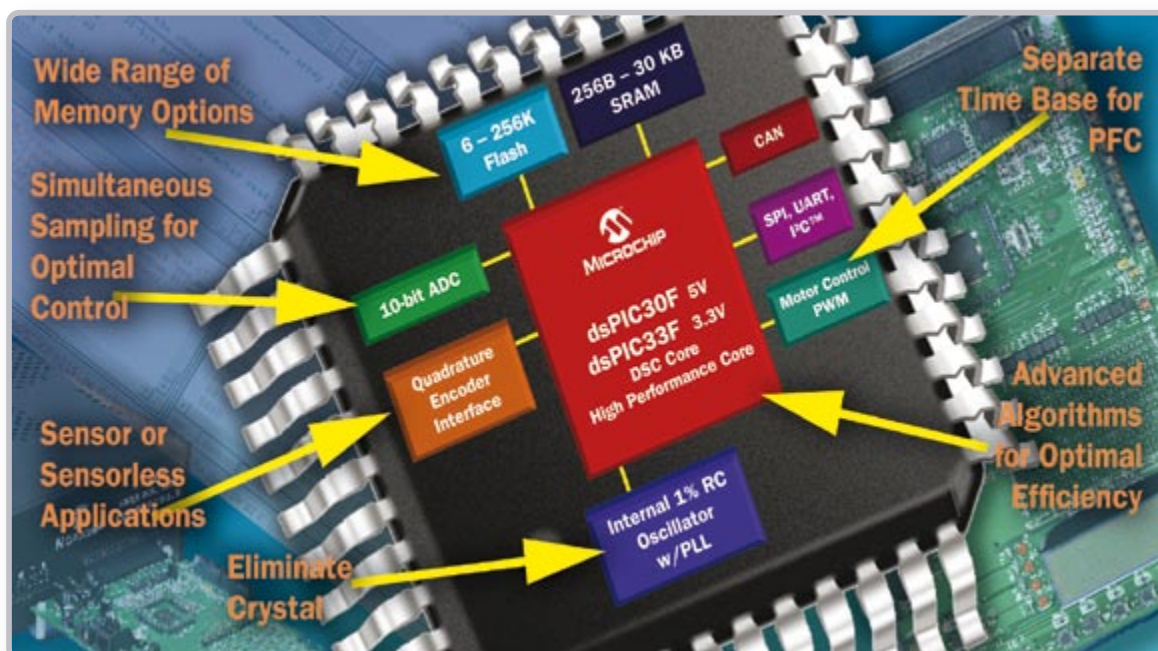

## Explore the new motor control solutions from Microchip

Are you considering moving to brushless motors, eliminating costly sensors or adding PFC? Let Microchip show you how to improve your efficiency, lower noise, reduce your form factor and explore cost reduction options.


Visit [www.microchip.com/DSCMOTOR](http://www.microchip.com/DSCMOTOR) and discover Microchip's comprehensive motor control solutions, featuring 16-bit Digital Signal Controllers, free software, technical training, development tool discounts and more!

Motor Control Solutions		
Looking for?	to...	Microchip has the solution!
Energy Savings	Add Power Factor Correction	PWM with 2 Time Bases
	Incorporate Field-Oriented Control	Free Software
Noise Reduction	Incorporate Sinusoidal Control	Free Software
Cost Reduction	Remove Expensive Sensors	Free Software, 4 S&H ADC
	Integrate PFC and Motor Controller	PWM with 2 Time Bases
	Integrate Controller on Motor	6x6 mm Small Packages
	Easily Migrate to Other DSCs in Portfolio	Optimized Feature Set
	Remove Crystal	1% Internal Oscillator
Better Torque Control	Incorporate Field Oriented Control	Free Software
	Better Loop Response	Multiple S&H ADC
Improved Reliability	Migrate from Brushed to Brushless Motors	Free Software
	Noise Profile Diagnostics	DSP Resource On-chip

Visit [www.microchip.com/DSCMotor](http://www.microchip.com/DSCMotor) today

**microchip**  
**DIRECT**  
[www.microchipdirect.com](http://www.microchipdirect.com)

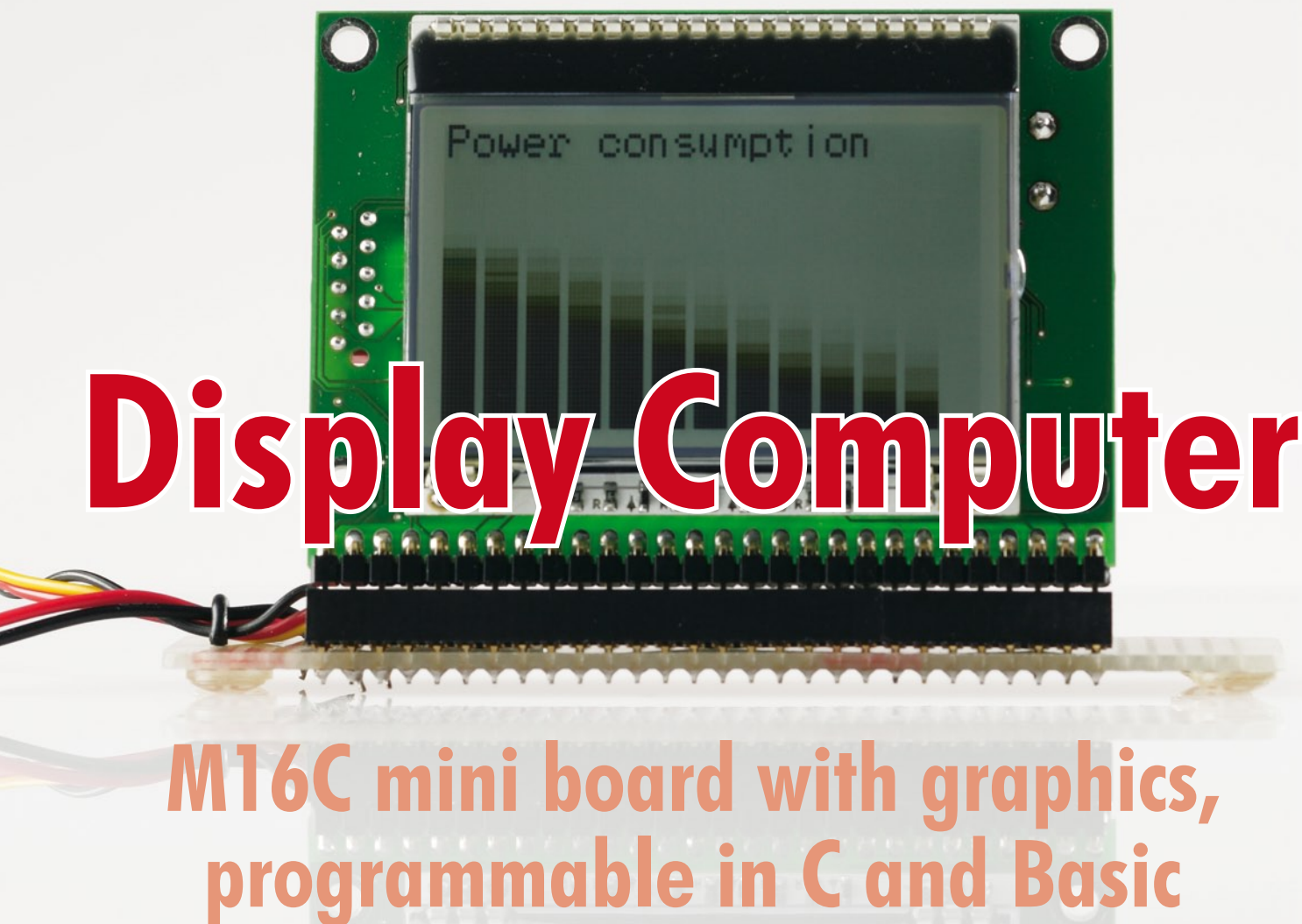 **MICROCHIP**  
[www.microchip.com](http://www.microchip.com)



**The prices of graphic displays are dropping, which makes them increasingly attractive for many applications. However, programming a graphic display is distinctly more difficult than programming a text display. Our mini microcontroller board features a new display-on-glass module and a high-performance Renesas M16C microcontroller. The board is available fully assembled, and the microcontroller is pre-loaded with a TinyBasic interpreter to simplify the development of graphics applications – even for novices.**

Dr Uwe Altenburg

There are countless applications for a stand-alone microcontroller board with a graphic display – everything from model railways or regulating the temperature in your home or conservatory to robotics.

However, driving the display and programming the associated microcontroller are tasks that exceed the skills of quite a few beginners. For this reason, in this article we present a ready-made board equipped with a display, a high-

performance 16-bit microcontroller, and even a Basic interpreter [1].

The powerful M16C – the big brother of the R8C, which is well known to many of our readers – can also be programmed in C just like any other microcontroller, so advanced users have plenty of opportunity to develop their own applications. In any case, you can take advantage of features such as 128 kB of flash memory, a 10-bit ADC, PWM signal generation and much

more, which make this mini board a truly versatile module.

### Display

Electronic Assembly has released a novel 'display on glass' module with the part number EA-DOGM128, which is driven via an SPI interface [2]. This interface can be clocked at up to 20 MHz, so data transmission is not a significant bottleneck. Data is only transmitted in one direction here (from the microcon-

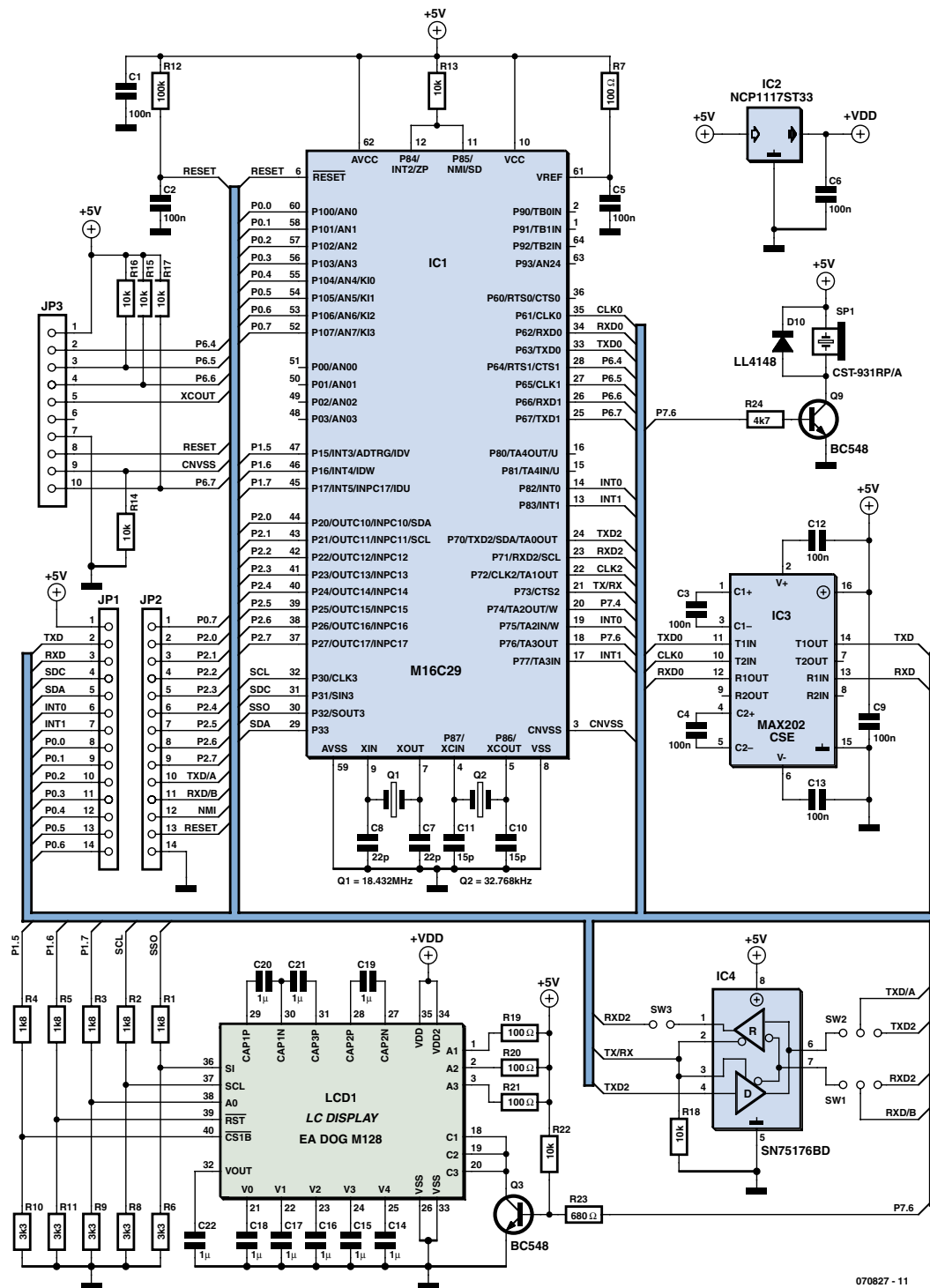


Figure 1. The circuitry around the M16C is relatively uncomplicated.

troller to the display), so only two signal lines are necessary. All in all, only five microcontroller I/O pins are needed – two for the data lines and three for the control lines (RESET, /CS and DATA). The display also features a very low profile of only 5.8 mm. The integrated LED backlight and automatic contrast adjustment ensure good legibility under all conditions, combined with low current consumption. Thanks to its pin-header contacts spaced at 2.54 mm, the module is easy to fit on a PCB. And

on top of all this, it is available in several colour combinations (e.g. from Reichelt Germany [3]).

### Microcontroller

Our search for a suitable microcontroller led us to choose the Renesas M16C28/29 [4]. This 16-bit machine has an impressive array of features. With 128 kB of flash program memory, 4 kB of flash data memory and 12 kB of RAM, it is generously endowed

with storage capacity. Although the display has its own graphic memory, the data for the display must still be assembled in the microcontroller. A monochrome display with a resolution of  $128 \times 64$  pixels requires an image memory of 1 kB in the microcontroller for this purpose ( $128 \times 64 \div 8$ ). The M16C28/29 has two DMA channels, so data can be copied directly from the image memory to the display without imposing any significant load on the microcontroller.

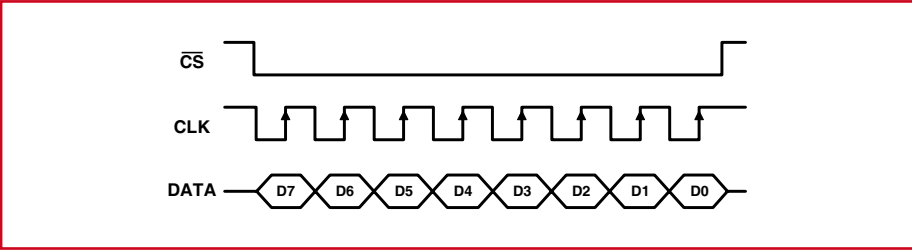


Figure 2. The data transferred via the SPI link is clocked into the display on the rising clock edge.

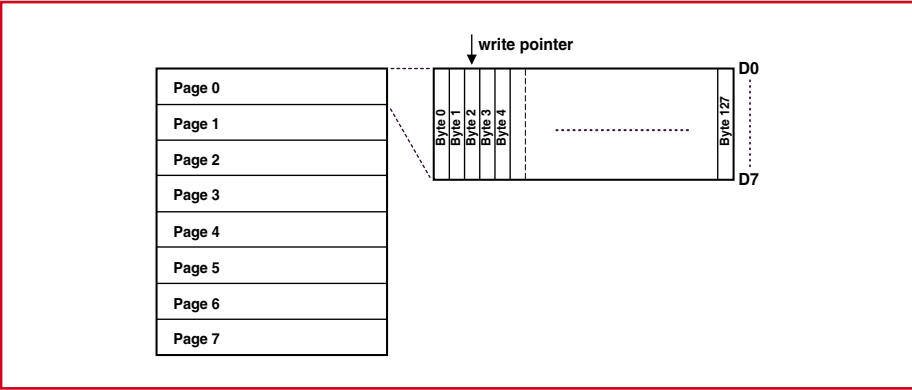


Figure 3. The image memory structure of the display.

Naturally, this little powerhouse in its 64-lead P-LQFP package also has a lot more to offer. Along with a 10-bit ADC with 16 input channels, it has several timer units, one of which can generate up to eight PWM signals with a resolution of 16 bits. There is an SPI interface for the display (of course), as well as two UARTs available for user-defined

functions. A third UART is used for the ISP/debug interface.

Without wishing to revive the old debate on the relative merits of RISC and CISC architectures, we can simply mention here that the instruction set of this CISC processor is extremely efficient. The instruction execution


time is only 50 ns with a 20 MHz clock. Several registers can be saved on the stack at the same time with a single assembly-language instruction when an interrupt routine is called. This results in extremely short interrupt response times. For information on other features, such as clock generation using a PLL, we suggest that you consult the datasheet.

Circuit

The schematic diagram of the circuit (Figure 1) is relatively uncomplicated. It is built around an M16C29 microcontroller (IC1) with a minimum of peripheral components. The Reset input manages nicely with a simple RC network (R12/C2). The primary clock signal is generated using an 18.432-MHz crystal (Q1). The microcontroller has a specified maximum clock frequency of 20 MHz. Given the capabilities of the internal dividers and the requirement to have the serial interfaces support all standard baud rates from 300 to 115,200 baud, the maximum clock frequency that can be used is 18.432 MHz. However, the SMD crystal used here is a standard component.

In the interest of maintaining a low profile, the display is soldered flush against the surface of the circuit board. All other components are mounted on the solder side. This means that SMD components must be used (with a few exceptions). This applies to the second crystal as well (Q2), which operates at 32.768 MHz to provide a secondary clock signal. There are essentially two situations in which the secondary clock can play a role. The first is when a timer is programmed to act as a real-time clock, for instance in order to trigger a low-priority interrupt once per second. Alternatively, the secondary clock can be used in place of the primary clock in order to operate the microcontroller with the lowest possible power consumption.

A 10-way MicroMatch connector is used for programming and debugging the microcontroller. The signals available on this connector correspond to the signals needed by the Renesas E8 emulator for this type of microcontroller. The Renesas emulator is available from Reichelt [3], among other sources, but it can also be obtained from Rutronik or Glyn along with an evaluation board. The emulator is accompanied by a very good C compiler, which

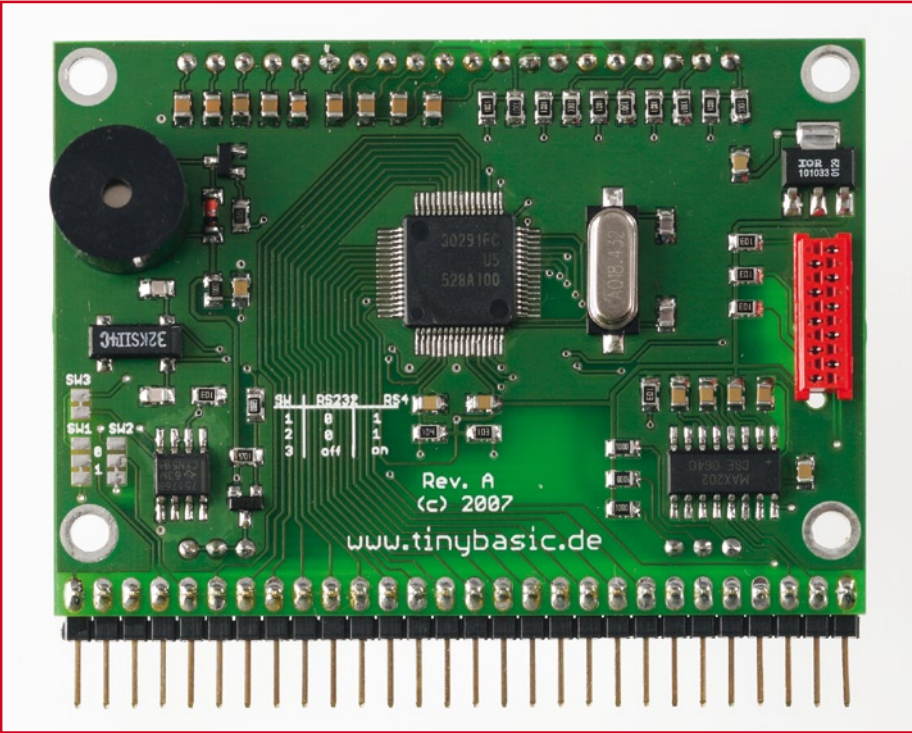

can handle a code size of up to 64 kB in the free version.

But that's not all: for the C fans among our readers, the next issue of *Elektor* will have an article describing a small circuit that lets you program the microcontroller without using purchased hardware. All you actually need to flash into the M16C is a serial interface and a few freely downloadable tools (for example, from Renesas), and many readers are probably already familiar with them from the R8C 'Tom Thumb' project.

## Display power

The display (LCD1) requires only a single supply voltage of 3.3 V. The microcontroller can be operated at 3.3 V or 5 V. As the display module is intended to be used in other circuits, we decided on a supply voltage of 5 V.

A supplementary low-drop 3.3-V voltage regulator (IC2) generates the supply voltage for the display. Simple voltage dividers (R1–R10) are used to adjust the levels of the signals from the microcontroller to the levels required by the display. Here the fact that the display is driven by only five lines, and only in one direction, is a distinct advantage. It keeps the amount of hardware necessary for level adjustment within reasonable limits.

The display microcontroller (an ST7565) needs higher internal voltages to drive the LCD segments. For this purpose, a set of external capacitors (C14–C21) must be connected to its integrated charge pump circuit.

The LEDs for the display backlight are driven via series resistors R19, R20 and R21 and a simple transistor stage (Q3). The display illumination is always on unless it is programmed otherwise. In the simplest case, the illumination can be switched on and off under software control. However, the I/O pin used for this purpose (P7.4) can also be programmed as a PWM output to provide a conveniently adjustable brightness level under software control.

One of the two free serial interfaces is connected to one of the 14-way headers via an RS232 level converter (IC3, a MAX202). This interface can be used for connection to a PC or a modem. The TinyBasic interpreter, which is described later on in this article, also uses this interface for downloading program code. (Note: if you're not afraid of a bit of soldering work, you

### Listing 1. Display initialisation

(Data types used: BYTE = 8 bits unsigned, WORD = 16 bits unsigned, INT8 = 8 bits with sign, INT = 16 bits with sign, LONG = 32 bits with sign)

```
// --- Init sequence ---
const BYTE InitList[] =
{
    0x40,                // start line
    0xA1,                // normal layout
    0xC0,                // normal COM0..63
    0xA6,                // normal display
    0xA2,                // set bias 1/9
    0x2F,                // booster regulator on
    0xF8, 0x00,          // booster to 4x
    0x27, 0x81, 0x16,    // set contrast
    0xAC, 0x00,          // no indicator
    0xAF,                // display on
};

// --- Init display ---
void InitDisplay()
{
    BYTE nCmd;

    LCD_CS = 1;          // no chip select
    LCD_RES = 0;
    Sleep(50);           // 50ms reset delay
    LCD_RES = 1;
    Sleep(50);           // 50ms power-up delay

    LCD_MODE = 0;        // command mode
    for (nCmd = 0; nCmd < sizeof(InitList); nCmd++)
    {
        SPISend(InitList[nCmd]); // send cmd
        Sleep(1);              // wait 1ms
    }
}
```

can tap off another V24 signal from the T2OUT pin of the MAX202 – see the schematic diagram.)

The second serial interface can be connected to the header either directly or indirectly via an RS485 level converter by suitable configuration of jumpers SW1, SW2 and SW3. This means that

the module can also be connected to a network and share a bus with other microcontrollers.

## Drive logic

Now let's turn our attention to the graphic display. The SPI interface is

### Listing 2. Page copying

```
// --- Copy a single page ---
void CopyPage(BYTE nPage)
{
    BYTE nPos;

    LCD_MODE = 0;        // command mode
    SPISend(0x40);       // memory base
    SPISend(0xB0 + nPage); // select page
    SPISend(0x00);       // col low
    SPISend(0x10);       // col high

    LCD_MODE = 1;        // data mode
    for (nPos = 0; nPos < 128; nPos++) // copy page
        SPISend(Pixels[nPage][nPos]); // send byte


    LCD_MODE = 0;        // command mode
    SPISend(0xE3);       // send nop
}
```

operated in Mode 0, which means that the data is clocked into the display on the rising edge of the clock. The timing diagram for this is shown in **Figure 2**. The individual data bytes are transferred to the display sequentially using this clocking scheme. In the code examples, the `SPISend()` routine is called for this purpose (see **Listing 1**). The display must be initialised before any image data is sent to it. The routine that does this is called `InitDisplay()`. This routine sends several commands after the Reset pulse and a short startup time delay. The A0 line of the display must be held low while the commands are being transferred. Consult the data sheet for the display microcontroller (ST7565) for the specific functions of the individual commands. The sequence of commands shown in Listing 1 is designed to initialise the display to an operational state. The next question is how to send image data to the display. To answer this question, you first have to understand how the image memory of the display is organised. The EA-DOGM128 is divided into eight sections called 'pages'. Each page consists of a  $128 \times 8$  array of pixels. This means that each page needs 128 bytes. The top left pixel corresponds to bit 0 of the first byte of the top page.

The display has a write pointer in addition to the image memory (see **Figure 3**). The write pointer can be set to a specific position in a page by sending commands to the display. All data bytes sent after this are written to the image memory starting from this position. The write pointer is incremented automatically during this process. Naturally, each data byte modifies eight pixels at the same time. Modifying a single pixel is thus not possible, and it would anyhow not be especially efficient. Instead, a copy of the image memory is maintained in the microcontroller, and it is also organised in pages. This can be achieved by declaring a suitable variable: `BYTE Pixels[8][128]`. All drawing operations are performed directly on this internal image memory. This simplifies the graphics routines, and it is significantly faster. Of course, the internal image memory must be copied periodically to the display. In the simplest case, this can be done by an interrupt routine that copies only one page at a time to the display. The `CopyPage()` routine first sends several commands to the display to set the write pointer to the start of

the page to be copied. After this, the page data is sent to the display, and the process is terminated by a NOP


command (see **Listing 2**). At a data rate of 1 Mbit/s, the copy process takes approximately 1.1 ms.

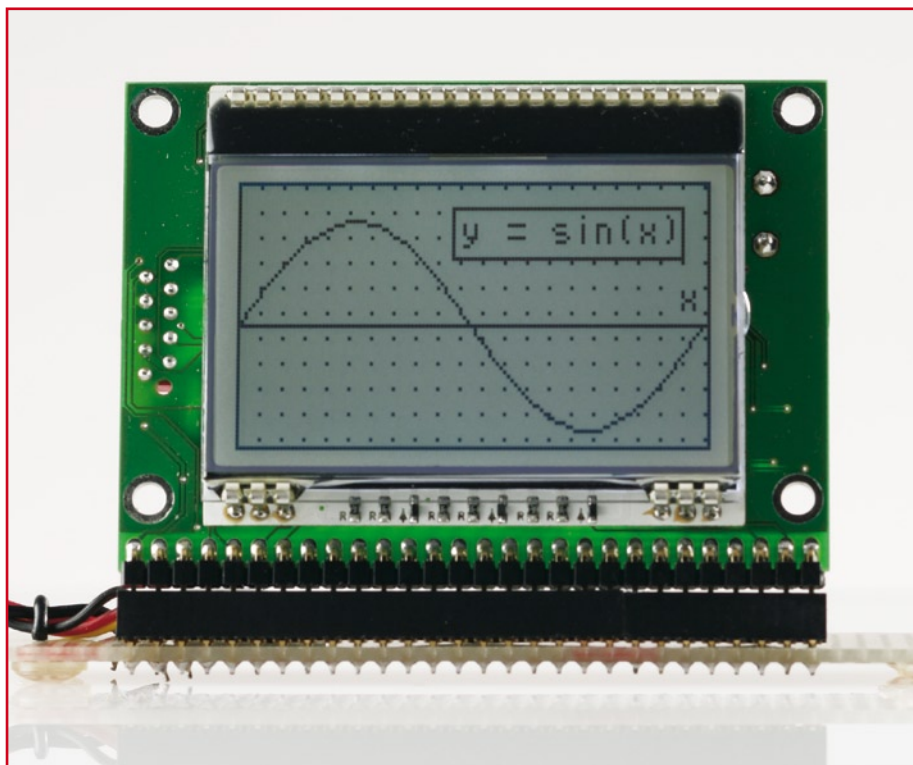

**Listing 3. Pixel setting**

```
// --- Set a single pixel ---
void SetPixel(BYTE x,BYTE y)
{
    if (x < 128 && y < 64)           // clip
    {
        BYTE nPage = y / 8;          // calc page
        BYTE nMask = 1 << y % 8;     // calc mask

        Pixels[nPage][x] |= nMask;   // set pixel
    }
}
```

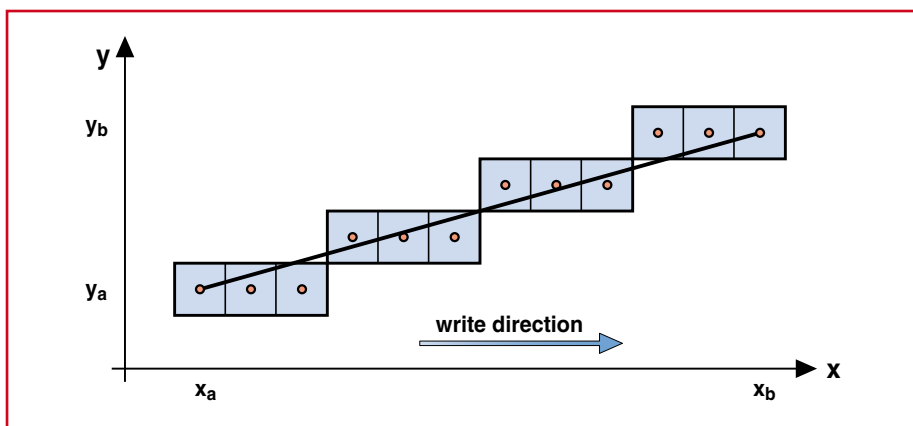

**Figure 4.** The Bresenham algorithm constructs lines as sequences of adjacent pixels. Here three steps in a straight line are followed by a diagonal step (see Listing 4).

If the interrupt routine is called every 10 ms, it takes around 80 ms to transfer a full image. Naturally, it is only neces-

sary to copy the pages where changes have actually occurred. For this purpose, a 'Dirty' flag is maintained for

each page. It is set by the graphics routines. The alternative 'high-end' solution is to use a DMA channel for the page data.

**Listing 4. Line from point A(ax,ay) to point B(bx,by)**

```
// --- Draw a line ---
void DrawLine(BYTE ax,BYTE ay,BYTE bx,BYTE by)
{
    INT x = (INT)ax;           // start
    INT y = (INT)ay;
    INT dx = (INT)bx - ax;     // distance
    INT dy = (INT)by - ay;
    INT8 sx = 1;               // step width
    INT8 sy = 1;

    if (dx < 0)                 // x orientation
    {
        sx = -1;
        dx = -dx;
    }

    if (dy < 0)                 // y orientation
    {
        sy = -1;
        dy = -dy;
    }

    if (dy <= dx)               // select direction
    {
        INT c = 2 * dx;
        INT m = 2 * dy;
        INT d = 0;

        while (x != bx)        // draw in x direction
        {
            SetPixel(x,y);     // set pixel

            x += sx;            // step x
            d += m;

            if (d > dx)
            {
                y += sy;
                d -= c;
            }
        }
    }
    else
    {
        INT c = 2 * dy;
        INT m = 2 * dx;
        INT d = 0;

        while (y != by)        // draw in y direction
        {
            SetPixel(x,y);     // set pixel

            y += sy;            // step y
            d += m;

            if (d > dy)
            {
                x += sx;
                d -= c;
            }
        }
    }
}
```

## Graphics programming

Now that you know how to connect and program the EA-DOGM128, you might think that you're all set – but in fact you're just getting started. Here we want to talk about drawing line and circles, which is not as simple as it seems.

Of course, the first thing you need is a routine for setting the values of individual pixels, which goes by the name SetPixel(x,y) – see **Listing 3**. As the image memory is virtually located in the RAM of the microcontroller, the routine only has to set the right bit. One of the most important tasks in this connection is range checking, as otherwise it would easily be possible to set bits that have nothing at all to do with the image.

When you hear the term 'straight line', you may well recall the standard algebraic formula for a straight line:  $y = ax + b$ . It can be used to calculate the y value of a straight line for all possible values of x. This is a good initial approach, but it requires very precise calculation of the factors, in particular the slope  $a$  ( $\Delta y/\Delta x$ ), and even with a precise calculation the formula for a straight line results in a broken line if the slope is steep, due to the quantisation of the x values.

Avoiding the need for floating-point arithmetic another is another factor that makes revisiting the 'stone age' of computer technology worthwhile. At that time, clever approaches were often devised to compensate for low processing power – something that seems to neglected more and more these days. In the 1960s, Jack Bresenham was working at IBM on graphic output for plotters, and around 1962 he developed an algorithm that bears his name: the Bresenham algorithm [5a][5b] – see **Figure 4** and **Listing 4**. Even now, 40 years later, this algorithm is just as important as ever.

## Lines and circles

The Bresenham algorithm first considers only straight lines with slope  $0 < a < 1$  (first octant). The line is drawn by processing the x coordinates incrementally starting from the initial point and deciding for each point

whether the y coordinate should be increased. The y coordinate is increased if the error relative to the straight line is greater than half a pixel.

The error is calculated for each step in a manner that only requires an integer comparison. Finally, the algorithm can be applied to the other seven octants by mirroring or by reversing the direction of drawing. This yields a very fast and exact line-drawing algorithm. The Bresenham algorithm can also be used to draw circles and ellipses, which avoids the need to calculate sine and cosine values. A suitable listing can be downloaded from the Elektor website [6].

## TinyBasic interpreter

As mentioned above, the microcontroller used here has enormous potential, including a relatively large memory capacity, analogue inputs, and a variety of interfaces. It would be a sin to use this potential for nothing more than driving the display. To make it even easier for novice programmers to create their own graphic applications, the author has developed a Basic interpreter.

Programs can be generated using a convenient PC-based text editor that highlights keywords in colour (Figure 5). The program code can then be downloaded directly to the flash memory of the microcontroller, where it will be launched immediately when the module is switched on.

An overview of the language and the available commands is available online [1]. Naturally, it supports conditional branching and loop commands, as well as mathematical functions such as SIN(), COS(), EXP() and LOG(). There are also commands for graphic output (PLOT, MOVE, DRAW, COLOR, FRAME, CIRCLE, PICTURE, BARGRAPH) and for accessing the hardware (POKE, PAUSE, SOUND, SETCOM, SETPWM, SETPORT, SETCLOCK, SETDRIVE, SETKEYPAD, SETDISPLAY, SETNETWORK, SETCOUNTER, SEND, RECV, I2CIN, I2COUT, and SPISHIFT).

As an example, up to eight R/C servos could be connected to the module, which is enough for a small walking robot with facial expressions and gestures.

## A sample application...

As a sample application to get you started, here we describe how to use

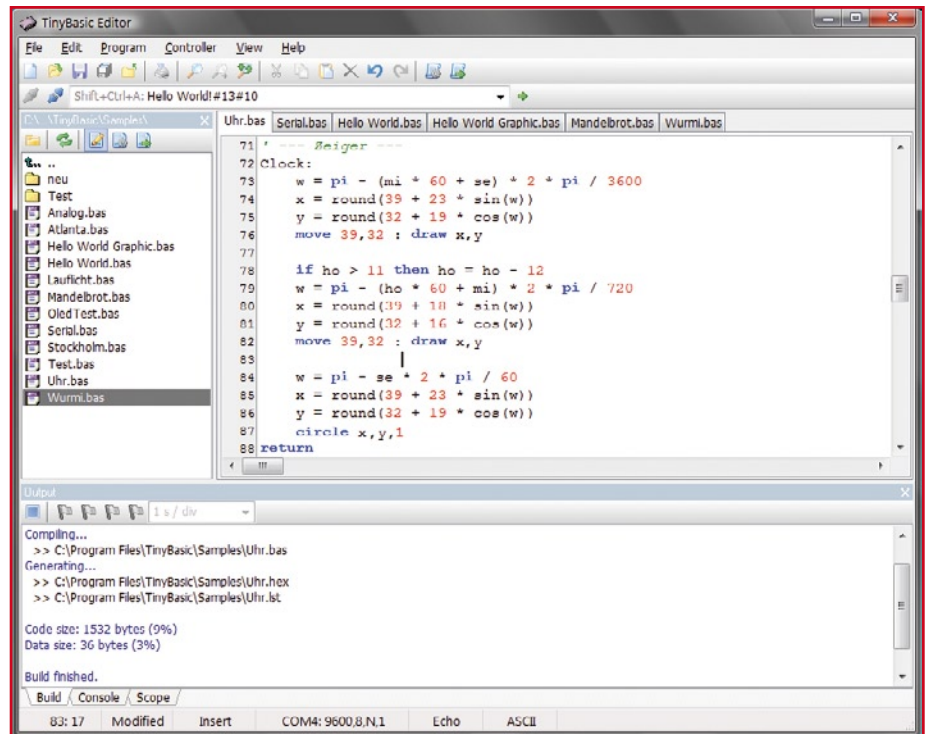


Figure 5. The PC-based text editor provides a convenient development environment for Basic programs.

### Listing 5. Analogue clock in TinyBasic (excerpt)

```
' --- Definitions ---
#define BTN1_PRESSED (port0.5 = 0)           ' Button 1
#define BTN2_PRESSED (port0.6 = 0)           ' Button 2
#define BTN3_PRESSED (port0.7 = 0)           ' Button 3
#define BACKLIGHT    port7.4                 ' LCD backlight
#define T20SEC       20000                   ' Backlight time

' --- Hardware ---
setdisplay LCD_DOGM128x64                    ' Display type
setclock REAL_CLOCK                          ' Real-time clock
setport 7,$10                                ' Backlight output
setport 0,0,$E0                              ' PB switch pull-ups

' --- Variables ---
float w,t0,t1
byte ho,mi,se,da,mo,ye,x,y
byte Icon[18]

' --- Init ---
BACKLIGHT = 1                                ' Backlight on
Timer0 = T20SEC                              ' Start timer

gosub Scale                                  ' Draw clock face


' --- Main loop ---
do
    if BTN1_PRESSED or BTN2_PRESSED or BTN3_PRESSED then
        Timer0 = T20SEC                      ' Start timer
        BACKLIGHT = 1                        ' Backlight on
    elseif Timer0 = 0 then
        BACKLIGHT = 0                        ' Backlight off
    endif

    if Time.Second <> se then
        gosub UpdateTime                    ' New second
        gosub UpdateTemp                    ' Update time
        Display temperature                  ' Display temperature
    endif
endif
```

the module to make an analogue clock with an integrated display of the indoor and outdoor temperature. This requires a small amount of additional circuitry for measuring the temperature in a suitable manner.

A temperature-dependent current source, such as the AD592, can be used as the temperature sensor. The advantage of this sensor is that it has a linear characteristic. You only have to connect a 10-k $\Omega$  resistor in series with the sensor in order to convert the current into a temperature-dependent voltage with a scale factor of 10 mV/K (see **Figure 6**). Unfortunately, this sensor is relatively expensive. As an alternative, you could construct a similar circuit using the more economical LM344 sensor.

The AD592 supplies a current of 273  $\mu$ A at a temperature of 0 °C. This results in a voltage of 2.73 V across the resistor. The analogue inputs (in this case P0.0

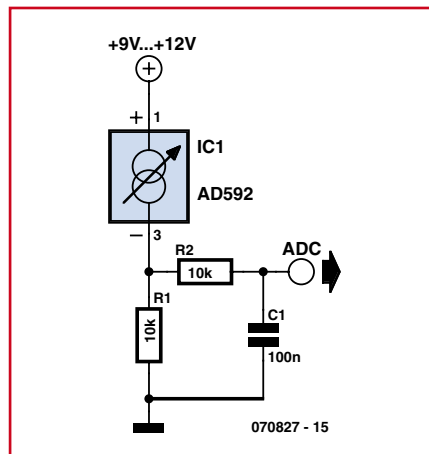

**Figure 6.** This additional circuitry can be used for temperature measurement.

and P0.1) have a resolution of 10 bits, which means they supply values in the range of 0 to 1023. The currently measured temperature can be calculated using the simple formula 'temp = (ana-

logue\_value - 559)  $\div$  2.04'.

Naturally, the previously described routines for lines and circles can be used for the analogue clock display. The sin() and cos() functions must be used to calculate the positions of the hands. TinyBasic provides these trigonometric functions (and others) – see **Listing 5**. As this is supposed to be an analogue clock, the hands should of course move smoothly. For this reason, the positions of the hour and minute hands are interpolated. This gives the impression of continuous motion. The second hand is represented by a small circle, which is more a question of design than necessity.

### ...and your own applications

If you buy the display board from the Elektor Shop, you receive a fully assembled and tested module. The TinyBasic interpreter is already installed in the microcontroller. The Basic development environment can be downloaded from the Elektor website [6] free of charge, along with additional examples and listings.

For beginners, we have also put together a step-by-step guide that describes how to install the necessary software on the PC and how to download your own application.

(070827-1)

### Web Links

- [1] [www.tinybasic.de/](http://www.tinybasic.de/)
- [2] [www.electronic-assembly.de/deu/dog/dog.htm](http://www.electronic-assembly.de/deu/dog/dog.htm)
- [3] [www.reichelt.de/](http://www.reichelt.de/) (in German)
- [4] [www.m16c.de/](http://www.m16c.de/)
- [5a] [http://en.wikipedia.org/wiki/Bresenham\\_algorithm](http://en.wikipedia.org/wiki/Bresenham_algorithm)
- [5b] <http://www.lehre.inf.uos.de/~cg/2002/skript/node30.html> (in German)
- [6] [www.elektor.com](http://www.elektor.com)

### Component availability notice

Ready assembled and tested board including display and pre-programmed microcontroller (bootloader and Basic Interpreter) available from the Elektor Shop, order code 070827-91.

Bare PCB, ref. 070827-1 available from [www.thepcshop.com](http://www.thepcshop.com).

```

loop

' --- Clock face ---
Scale:
    frame 0,0,127,63
    circle 39,32,29,25

    for w = 0 to 2 * pi step 2 * pi / 12
        x = round(39 + 25 * sin(w))
        y = round(32 - 22 * cos(w))
        plot x,y
    next

    for w = 0 to 2 * pi step 2 * pi / 4
        x = round(39 + 26 * sin(w))
        y = round(32 - 23 * cos(w))
        plot x,y
    next

return

' --- Hands ---
Clock:
    ' Hour hand...
    w = pi - (mi * 60 + se) * 2 * pi / 3600
    x = round(39 + 23 * sin(w))
    y = round(32 + 19 * cos(w))
    move 39,32 : draw x,y

    ' Minute hand...
    if ho > 11 then ho = ho - 12
    w = pi - (ho * 60 + mi) * 2 * pi / 720
    x = round(39 + 18 * sin(w))
    y = round(32 + 16 * cos(w))
    move 39,32 : draw x,y

    ' Second hand...
    w = pi - se * 2 * pi / 60
    x = round(39 + 23 * sin(w))
    y = round(32 + 19 * cos(w))
    circle x,y,1

return

```

# assembly, test and software

## DigiButler (2)

Richard Sumka & Eric Gregory (Freescale Semiconductor Inc.),  
Luc Lemmens & Jan Buiting (Elektor)

Continuing on from the April 2008 issue, in this the second and final part of the article we go about assembling the kit and connecting up the hardware and software to get DigiButler active on the web and in control of an electrical appliance in your home or office.

### Assembly and test

All components used in this project are contained in a kit that's available through the Elektor Shop as # **071102-71 (Figure 1)**. The PCB contained in the kit

comes with all but six SMD components ready-soldered and the Coldfire micro ready programmed with the DigiButler firmware. This makes building the project a matter of soldering three dozen or so through-hole components and six relatively large SMD parts including the Ethernet transformer T1.

The component mounting plan of the DigiButler board is shown at true size in **Figure 2**. The associated parts list clearly indicates which parts are prestuffed on the board you get, and which ones have to be soldered.

Assembly of the board should be straightforward using the parts from the kit. Solder the SMD components first and follow with the through-hole components. The SMD parts you have to solder yourself are:

- capacitors C20, C21 (both 4.7 $\mu$ F solid) located at the underside of the board;
- capacitor C15 (4 $\mu$ F7 solid) located


between J11 and J12 located at the top side of the board;

- transformer T1 (H1102NL) located at the top side of the board. Triangle marker on the PCB overlay to register with the white dot printed on the device;

- quartz crystal Y1 (25 MHz) located at the top side of the board;

- voltage regulator U2 (LD29080DT33R) located at the top side of the board.

If you use a fine-tipped solder iron and the usual care and precision then mounting these parts should not cause problems. Give the mounting of T1 a thorough visual inspection to make sure no adjacent pins are short-

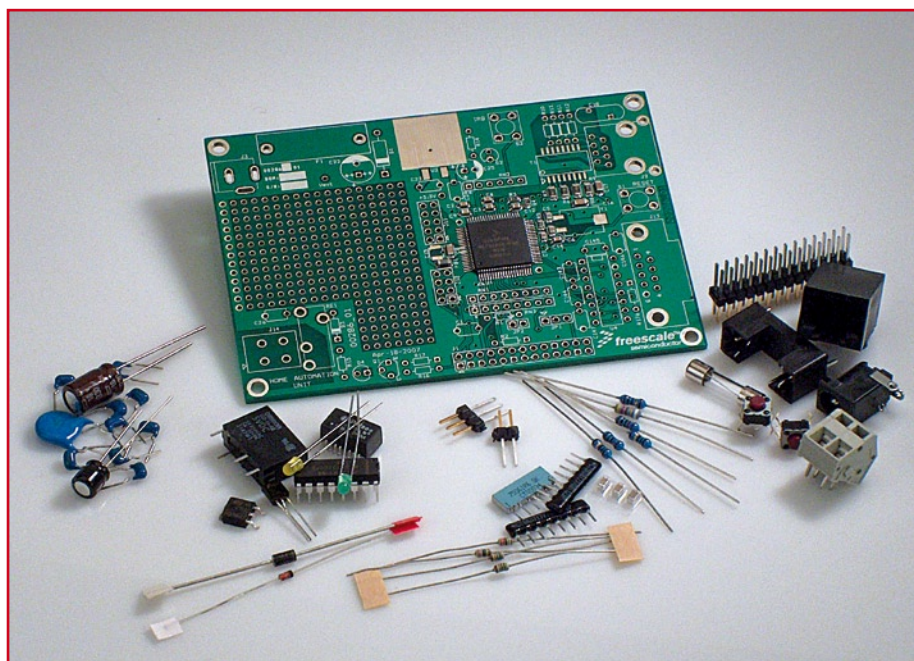

**Figure 1.** The DigiButler kit ready to be assembled, complete with the SMD-prestuffed PCB. The project is an hour's worth of careful soldering. (packaging not shown; actual parts supplied may differ from photograph)

# installation

circuited by solder blobs.

Now, on with the soldering of the leaded parts from the kit. Voltage regulator U2 has a thermal pad on the underside of the device, the tip of which should be soldered to the nearby copper square on the PCB. The centre pin is not used — the metal pad establishes the ground connection.

The connectors, fuseholder and relay should be assembled last. Pay special attention to J14 and RE1 which should be placed on the board together before being soldered.

The 'pin-1' marker printed on resistor networks RN1, RN2 and RN3 should register with the respective little circles on the PCB overlay. Watch the polarity of radial electrolytics C22 and C25, LEDs D2 and D4, diodes D1 and D3, and finally U4, the MAX3232ECPE.

When placing the assembled PCB directly onto a hard surface, take care to avoid damage to the passive surface mount components at the underside of the PCB. Four 5 mm high PCB pillars secured with M3 nuts will take care of the problem.

The base of RS232 socket J13 may be secured to the board using two M3 screws and bolts. RJ45 socket J2 has two plastic studs that snap secure into the 3 mm holes on the board.

Do not install jumper JP2 (BDM\_ENable) and set JP1 (BDM\_SEL0) the right-hand position (2-3).

Check the board carefully before applying power. Ensure that all solder joints are good and that there are no shorts. Connect power to the board using either an unregulated or a regulated DC supply with an output voltage of 5-8 V. LED D2 should light up.

## I can do it cheaper

Be our guest, although you'll find the price of the DigiButler kit hard to beat. Especially for those among you who insist on sourcing their components locally and doing the microcontroller programming all by themselves we also supply the same SMD-prestuffed PCB with an **empty microcontroller** as Elektor Shop # 071102-1. 'Empty' means no firmware in the MCF52231, so you will also need the TBLCF hardware and software, or a professional equivalent from Freescale or a third party.


**Exercise extreme caution if using this board to switch power to an AC mains powered load as dangerous voltages will exist on the pins of J14 and RE1. The maximum current switched by the relay contacts is 2 A. If in doubt consult an experienced professional.**

## TBLCF hardware

For completeness' sake we recall that the PCB design and construction notes for Daniel Malik's Turbo BDM Light Coldfire Interface (TBLCF) may be found at [7] referenced in Part 1 of this article (April 2008). PCBs for the TBLCF are supplied through the Elektor Shop as # 071102-2. The bare board is shown in **Figure 3**. You will need TBLCF if you want to make changes to the DigiBut-

ler firmware, or use the hardware as a Coldfire development system.

Remember the 'free samples' trick we showed in last year's 3-Axis Accelerometer article? Use the Freescale website again to get a free MC908JB16JDWE chip for the TBLCF programmer. For the project name, enter: 'Elektor DigiButler'. Caution: the supply of free samples is strictly at the discretion of Freescale Semiconductors Inc. Look in Elektor's forum topics on

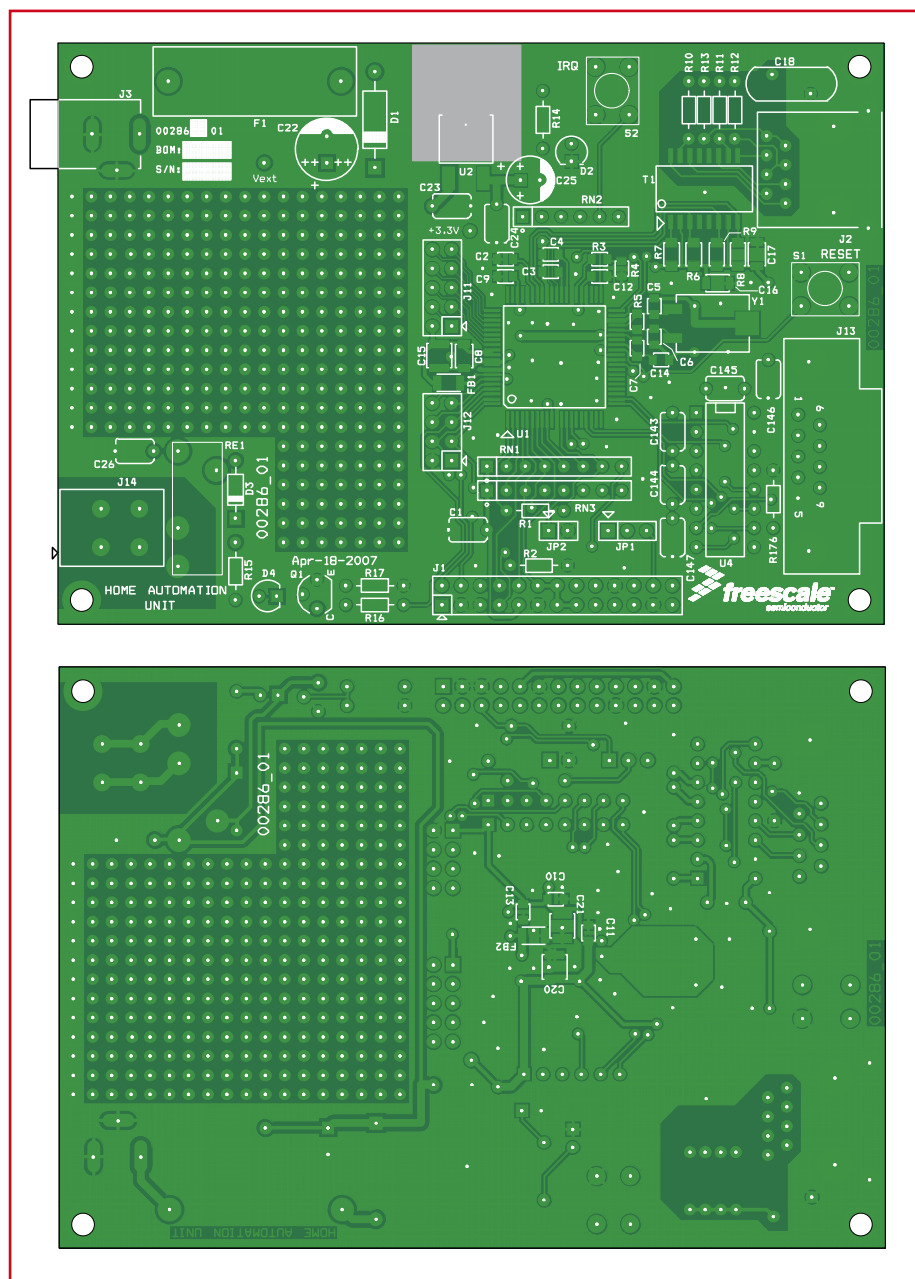

**Figure 2.** DigiButler board layout. The board comes with all but six SMD parts premounted

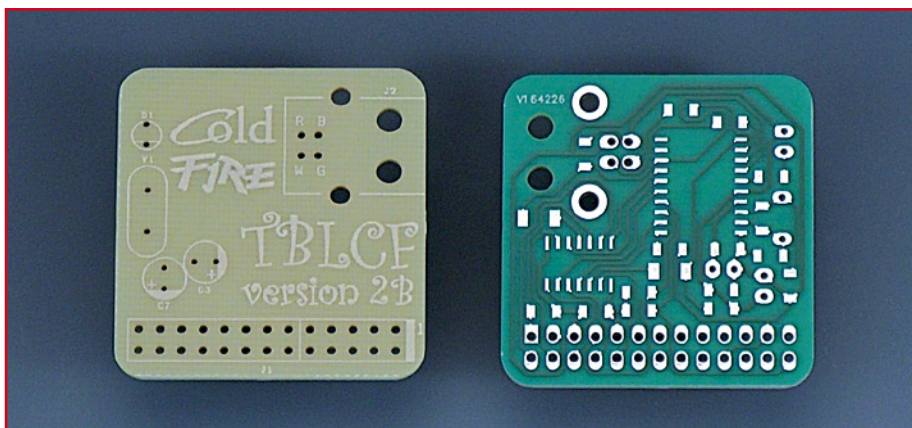


Figure 3. TBLCF board, unstuffed.

the SpYder and Accelerometer projects how others did it.

TBLCF is programmed from the ground up as described in its extensive manual.

## Compilation and programming

Code (re)compilation and device (re)programming is only necessary if you

1. have an unprogrammed board # 071102-1 and/or

2. want to make changes to the existing firmware.

The project software including the full C source code is available from the Elektor website as a free download — you'll find it as archive file # **071102-11.zip**. Unpack it into an appropriate directory.

Compilation and (re)flashing the MCF52231 requires **CodeWarrior Development Studio for Coldfire Architectures, v. 6.3**. CodeWarrior is an integrated development environment which includes a project manager, editor, compiler and debugger. Version 6.3 is a free download. At ref. [1] it's marked as "Updates and Patches" but Elektor has 'inside information' that it's actually a full install version! The download is about 140 MB. Type 'Elektor DigiButler' when you are asked for the project name.

At the time of writing, the 'Special Edition: CodeWarrior for ColdFire Architectures' (v. 7.0) revealed some issues with the MCF52231 micro we're using. An update/patch or service pack for 7.0 has been announced by Freescale. It should be well worth the wait considering that the suite can compile up to 128 k of code in 'C' and unlimited assembly code. The Special Edition can be downloaded at [1] too — sit back & relax for 270 MB or so.

Programming and debugging also needs a background debug pod such as TBLCF or the USB-ML-CFE [2] from P&E Micro. A detailed procedure to do the firmware flashing is given in the '(re-)Flashing your board' inset.

## Network connection

The most important part of the project is connecting DigiButler to a network, and for this we need an IP address for the board. An IP address is similar to a telephone number and allows the board to be identified by other devices on the network. By default, the board software is configured to request an IP address from a DHCP server, although it can be reconfigured to have a fixed, or static, IP address. Most home cable or DSL modem routers have built in DHCP server functionality and are able to provide local IP addresses. To link to your network, connect the DigiButler board to your router using a standard RJ45 cable. Next, connect the

## COMPONENTS LIST

### 1. Components pre-fitted on board

#### Resistors

R3 = 12k $\Omega$ , SMD 0805  
R4 = 390 $\Omega$ , SMD 0805  
R5 = 10M $\Omega$ , SMD 0805  
R6,R7,R8,R9 = 51 $\Omega$ , SMD 1206

#### Capacitors

C2,C3,C4,C12,C13,C14 = 220nF ceramic, SMD 0805  
C9,C10,C11 = 100nF ceramic, SMD 0805  
C17 = 220nF ceramic, SMD 1206  
C5,C6 = 22pF ceramic, SMD 0805  
C7 = 1nF ceramic, SMD 0805  
C8 = 100nF ceramic, SMD 1206  
C16 = 10nF ceramic, SMD 1206

#### Inductors

FB1,FB2 = BLM31PG601SN1 ferrite bead, SMD 1206

#### Semiconductors

U1 = MCF52231CAF6 (Freescale)\*

### 2. Components to fit on board

#### Resistors

R1 = 22 $\Omega$  SFR16S  
R2,R17,R176 = 10k $\Omega$  SFR16s  
R15 = 470 $\Omega$   
R10-R13 = 75 $\Omega$  SFR16S  
R14 = 270 $\Omega$   
R16 = 1k $\Omega$  SFR16S  
RN1 = 7-way 4k $\Omega$  SIL  
RN2 = 5-way 10k $\Omega$  SIL  
RN3 = 7-way 10k $\Omega$  SIL

#### Capacitors

C1,C23,C24, C26,C143,C144-C147 = 100nF ceramic, lead pitch 5mm  
C15,C20,C21 = 4 $\mu$ F7, solid, SMD1206

C18 = 2nF2 1000V ceramic (TDK)  
C22 = 330 $\mu$ F 16V, electrolytic, radial  
C25 = 220 $\mu$ F 6.3V, electrolytic, radial

#### Semiconductors

D1 = 1N4004  
D2 = LED, 3mm, green  
D3 = 1N4148  
D4 = LED, yellow, 3mm  
Q1 = BC546B  
U2 = LD29080DT33R (STMicro)  
U4 = MAX3232ECPE

#### Miscellaneous

F1 = 0.5A slow, 5x20mm  
J1 = 26-way double-row pinheader  
J2 = RJ45 socket, PCB mount  
J3 = DC adaptor socket, PCB mount  
J11 = 10-way double-row pinheader  
J12 = 8-way double-row pinheader  
J13 = 9-way sub-D socket (female), angled pins, PCB mount  
J14 = 2-way terminal block, 5mm lead pitch  
JP1 = 3-way pinheader with jumper  
JP2 = 2-way pinheader with jumper  
RE1 = G6D-1A-ASL-DC5 (Omron)  
S1,S2 = pushbutton, EVQ-PAE05R (Panasonic)  
T1 = H1102 Ethernet transformer (Pulse)  
Y1 = 25MHz quartz crystal  
Fuse holder, PCB mount  
Kit of parts, Elektor Shop # **071102-71**, contains all parts and SMD-prestuffed circuit board (see text)  
PCB, Elektor Shop # **071102**, available separately. Marking: 00286\_01 "HOME AUTOMATION UNIT"  
PCB for TBLCF, Elektor Shop # **071102-2\*\***

\* ready-programmed on PCB in kit 071102-71; blank on PCB 071102-1.

\*\* optional, see text.

Start up a terminal session such as Minicom for Linux or HyperTerminal or TeraTerm for Microsoft Windows. The communication settings are

- 115,200 databits/second
- 8 data bits
- no parity
- 1 stop bit
- no flow control

Power up the board and push switch S1 to reset it. This will cause the application software to communicate with the DHCP server in the router to acquire an IP address for the board. On the PC screen, the terminal window will display the board IP address, like **F 4**, indicating connection to the network and ability to be accessed remotely. Note that it takes a few seconds for the board to obtain an IP and include it in the message sent to the terminal. Got the complete message? Congratulations, your hardware is working. If you just want to connect the board direct to a PC, you will need a **crossover RJ45 cable** and a **fixed IP address** in the application software.

## Ethernet setup and access security


We have assumed so far that DigiButler will be connected to the Internet via an Ethernet router. A router allows many computers on a local network to share the same internet connection. It also prevents unwanted Internet visitors accessing those same computers unless authorised. Preventing access to your private DigiButler could be a problem if it were not for a router feature called Port Redirection or Port Forwarding, see **Figure 5** for a typical example. Port Forwarding lets through Internet traffic destined for a given IP address and port and then sends it to a computer or other device on your local network. Let's say the local IP address of the server is 192.168.0.2 and the address of your router – given to you by your Internet Service Provider (ISP) — is 86.131.222.120. Login to the administration pages of the router and change the router settings to forward any incoming traffic destined for port 80 to DigiButler at address 192.168.0.2. Anyone who now enters <http://86.131.222.120>

Be aware that you probably won't be able to see the server if you try this from a PC on the same local network. Instead you will have to use `http://192.168.0.2`.

Another important point to note is that each port can only be forwarded once. It's not possible to have port 80 forwarded to multiple IP addresses so you won't be able to run a web server on a local network and also run DigiButler as they both use port 80.

## The end result: network, web and WAP

The home automation server is ready for access over a network as soon

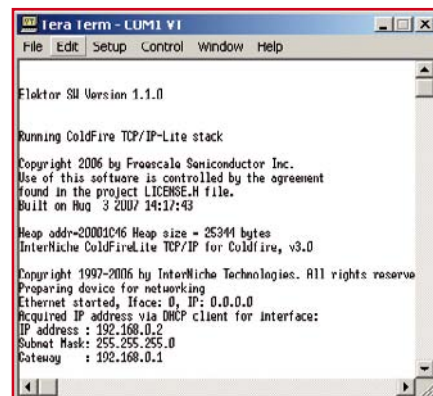




**Figure 4. "It's alive Jim!"**  
Output from serial port after DigiButler is reset.

as the Coldfire device has been programmed and the network cable is

## (re-)Flashing your board

The following procedure was recorded with a PE Micro parallel programmer / debugger pod connected to J1 on the DigiButler board, a laptop PC running Windows XP and a downloaded version of CodeWarrior 6.3. TBCLF may require different jumper settings and steps, please consult the TBCLF documentation. Updates to this procedure may become available at [www.elektor.com/digibutler\\_en](http://www.elektor.com/digibutler_en).

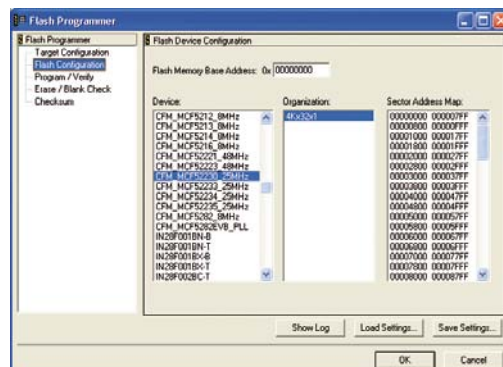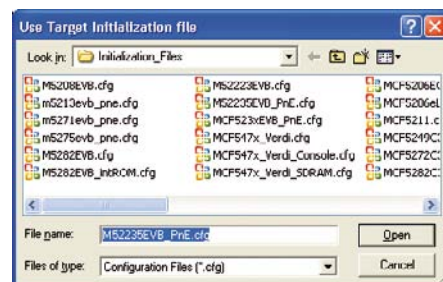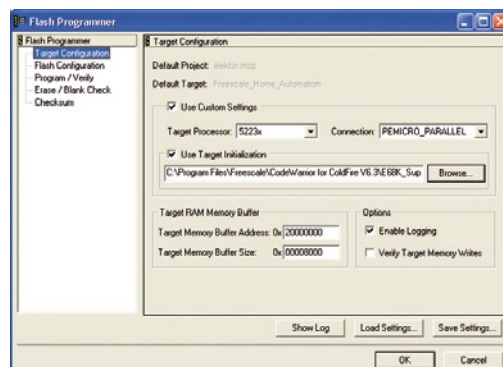1. Fit jumper JP2 and set jumper JP1 to the right-hand position (2-3).
2. Start the CodeWarrior IDE, open the project 'elektor.mcp' using the File→Open command in the IDE menu bar. Connect the debug pod to connector J1 and apply power to the board.
3. Use Tools→Flash Programmer to bring up the Flash Programmer dialogue box.
4. In the Target Configuration menu, Browse to the Target Initialization files and there select and Open: M52235EVB\_Pne.cfg
5. In the Flash Configuration menu, select: CFM\_MCF52230 25 MHz.
6. Go to the Erase /Blank Check menu and run an Erase action. This is useful to check if the connection to the target is okay. If erasure is successful, the comms are okay. Click on Save Settings.
7. Now go to Program/Verify and browse to the file 'web\_coordinator' (without an extension). This is a precompiled binary image, included for those who do not wish to recompile the source code.
8. Program the device! With the device programmed, the board is ready to be used.



connected to either a router or a PC. Remember that when connecting directly to a PC, the network cable must be a crossover type. Enter DigiButler's IP address in the web browser of a PC on the same network and an authorisation dialog box will be presented (Figure 6). The default user name is 'user' and the password is '1234567'. If required, both can be changed in the project source code.

Successful authentication brings up the default main web page, *index.htm*. As illustrated in Figure 7, a graphic image on the example default web page shows the status of the relay. The project source code allows you to substitute your own image! A dark image signifies that the relay (RE1) (lamp) is off, while a bright image shows that the relay (lamp) is on. The relay can be switched on and off remotely using Light ON / Light OFF button on the web page. Application note AN3455 (ref. [2] in part 1) gives an in depth description of an alternative method of switching the relay on and off using web page variables in a browser address bar. From the same web page it is also possible to set a timer for when the relay should switch on or off, this function making use of the Coldfire's real time clock. And lastly, the example page allows the user password to be changed if desired.

The process for talking to DigiButler over the Internet is exactly the same. Entering the router IP address in the browser of an Internet connected PC gives the same results, but only if the router has been set up for forwarding port 80 to the DigiButler's local IP address. In our example, the router address is 86.131.22.120. Be aware that it might not be possible to access the server from a PC within a local network, if you use the router IP address. If you are having difficulty remembering the IP address, NO-IP [3] offers a free service which maps the IP address to an easy to remember sub domain name.

Finding an Internet connected PC is not always possible or safe, so WAP phone access is also supported. Nearly all modern mobile phones have WAP, but the serv-

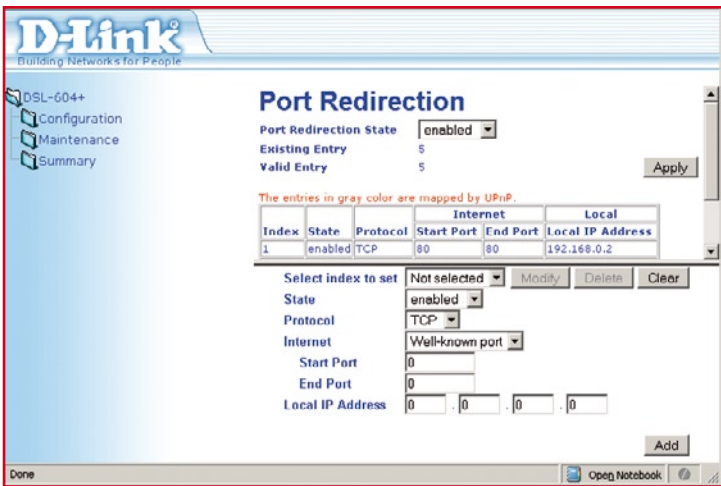


Figure 5. Most routers support port redirection or port forwarding. Setting the IP address and port number allows Internet users to access DigiButler on a local network.

ice is subject to what your provider is offering you. DigiButler's default WAP page is *wap.wml*. Entering our example URL,

```
http://86.131.22.120/wap.wml
```

from the browser of a WAP enabled phone, gives similar results as before but without the images. The WAP pages have been tested using Nokia and Samsung mobiles, but may need to be changed to support other manufacturers' handsets.

Creating and uploading web pages

A neat feature of the software is its support for dynamic uploading of new web pages. The following is intended for those having some experience in programming web-connected devices.

By implementing an Ethernet writable FLASH based file system, it's possible to update web pages remotely without reprogramming the Coldfire device. Two file systems are actually implemented — a static compile time system and the dynamic writable sys-

tem. Both can be used to store web pages, graphics files and other content and both allow directory structures and file names up to 255 characters. Since the application looks in the writable system for a requested file before searching the compile time file system, it's possible to override the compiled files. For example, if an image file exists in both file systems with the same name, then the file in the writeable system will be used and the one resulting from the compile will be ignored.

Example web pages and Ethernet loading utilities can be found in the *web\_page* directory of the project. The files required to upload new web content to the automation server are *make.bat*, *filelist.txt*, *emg\_dynamic\_ffs.exe* and *emg\_web\_uploader.exe*.

The batch file *make.bat* conveniently calls the necessary utilities to compress and upload the web-resultant content image file using the files listed in *filelist.txt*. Before executing *make.bat*, change the IP address in the line

```
emg_web_uploader 10.171.88.63 dynamic.ffs joshua
```

in *make.bat* to the board's IP address as shown in the terminal window. The parameter *dynamic.ffs* is the name of the compressed file image generated by compression utility *emg\_dynamic\_ffs.exe*. This compresses the files in *filelist.txt* into a single image. The parameter *joshua* is the upload security key, used to prevent unauthorized upload of web content. DigiButler will verify the supplied security key with the version in memory and upload only if both match. The security key can be changed in the server source code if required.

An example of the contents of *filelist.txt* is shown below. These files will be compressed into one image for upload to the server. The last line in the file must be a blank line with only a CRLF (i.e. hit Enter in the last blank line).

\* This is a list of the files stored in the bin file.

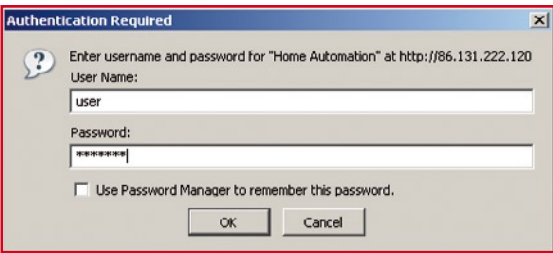


Figure 6. The first access in a web session requires the user to enter a username and password before access is granted to the main page of the home automation server.

\* The files are arranged in the order they are listed here.

```
index.htm
kitchen.jpg
black.jpg
main.js
pot_data.txt
fsllogo.gif
variables.htm
wap.wml
wap1.wml
wap2.wml
wap_main.wml
incorrect.wml
```

## Overcoming firewalls

Both FTP or TFTP protocols are commonly used to upload files to web servers. However, many firewalls and routers consider these protocols as dangerous and block the transfer, which causes a problem if trying to upload new content to the automation server. To overcome this, the utility *emg\_web\_uploader.exe* uses TCP and port 80 thereby getting around the problem.

## Enhancements and your contributions

DigiButler opens up many exciting opportunities for controlling devices remotely and for remote real time data measurement. Analogue and digital signals can be captured, measured and subsequently analysed from a web browser. For example, a sensor could

be added to the DigiButler analogue inputs and be read remotely using the HTML VARS function described in AN3455. With some modification to the software, images could be captured using a VGA camera module such as the C328-7640 [4].

The prototyping area on the board allows you build your own extension circuits. Many signals to and from the microcontroller are conveniently found

on J11 and J12, while the  $V_{ext}$  pin close to the fuse may help to power the extension(s). The same for the +3.3 V rail which can be 'tapped' near J11 (but watch the extra current consumption of your extension circuit). If you duplicate the existing relay circuit for the control of a second 230 VAC load, be sure to observe electrical safety precautions.

The authors look forward to seeing your applications and extensions as the project was designed and published with the open-source concept in mind. A dedicated web page will be 'at your service' at [www.elektor.com/digibutler\\_en](http://www.elektor.com/digibutler_en).

(071102-1)

## Web Links


[1] [www.freescale.com/webapp/sps/site/prod\\_summary.jsp?code=CWS-MCF-STDED-CX&nodeId=01272694012E704080&fsp=1&tab=Design\\_](http://www.freescale.com/webapp/sps/site/prod_summary.jsp?code=CWS-MCF-STDED-CX&nodeId=01272694012E704080&fsp=1&tab=Design_)

Tools\_Tab

[2] [www.pmicro.com/products/product\\_view\\_Details.cfm?product\\_id=163&menu\\_id=details&CFID=1032336&CFTOKEN=52342289](http://www.pmicro.com/products/product_view_Details.cfm?product_id=163&menu_id=details&CFID=1032336&CFTOKEN=52342289)

[3] [www.no-ip.com/services/managed\\_dns/free\\_dynamic\\_dns.html](http://www.no-ip.com/services/managed_dns/free_dynamic_dns.html)

[4] VGA camera module  
[www.electronics123.com/s.nl/it.A/id.2027/.f?sc=8&category=233](http://www.electronics123.com/s.nl/it.A/id.2027/.f?sc=8&category=233)

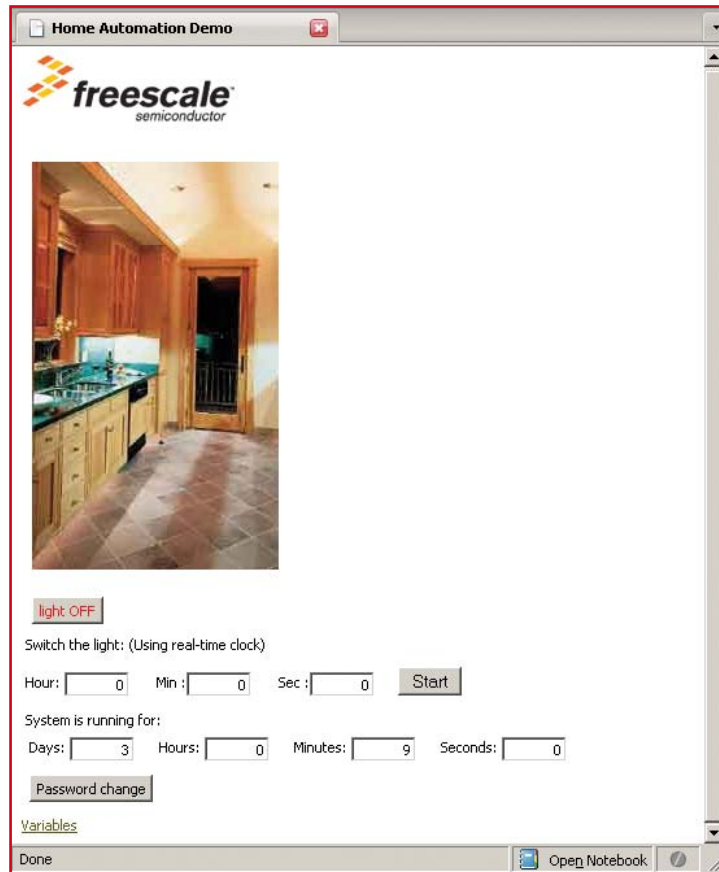

**Figure 7.** The first web page the user sees when accessing DigiButler from a PC web browser. You can switch the kitchen lighting on and off.

## Changing the IP address

You may wish to use a fixed IP address instead of having an IP address assigned by the router's DHCP server functionality. This is possible by making two simple code changes. The first is to switch off the DHCP functionality by commenting out the line

```
#define DHCP_CLIENT 1 /* include DHCP client code */
```


in the file 'ipport.h'. The second is to set the IP and gateway addresses and subnet mask. Example values for these parameters are included in file 'main.c'. Change them according to your setup and remember to change the #if 0 statement to #if 1.

```
#if 0
IP_ADDRESS (213, 194, 223, 49);
DEF_GATEWAY (213, 194, 223, 1);
SUBN_MASK (255, 255, 255, 128);
```

# Two-wire LCD

## ATM18 display for the Elektor AVR project

Udo Jürss  
and Wolfgang Rudolph

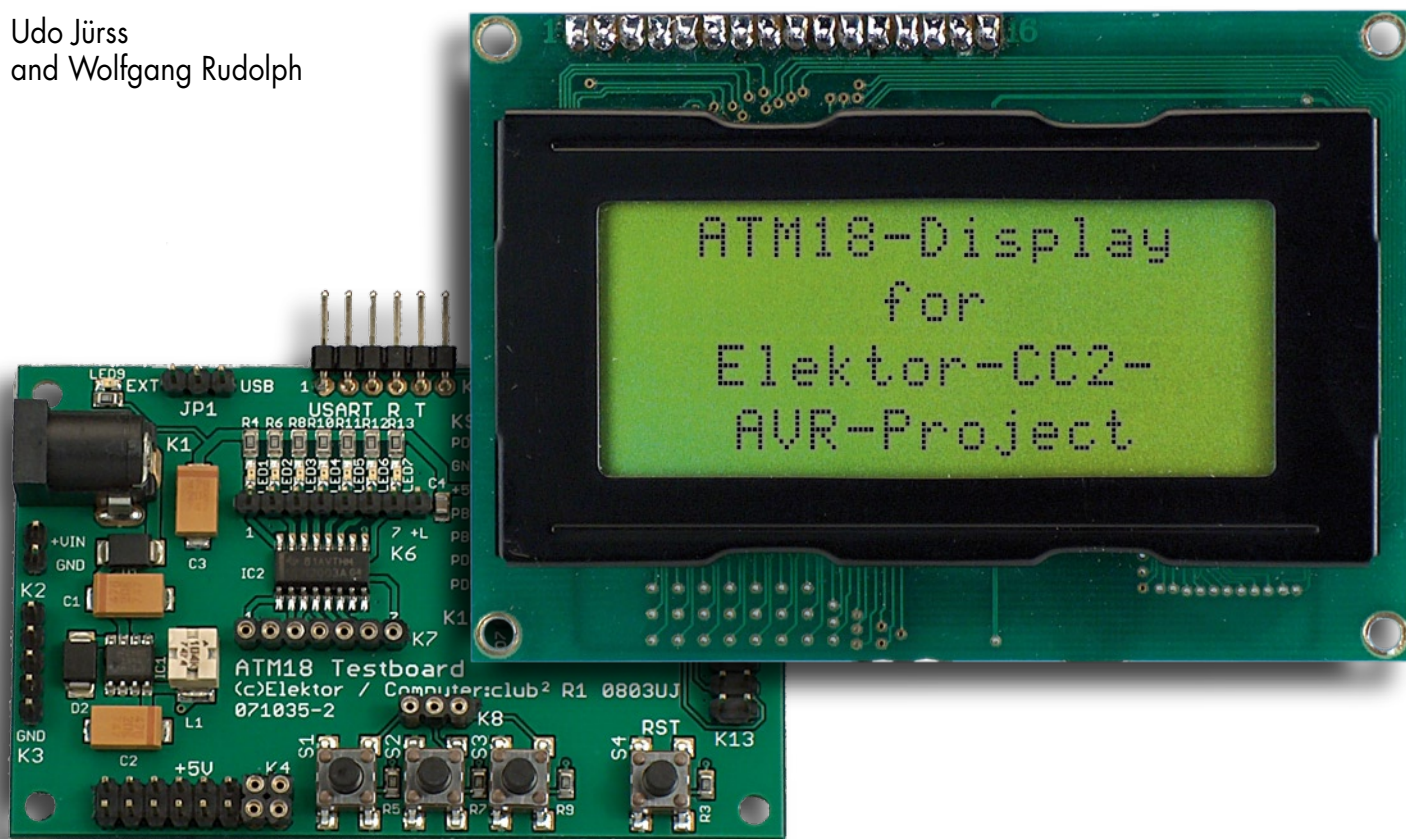

**This LCD expansion module for the ATM18 test board opens up a huge range of applications. Although the design might look like a standard interface between microcontroller and LCD panel, there is an elegant technical detail: in order to minimise the number of port pins required, a special two-wire interface has been developed.**

An ordinary LCD panel can be driven from a microcontroller using either four or eight data wires. In addition to these, an RS signal is needed to distinguish data from commands, and an E signal

is needed to clock the data into the panel. This large total number of connections is unfortunate in our application because it ties up a number of port pins that could be used for other purposes.

### Data transfer

All ordinary LCD panels are connected using 14 wires, plus any connections needed for the backlight. It is here

Pins 14 down to 7: data bus

Pin 6:E (enable signal), active high

Pin 5: R/W, 0 = write, 1 = read

Pin 4: RS, 0 = command, 1 = data


Pin 3: V0, contrast adjustment from 0 V to 2 V

Pin 2: VDD, +5 V


Pin 1: VSS, 0 V
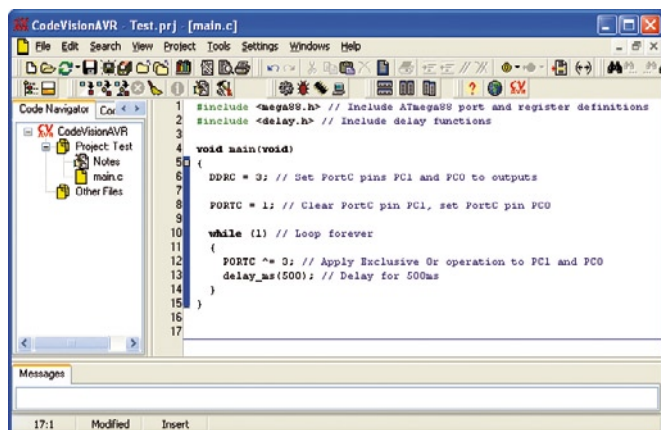
## C compiler

Software house HPInfoTech has produced a special free-of-charge version of their popular 'CodeVisionAVR' compiler for this Elektor project. The compiler supports the ATmega48, ATmega88, ATmega168 and



CodeVisionAVR in use

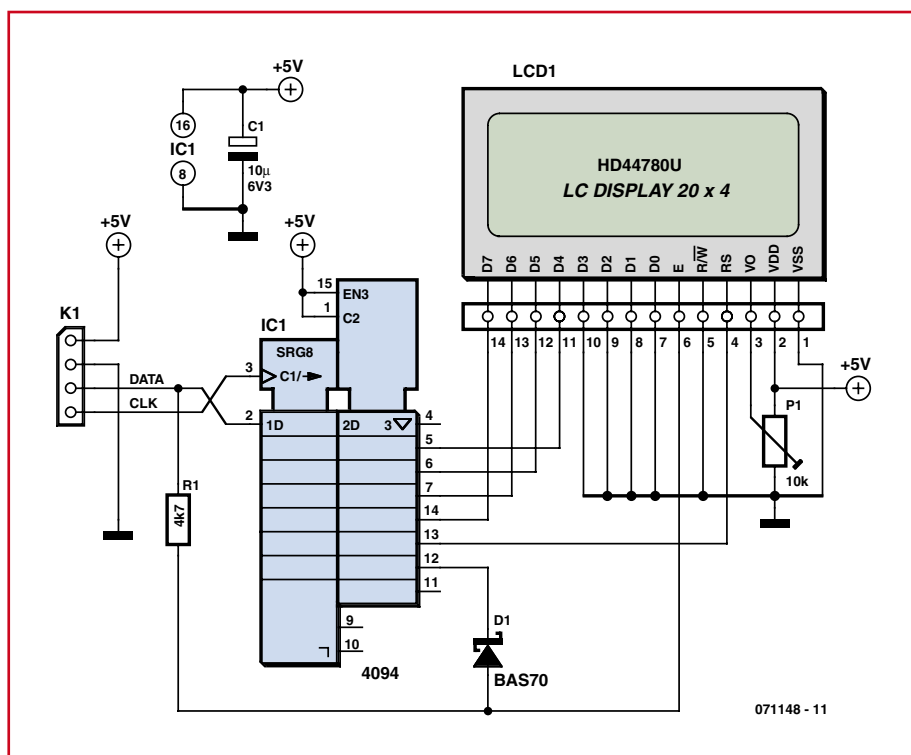

**Figure 1.** The LCD interface is built around a shift register.

The circuit is based around a port expander that uses two port bits. A natural choice for such a design would be

the I<sup>2</sup>C bus, but we have chosen a faster and cheaper approach. All that we need is a type 4094 shift register (see Figure 1). This allows clock rates of sev-

A version limited to 16 kB code size costs around fifty pounds and a 32 kB version is around sixty pounds, within the reach of many hobbyists.

The compiler produces very efficient code and includes a so-called 'smart linker' that only includes in the final object file functions that are actually called. It is therefore possible to use comprehensive libraries without having to tailor them to each application.

CodeVision makes setting up a project very straightforward. The integrated 'CodeWizard' automatic program generator generates a complete skeleton for your program. Beginners in particular will find it helpful to use this as a model for their programs in the same way as they can learn from our example programs. Automatic generation of libraries and selection between application and bootloader code, as well as code templates for frequently wanted program functions, make it easier to get started. Built-in drivers for all current programming adaptors allow devices to be programmed directly from within CodeVision. Internal EEPROM and fuse bits can also be programmed, and there is a built-in terminal with file transfer and hexadecimal debugging output. The compiler offers powerful optimisation features for advanced users including global register allocation and freely-programmable ISR entry and exit code, comprehensive help (also available on-line) and a debugging interface to AVR Studio.

eral MHz rather than the 400 kHz maximum that can be achieved using I<sup>2</sup>C.

At first sight things might look a little complicated. First we have to send the data bits D4 to D7 and RS, and then we have to generate an enable pulse on the E wire. To achieve this, the data input to the shift register is logically ANDed with output Q7 using a resistor and a diode.

Only when Q7 is high will a pulse on

the data input be transmitted to the LCD as a pulse on its E input. To make sure that no spurious E pulses are generated, the following sequence must be observed.

1. Clock eight zero bits into the shift register by setting the data signal low and generating eight clock pulses. The bits are clocked in on each rising clock edge. Now all the Q outputs of the shift

register are low, and in particular no E signal can be generated.

2. Now send seven data bits. The first bit must be high and will ultimately appear on Q7, where it will allow an E pulse to be generated. The second bit is destined for the RS signal on Q6; the next four bits are data. The final bit is zero, ensuring that the data signal is left low. After a total of seven clock pulses the data bits will appear as required on the Q outputs, and in particular Q7 will be high.

3. Now we emit a pulse on the data signal, which in turn generates a pulse on the E line because Q7 is high.

The above procedure must be carried out twice, once for the high data nibble (bits D4 to D7) and once for the low data nibble (bits D0 to D3). **Listing 1** shows an excerpt from the BASCOM example program that can be downloaded from the *Elektor* website. Data can be written to the LCD (with RS being set high) using `Lcd_write_data`, while commands can be sent (RS low) using `Lcd_write_ctrl`, for example when initialising the display controller.

## Initialisation

The display recognises a large number of commands, all of which are sent with RS set low. The commands are grouped into families according to the number of zeros that appear in the high-order bits of the command byte (see **Table 1**). The display also includes an internal cursor register that points to an individual character position on the display. In the case of a two-by-sixteen display we have:

Row 1: addresses 00h to 0Fh  
Row 2: addresses 40h to 4Fh

while for a four-line display with 20 characters per line we have:

Row 1: addresses 00h to 13h  
Row 2: addresses 40h to 53h  
Row 3: addresses 14h to 27h  
Row 4: addresses 54h to 67h

The cursor advances automatically as each character is written, or the address can be set directly in order to write to any desired position. On power-up a number of initialisation commands must be written to the command register. **Listing 2** shows an example of how an LCD can be initialised

## Listing 1

### Data transfer using the shift register

```
Sub Lcd_write_data(byval D As Byte )
  Rs = 1
  Low_nibble = D And 15
  High_nibble = D / 16
  Lcd_write_nibble High_nibble
  Lcd_write_nibble Low_nibble
End Sub

Sub Lcd_write_ctrl(byval D As Byte )
  Rs = 0
  Low_nibble = D And 15
  High_nibble = D / 16
  Lcd_write_nibble High_nibble
  Lcd_write_nibble Low_nibble
End Sub

Sub Lcd_write_nibble(byval D As Byte )
  Pe_clock = 0
  Pe_data = 0
  'Clear all stages of shift register
  For N = 1 To 8
    Pe_clock = 1
    Pe_clock = 0
  Next N
  'Set E level at Q7
  Pe_data = 1
  Pe_clock = 1
  Pe_clock = 0
  'Set level for RS at Q6
  Pe_data = Rs
  Pe_clock = 1
  Pe_clock = 0
  'Shift in 4 bits
  Mask = 8
  For N = 1 To 4
    State = D And Mask
    If State = 0 Then
      Pe_data = 0
    Else
      Pe_data = 1
    End If
    'Clock in data with rising edge
    Pe_clock = 1
    Pe_clock = 0
    Shift Mask , Right
  Next N
  'Shift in zero bit
  Pe_data = 0
  Pe_clock = 1
  Pe_clock = 0
  'Set E
  Pe_data = 1
  Pe_data = 0
End Sub
```

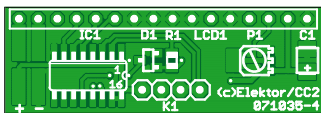


Figure 2. Printed circuit board for the LCD expansion module.

## COMPONENTS LIST

### Resistors

R1 = 10k $\Omega$  (SMD 805)  
P1 = 10k $\Omega$  preset (SMD)

### Capacitors

C1 = 10 $\mu$ F 6.3V (SMD)

### Semiconductors

D1 = BAS70 (SMD)  
IC1 = 4094 (SMD SO16)

### Miscellaneous

K1 = 4-way SIL pinheader  
LCD1 = LC Display 4x20 characters  
(HD44780 compatible)  
14-way SIL pinheader  
PCB with SMDs premounted, incl. all  
parts and 4x20 LCD; Elektor Shop #  
**071035-93**

Table 1. Display commands

Function	7	6	5	4	3	2	1	0
Clear display	0	0	0	0	0	0	0	1
Cursor home	0	0	0	0	0	0	1	x
Entry mode	0	0	0	0	0	1	ID	S
(ID=1/0: right/left, S=1/0: without/with scroll)								
Display, Cursor	0	0	0	0	1	D	C	B
(D,C,B=1/0: display, cursor, blink on/off)								
Scroll	0	0	0	1	SC	RL	x	x
(SC=1/0: scroll/cursor moves to RL=1/0: right/left)								
Initialisation	0	0	1	DL	N	x	x	x
(DL=1/0: 8-/4-bit bus, N=1/0: two lines/one line)								
User-defined character memory	0	1	Character			Column		
Display memory	1	Memory address						

over its four-bit data bus.

### Text output

In order to display text at a defined po-

sition we must first set the cursor address. It is convenient to express the position in terms of the column (x-coordinate) and row (y-coordinate). Then a call to Lcd\_pos will move the cursor as

## Listing 2

### Initialisation

```
Sub Lcd_init
  Waitms 50
  Lcd_write_ctrl &H20
  Waitms 50
  Lcd_write_ctrl &H20
  Waitms 50
  Lcd_write_ctrl &H28
  Waitms 50
  Lcd_write_ctrl &H0C
  Waitms 50
  Lcd_write_ctrl &H01
  Waitms 50
End Sub
```

## Listing 3

### Text output

```
Sub Lcd_pos(byval X As Byte , Byval Y As Byte )
  D = 127 + X
  If Y = 2 Then D = D + 64
  Lcd_write_ctrl D
End Sub

Sub Lcd_text(byval Text As String )
  J = Len(text)
  For I = 1 To J
    Char = Mid(text , I , 1 )
    D = Asc(char)
    Lcd_write_data D
  Next I
End Sub
```

Advertisement



Die-cast aluminium,  
metal and plastic  
enclosures.

sales@hammond-  
electronics.co.uk

[www.hammondmfg.com/uk](http://www.hammondmfg.com/uk)



required. For example, Lcd\_pos 1,1 will move the cursor to the leftmost column of the first row. Then Lcd\_text can be used to write a string of characters, as illustrated in **Listing 3**.

## Printed circuit board

The interface circuit can be constructed on the compact printed circuit board shown in **Figure 2**, which uses SMD components. Those wary of soldering SMDs can purchase ready-populated boards from the Elektor shop, with just the external connections left to be soldered by hand. The four-way connection to the ATM18 test board is best fitted with a header socket so that temporary connections can be made for test purposes using lengths of solid-core wire.

The 16-way connection can also be fitted with a socket or plug to mate with a connector on the LCD, or direct connection can be made using header pins or a ribbon cable. The four connections to the microcontroller are  $V_{CC}$ , GND, data and clock. Data and clock can be

connected to any two port pins: the example software uses port B.1 for clock and port B.2 for data.

## In use

Using the display module is very easy. **Listing 4** shows a simple example program that displays a measured voltage

on analogue input ADC(0). The analogue-to-digital converter is configured to use the external 5 V reference, and the 10-bit conversion result, in the range 0 to 1023, is written to the display. The complete example program is available for free download from the *Elektor* website at [www.elektor.com](http://www.elektor.com).

(071148-1)

## Listing 4

### Outputting a measured value

```
Config Adc = Single , Prescaler = 64 , Reference = Off
Start Adc

Lcd_init

Lcd_pos 2 , 1
Lcd_text „adc(0) = “

Do
    Lcd_pos 2 , 2
    Value = Getadc(0)
    Text = Str(value)
    Lcd_text Text
    Waitms 500
Loop
```

Advertisement

# PCB-Soldering.co.uk

Suppliers of PCB Soldering Equipment & Rework Stations

## NEW IN STOCK

### 328 Working Platform

<p style="writing-mode: vertical-rl; transform: rotate(180deg);"><b>850A+ SMD Rework Station</b></p> <p style="text-align: center;">Online Price £44.95</p>	<p style="writing-mode: vertical-rl; transform: rotate(180deg);"><b>932 Vacuum Pick Up Station</b></p> <p style="text-align: center;">Online Price £29.95</p>	<p style="text-align: center;"><b>937+ 45W Soldering Station</b></p> <p style="text-align: center;">Online Price £37.95</p>	<p style="text-align: center;"><b>Range Of Tools &amp; Accessories</b></p>
<p style="writing-mode: vertical-rl; transform: rotate(180deg);"><b>2738 CPU Controlled PCB Work Station</b></p> <p>Kit Includes: Hot Air Gun 6 x Air Nozzles 70W Soldering Iron with Fume Absorber Soldering Iron Stand Soldering Iron Tip with Heating Element Vacuum Suction Pen Heat Resistant Pad IC Removal Tool 2 x Carbon Filters</p> <p style="text-align: center;">Online Price £139.95</p>	<p style="text-align: center;"><b>2900 70W Soldering Station</b></p> <p style="text-align: center;">Online Price £74.95</p>	<p style="text-align: center;"><b>Soldering Iron Tips &amp; Air Nozzles</b></p> <p style="text-align: center;">Wide Selection Available</p>	
<p style="writing-mode: vertical-rl; transform: rotate(180deg);"><b>853A Quartz Infrared Preheater</b></p> <p style="text-align: center;">Online Price £69.95</p>	<p style="text-align: center;"><b>950 SMD Hot Tweezers &amp; Station</b></p> <p style="text-align: center;">Online Price £44.95</p>	<p style="text-align: center;"><b>710 Infrared Welding Station</b></p> <p style="text-align: center;">Online Price £750.00</p>	

## www.pcb-soldering.co.uk

Allendale Electronics Ltd, 43 Hoddesdon Industrial Centre,  
Pindar Road, Hoddesdon, Hertfordshire. EN11 0FF.

T: +44 (0)1992 450780 W: [www.pcb-soldering.co.uk](http://www.pcb-soldering.co.uk)  
F: +44 (0)1992 450781 E: [sales@pcb-soldering.co.uk](mailto:sales@pcb-soldering.co.uk)

Suppliers of Test-pins, Receptacles & Probes...

For Test-pins & Probes Visit [www.test-pins.co.uk](http://www.test-pins.co.uk)  
Above discount code also applies

**08717**

**Credit Card  
Sales**

**177 168**

## Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, Unipolar/Bipolar stepper motors and servo motors. See website for full details.

### PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm.  
Kit Order Code: 3179KT - **£12.95**  
Assembled Order Code: AS3179 - **£19.95**



### Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30Vdc. PCB: 75x85mm.  
Kit Order Code: 3158KT - **£17.95**  
Assembled Order Code: AS3158 - **£27.95**



### Bi-Directional DC Motor Controller (v2)

Controls the speed of most common DC motors (rated up to 32Vdc, 10A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections.  
Kit Order Code: 3166v2KT - **£17.95**  
Assembled Order Code: AS3166v2 - **£27.95**



### DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H.  
Kit Order Code: 3067KT - **£13.95**  
Assembled Order Code: AS3067 - **£21.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

## Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 £8.95

### 8-Ch Serial Isolated I/O Relay Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs. 4 isolated digital inputs. Useful in a variety of control and sensing applications. Controlled via serial port for programming (using our new Windows interface, terminal emulator or batch files). Includes plastic case 130x100x30mm. Power Supply: 12Vdc/500mA.  
Kit Order Code: 3108KT - **£54.95**  
Assembled Order Code: AS3108 - **£64.95**



### Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 45x45mm. Powered by PC. Includes one DS1820 sensor.  
Kit Order Code: 3145KT - **£17.95**  
Assembled Order Code: AS3145 - **£24.95**  
Additional DS1820 Sensors - **£3.95 each**



### Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two and Ten channel versions also available.  
Kit Order Code: 3180KT - **£44.95**  
Assembled Order Code: AS3180 - **£54.95**



### DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. Not BT approved. 130x110x30mm. Power: 12Vdc.  
Kit Order Code: 3140KT - **£54.95**  
Assembled Order Code: AS3140 - **£69.95**



## Infrared RC Relay Board

Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12Vdc/0.5A  
Kit Order Code: 3142KT - **£47.95**  
Assembled Order Code: AS3142 - **£59.95**



## PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

### Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) **£14.95**  
18Vdc Power supply (PSU010) **£18.95**  
Leads: Parallel (LDC136) **£395** / Serial (LDC441) **£3.95** / USB (LDC644) **£2.95**

### NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. Wide range of supported PICs - see website for complete listing. ZIF Socket/USB lead not included. Supply: 16-18Vdc.  
Kit Order Code: 3149EKT - **£39.95**  
Assembled Order Code: AS3149E - **£49.95**



### NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB lead not included.  
Assembled Order Code: AS3128 - **£44.95**



### "PICALL" PIC Programmer

"PICALL" will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC16C5x family) programmed PIC micro controllers. Free fully functional software. Blank chip auto detect for super fast bulk programming. Parallel port connection. Supply: 16-18Vdc.  
Assembled Order Code: AS3117 - **£24.95**



### ATMEL 89xxx Programmer


Uses serial port and any standard terminal communications program. Program/ Read/ Verify Code Data, Write Fuse/Lock Bits, Erase and Blank Check. 4 LED's display the status. ZIF sockets not included. Supply: 16-18Vdc.  
Kit Order Code: 3123KT - **£24.95**  
Assembled Order Code: AS3123 - **£34.95**



# Elektor AVRprog

Benedikt Sauter and Dr. Thomas Scherer

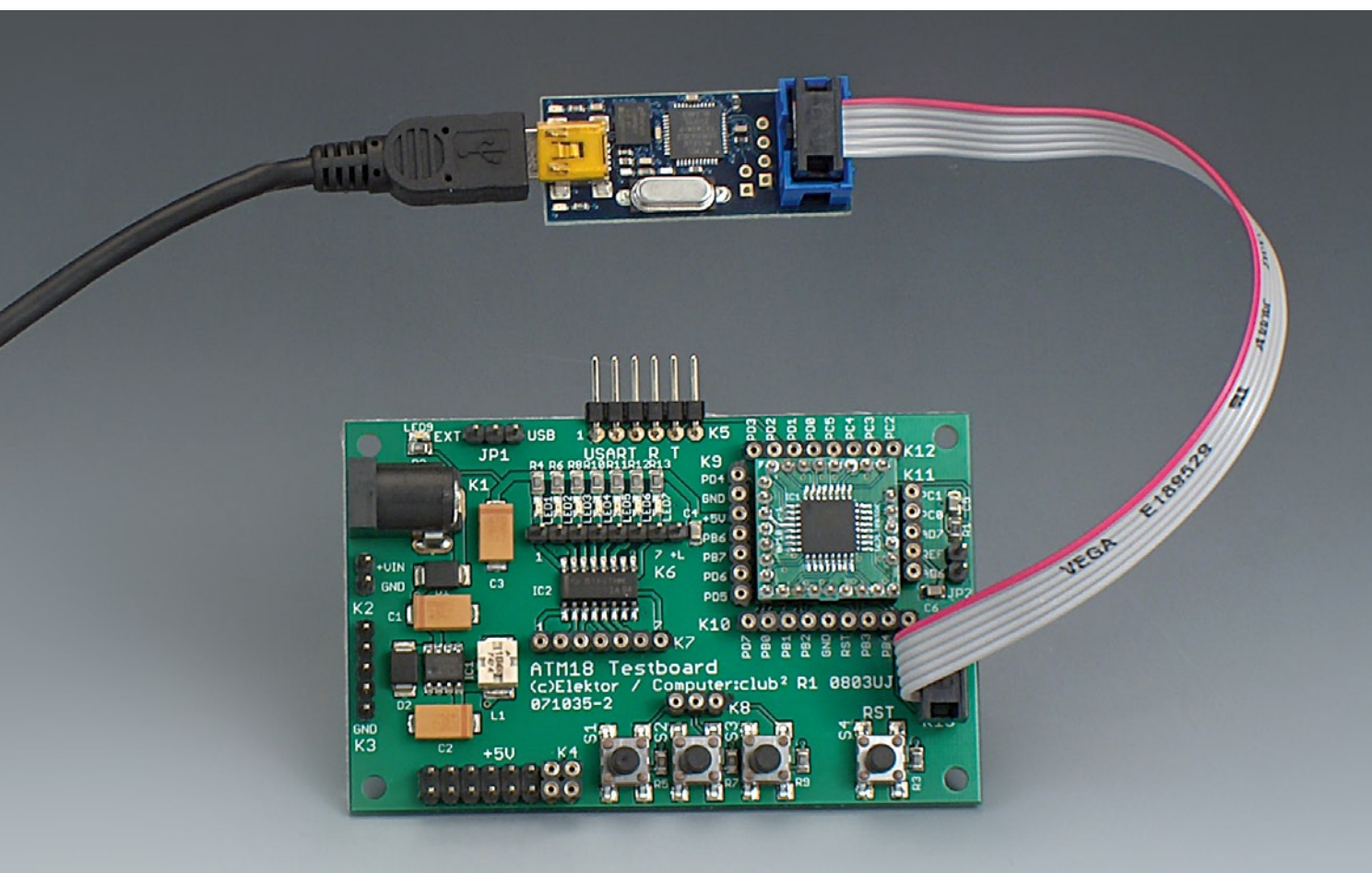**Two events triggered the conception of this AVR programmer: the feedback received on USBprog from Elektor, October 2007 and a series of articles started last month around our ATM18 project. The outcome is a plug-and-play AVRISP mk2-compatible USB programmer for AVR controllers!**



Since the launch of USBprog in October 2007 [6] many readers have explored Benedikt Sauter's website [1] and discovered his amazing open source circuit, on a par with the all-in-one animal of mythology that provided mankind with eggs, wool, milk and meat. This little printed circuit board (PCB) has aroused deserved admiration and to the extent that it fulfilled the requirements of a number of *Elektor* readers it was certainly a success story. All the same, feedback from other readers indicated that the capabilities offered in

Benedikt's solution (USB-serial converter and ARM programmer for instance) were not exactly top of their wants list. They were mainly interested in using the device as a straightforward AVRISP mk2-compatible programmer for deploying with a diverse range of software applications.


## Simple solution

A sample wish list for a new programmer would include the phrases 'simple to construct', 'user-friendly' and

'inexpensive' (OK, let's be honest — 'cheap'). A quick opinion poll indicated that reinventing the wheel was not what people wanted, so Mr Sauter got on with slimming down the circuit of USBprog to produce a kind of dedicated programmer for AVR controllers with a user outlay that would be a whole lot cheaper than the more complex circuits already available.

Doing without a bootloader and other technical frills in this programmer made it possible to employ an ATmega16 instead of an ATmega32. The cir-

# Simple AVR universal programmer with USB

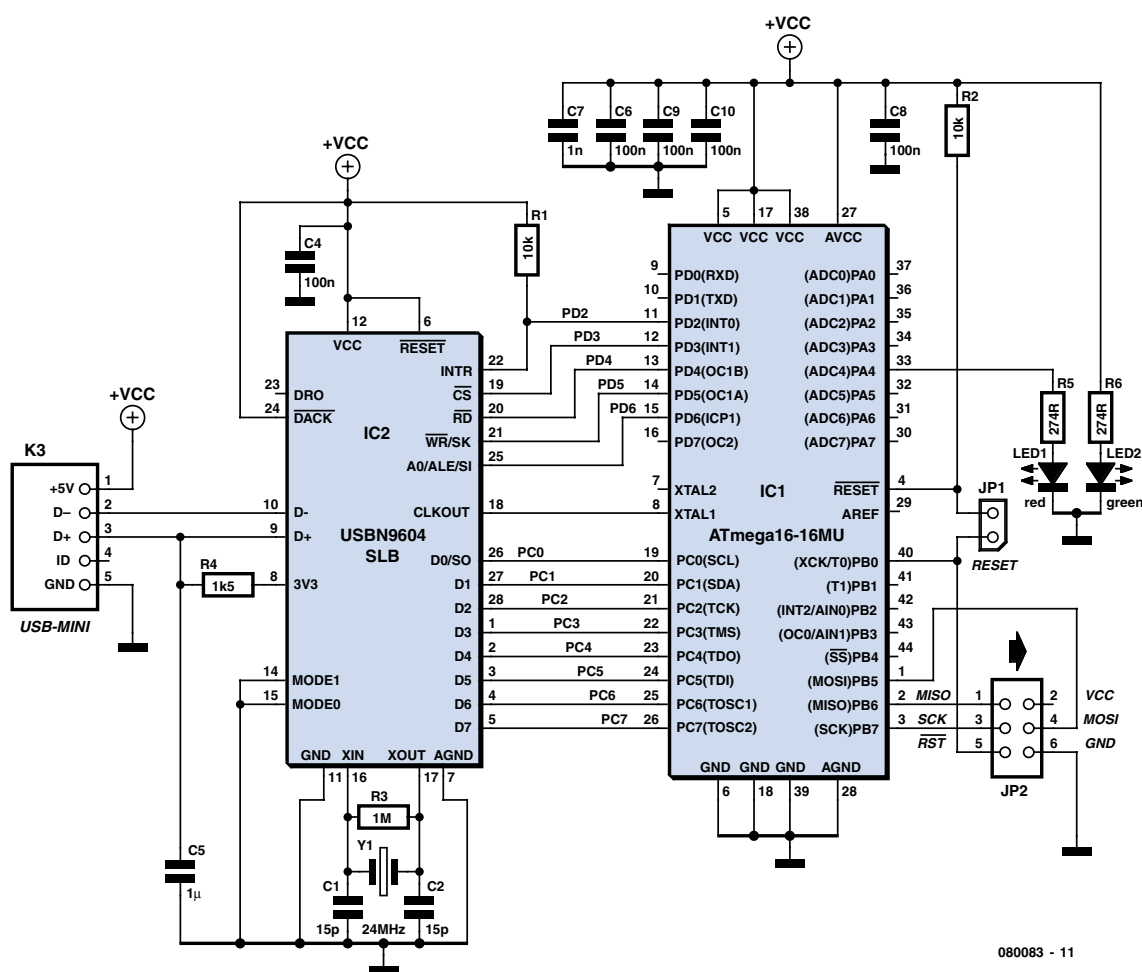

**Figure 1.** The circuit of the Elektor AVRprog has much in common with its predecessor, USBprog, published in Elektor, October 2007. A USB bridge and a microcontroller are the only other components.

cuit of the Elektor AVRprog is little altered from the source design, as you can see in **Figure 1**. Space on the PCB is optimised by using a miniature USB connector and a 6-pin (instead of 10-pin) ISP interface. The resulting PCB is commendably petite, measuring just 4.0 x 1.7 cm (**Figure 2**).

We decided against offering this programmer in semi-kit form as a part-populated board; not everybody feels comfortable soldering microscopic surface-mount components in confined spaces. It seemed more logical to pro-


vide the ready-programmed ATmega16 along with the remaining electronics and PCB as a ready-to-use module that readers could employ without fiddling about. So that's what we decided to produce: a remarkably cheap AVR programmer for instant use, supplied complete with a matching USB cable and the necessary 6-way ISP cable.

## Software


As an AVRISP mkii clone the Elektor AVRprog is usable with a broad range

of software—effectively every program that supports this variant of AVRISP. That said, even the best USB hardware will achieve precious little without suitable drivers. The program AVR Studio 4 [2] from Atmel solves this problem at a single stroke; simply installing AVR Studio as shown in **Figure 3** with its own integrated drivers does everything necessary. Once this is done, you can plug the Elektor AVRprog into your PC straightaway.


Under Windows the new hardware is recognised automatically, using the

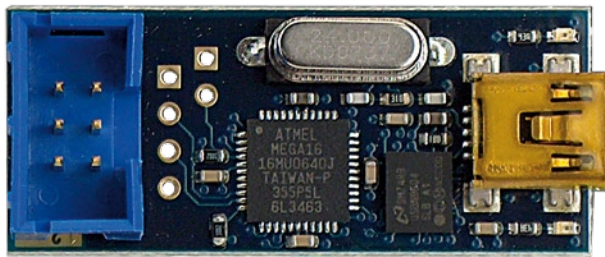

**Figure 2.** This is how the module looks when complete. A Mini USB connector and a 6-pin ISP interface help ensure its extremely compact dimensions.

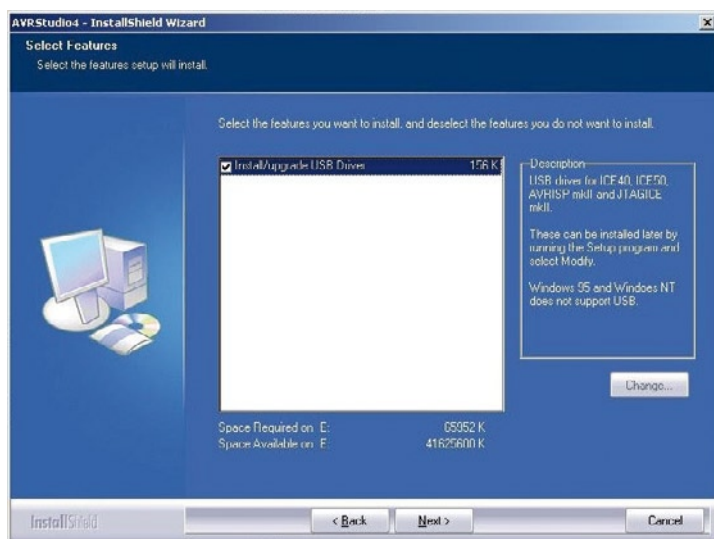

**Figure 3.** A screenshot taken during installation of AVR Studio 4 by Atmel. Once the software and drivers are installed, the Elektor AVRprog is usable without further ado.

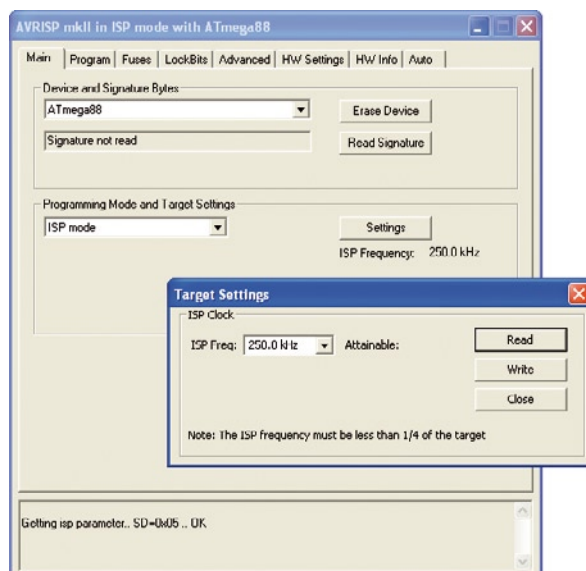

**Figure 4.** In this dialogue with AVR Studio (version 4.13) the so-called ISP frequency is being entered under 'Settings'.

dedicated driver. On many Windows XP installations, a false error message can occur at this stage, with the file 'libusb0.sys' not found and the user asked to indicate where the computer should look for it. Simply ignore this and click on 'Cancel'. The driver will in fact be found — assuming it is actually present — and installed without any further problems.

With the driver now installed you can deploy your Elektor AVRprog with a variety of software. For example, you can program it direct from CodeVision-AVR [3], but currently not directly from BASCOM [4] owing to a lack of AVRISP mkII protocols.

The Elektor AVRprog will also work with non-Windows computers. For Linux you have plenty of choice (search Google for Linux + AVRISP mkII + software), whilst the popular Open Source program AVRDUDE [5] is a stand-out solution for both Linux and Mac OS X. The command line interface of this program may be unfamiliar for Mac users, which is why the Elektor website has a PDF file explaining how to integrate AVRDUDE into a 'normal' graphical interface.

## Warning: speed trap!

AVR microcontrollers cannot be programmed at any frequency you might desire. The 'bitrate' for programming must be set no higher than a quarter of the clock frequency of the controller being used. If the controller's clock frequency is 8 MHz, the frequency you set in Elektor AVRprog must not exceed 2 MHz. This is the top limit feasible with this programmer. The lower limit is a rather tranquil 249 Hz. In truth this value is largely theoretical and not actually practicable. In any case AVR Studio version 4.13 will not allow you to program frequencies below 5 kHz. To see how you set this so-called ISP Frequency in AVR Studio take a look at **Figure 4**.

The programmer is, as already mentioned, an Open Source project. Among other things this means that not absolutely 100 per cent of AVR's are fully supported. No problems should arise with the usual types, however. Nevertheless, if something nasty crops up then it's worth taking a look at reference [1] to see if newer firmware exists. Although it may not be obvious, it is in fact possible to change firmware on the Elektor AVRprog. For this you need to link the two holes directly next to the crystal (it might be better to sol-

## COMPONENTS LIST

### Resistors

R1,R2 = 10k $\Omega$ , SMD 0603  
R3 = 1M $\Omega$ , SMD 0603  
R4 = 1k $\Omega$ , SMD 0603  
R5,R6 = 274 $\Omega$ , SMD 0603

### Capacitors

C1,C2 = 15pF, SMD 0603  
C4,C6,C8,C9,C10 = 100nF, SMD 0603  
C5,C7 = 1 $\mu$ F, SMD 0603

### Semiconductors

IC1 = Atmega16-16MU, MLF44  
IC2 = USBN9604SLB  
D1 = LED red, SMD 0603  
D1 = LED green, SMD 0603

### Miscellaneous

Y1 = 24 MHz quartz crystal, HC49/4 case  
K3 = Mini USB socket type A-USBB-M5/SMD  
JP2 = 6-way boxheader  
Ready-assembled and tested module, incl. USB and ISP cable, order code **080083-71** from Elektor Shop

## About the lead author

Benedikt Sauter is a passionate Open Source hardware and software developer and keeps himself busy with his website where he documents the Open Source applications he has developed.

der a small two-pin header and insert a jumper). Then, using a second programmer connected via the 6-pin ISP connector, you can introduce new firmware 'backwards' so to speak.

Bear in mind too that the Elektor AVRprog is designed to operate on 5 V. If the target chip is powered with 3.3 V or less during programming, the operation may fail under some circumstances. In this case the target controller should be powered with 5 V and 'transplanted' onto a small experimenter board if necessary.

(080083-1)

## Web Links and Literature

[1] **Project page:**  
[www.embedded-projects.net/usbprog](http://www.embedded-projects.net/usbprog)

[2] **AVR Studio 4:**  
[www.atmel.com/avrstudio](http://www.atmel.com/avrstudio)

[3] **CodeVisionAVR:**  
[www.codevision.be](http://www.codevision.be)

[4] **BASCOM:**  
[www.mcselec.com](http://www.mcselec.com)

[5] **AVRDUDE:**  
[www.nongnu.org/avrdude](http://www.nongnu.org/avrdude)

[6] **USBprog,**  
*Elektor*, October 2007.

Advertisement

# Displaying New Thinking



## Digital Panel Meters

An extensive range of LCD and LED voltmeters providing high-accuracy measurement of voltage, current and resistance.



## Graphics and Data Displays

A range of dot-matrix and data displays for micro-controller based applications available in LCD or LED.



## Custom Displays

Comprehensive custom design service offering a choice of technologies to deliver a functional, cost-effective and reliable display solution for your next project.

Whatever your display needs for your next project, Lascar can help.

Tel: +44 (0)1794 884567 - Fax: +44 (0)1794 884616 - E-mail: [sales@lascar.co.uk](mailto:sales@lascar.co.uk)

[www.lascarelectronics.com](http://www.lascarelectronics.com)

# Soldering SMDs with Simple job thanks to comprehensive

Harry Baggen

**The latest version of The Elektor DIY SMD oven, which goes by the name of ‘Reflow Control’, makes easy work of doing your own soldering of SMD parts on printed circuit boards, using a simple little electric oven. We already introduced the electronics for this project in last December’s issue. There is now a comprehensive kit available for this project, which allows even electronics enthusiasts with two left hands (do they exist even?) to easily build such an SMD oven.**

Since more and more electronics components are now available from their manufacturers only in SMD versions it is as a designer impossible to avoid using SMD parts. But making a single circuit or a small run of a few boards does not justify (certainly for use at home!) the purchase of a real SMD oven, which is necessary to mount all those little, leadless parts on the board. Can’t we think of a simpler solution?



Yes, of course we can! As we already wrote in the December 2007 article, with a special control circuit you can transform an ordinary kitchen oven into a handy SMD baking station. The control circuit that is required for this is now available from Elektor as a kit, so that there is no chicken and egg problem. To solder the SMD parts on the PCB you really need a reflow oven. But this is not ready yet because you need this board for that... etcetera. Now, that is no longer a problem because of this handy kit.

**Simple job**

The kit available in the Elektor Shop under part number **060234** contains all the parts for building the controller section. The only other thing you need is a cheap electric oven that you can buy from any appliance store.

A quick recap of the requirements for this oven. Use a simple analogue type, that is fitted with a mechanical thermostat and a mechanical clock. The temperature has to be adjustable to at least 225 °C and preferably a little higher still.

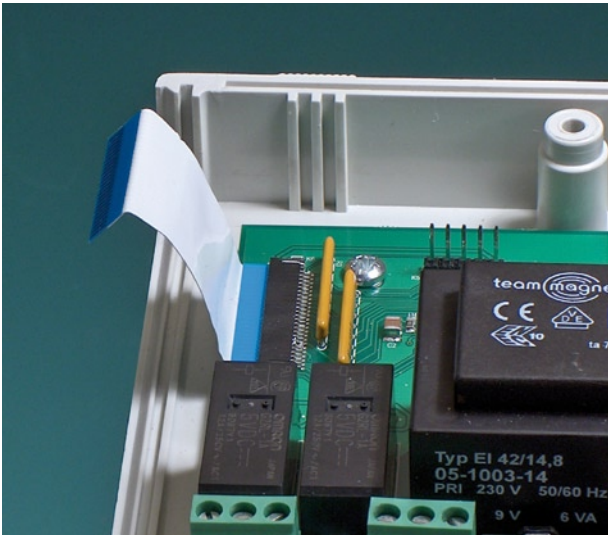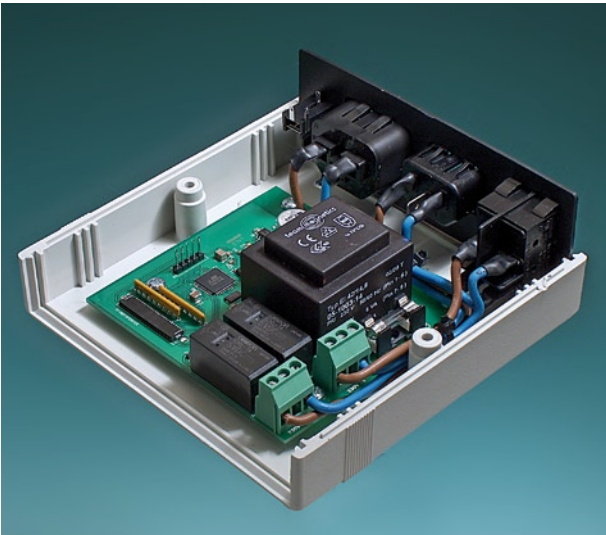It is also beneficial if the volume of the oven is as small as possible. This allows the temperature of the oven to increase rapidly. A power rating of 1.5 kW is usually enough. There is no need to make any changes to the oven itself.



# Reflow Control kit



The plug on the end of the standard power cord is replaced with the appliance connector that is included in the kit. The thermocouple from the kit is attached inside the oven.

## Contents of the kit



The kit for the Reflow Control circuit contains a completely assembled main board, a display and control panel board, and an enclosure with pre-milled front and rear panels. Plus of course all the other required little bits and pieces such as thermocouple, sockets, nuts, cables, cable ties, self-adhesive feet, mains switch, IEC connectors and a mains cable.

You only need to mount the boards in the case and make a few connections between the PCBs and the sockets/switch on the rear of the box.

The kit includes a clear construction manual which gives a step-by-step description of what you have to do. Even without electronics knowledge it is easily assembled within an hour. A separate operating manual describes how to use the Reflow Control circuit. This manual also discusses the calibration, the changing of the temperature profile and drying of components ('baking') using the oven.

With this kit you can build a very handy SMD oven in no time at all. A very useful device that quite possibly you may end up using more often than your ordinary soldering iron.


(071007-1)

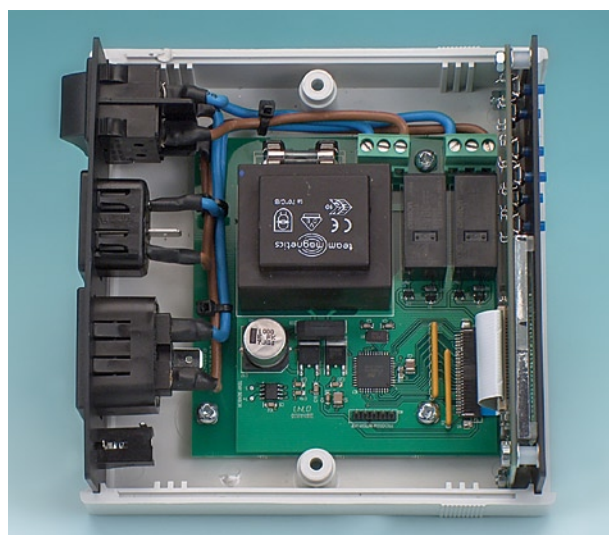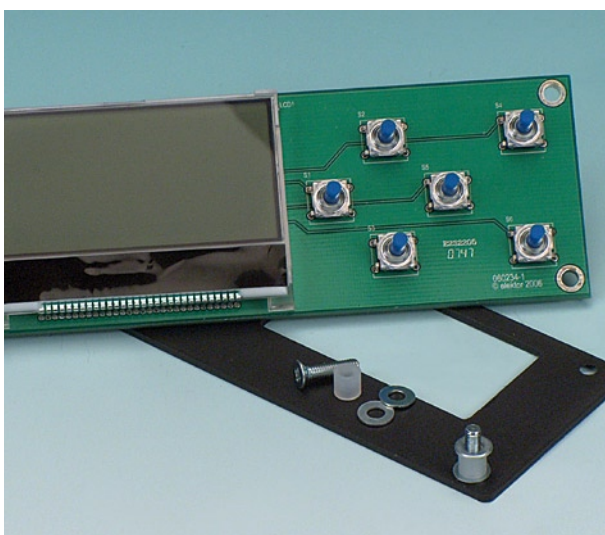

# paX: a Power Amplifier w

## Part 2: The voltage amplifier and input

Jan Didden

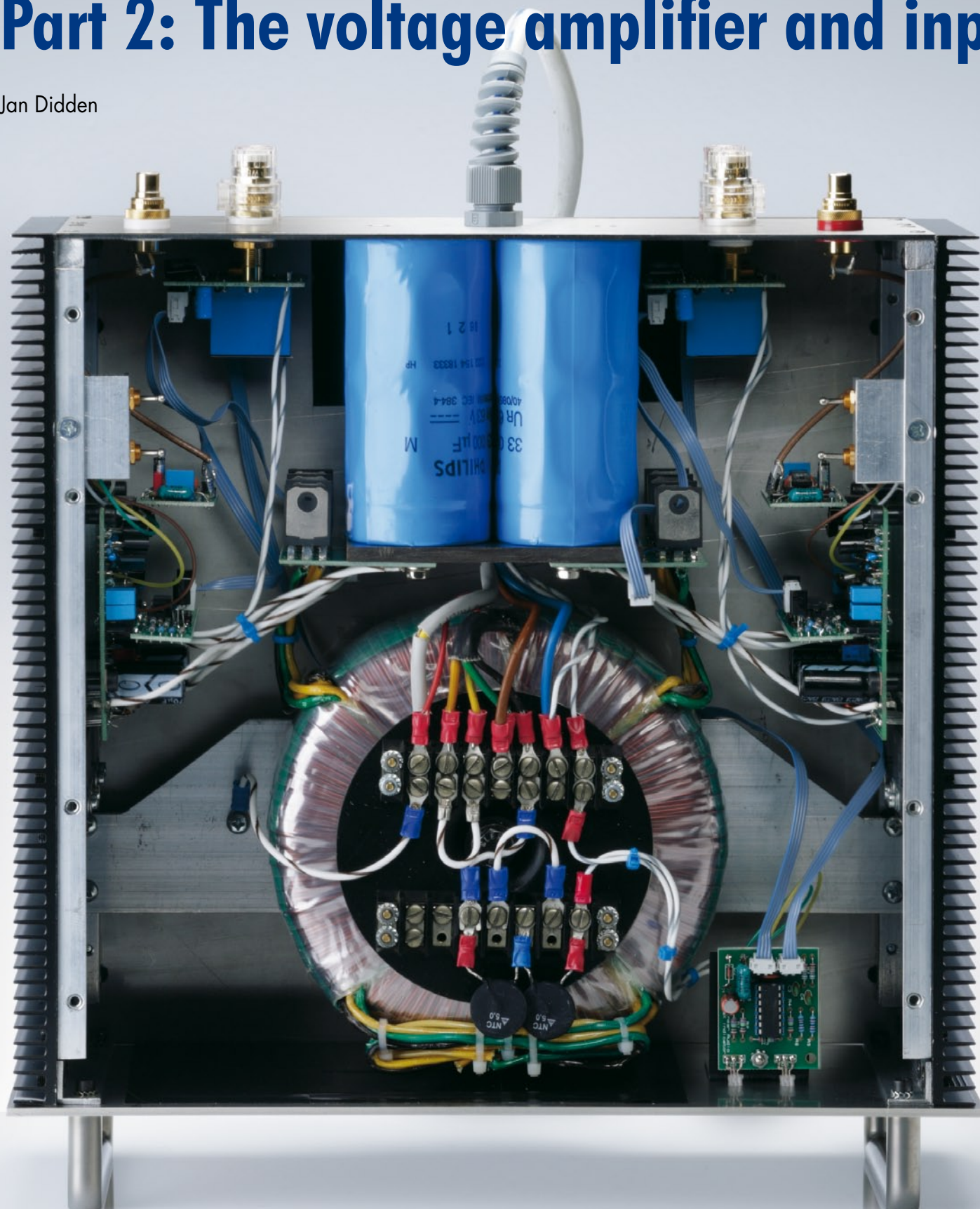

# With Error Correction

## buffer stages

Last month we discussed the principle of error correction and developed an error-correction power output stage. In this instalment we will use H.ec in a voltage amplification stage and present the complete amplifier.

Let's revert to the conceptual circuit of error correction as defined by Malcolm Hawksford, shown in **Figure 1a**. We know that if summing circuits S1 and S2 are unity gain summers, we get  $V_{out} = V_{in}$ , an ideal gain-of-one amplifier stage. But for our voltage amplification stage ( $V_{as}$ ) that drives the output stage, we need much more than unity gain. Common amplifier gains are around 26 to 30 dB, a gain of some 20 to 30 times. I like the lower value because it is better to have less gain in the power amp than to have a lot of unnecessary gain, only to turn down the volume control to get rid of it. It turns out we can use H.ec in voltage amplifiers quite easily if we insert an attenuator in the  $V_{out}$  sense leg, similar as we would do in a regular negative feedback circuit. We do that in **Figure 1b**. The sums are slightly different:

$$V_c = (V_{out}/\beta) - V_e,$$

but still

$$V_e = V_{in} - V_c.$$

Substitution and rearranging shows us that  $V_{out}/V_{in} = 1/\beta$ . So, if we make  $\beta$ , as is customary, from a simple resistive 1:20 voltage divider, we have now an amp with gain, linearised by error correction.

There is one other very important thing to note here. When we found that the open loop gain no longer is part of the amplifier transfer equation, we said that the gain of the amplifier block no longer has any bearing on the final result. That is true in theory, but not in practice. In the case of the power output stage, we said the gain is 'about 1'. A realistic value would be 0.98 at mid frequencies and light load, down to 0.95 at higher frequencies and higher loads. That means that the error correction circuit needs to add 0.02 to 0.05 times the

signal level to the input to straighten out the amp. Intuitively we feel that it is advantageous to have only small signals in the error correction circuitry that helps it to work linear and with low distortion. But in the case of the  $V_{as}$ , if the forward gain block would have only a gain of 1, the error correction circuit would have to add 19 times the signal level, and it would be much more difficult to design simple circuits that could handle those levels with high linearity. So, what we would want is to make the open loop gain of the  $V_{as}$  amplifier block such that the signal levels in the error correction circuit are mini-

bility wise, to have a lot of excess gain for the feedback loop to work with. Not so with H.ec, and a corollary to this is that your  $V_{as}$  can now be a very simple gain-of-20 amp.

### Voltage amplifier

The particular topology I chose is in **Figure 2**. It's very simple. U1 is a unity-gain buffer.  $V_{in}$  applied appears at the buffer output across R7. The output current through R7 comes from the supplies, of course, so we find a signal current  $V_{in}/R7$  in the current mirrors formed by Q1 and Q3. The quiescent

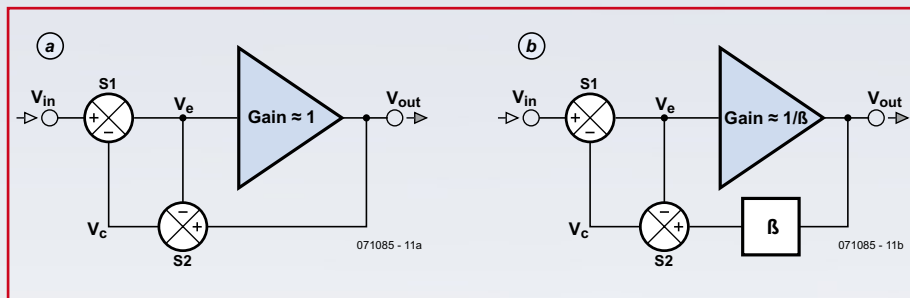


Figure 1. Basic H.ec topology for gain-of-1 stage (a) and arbitrary gain stage (b).

mized. This will be the case when the open loop gain is as close as possible to the closed loop gain. Then, there will be quite small differences between the input of the actual amplifier and the scaled down output (by  $\beta$ ), and that small difference then is the error signal. This limits the signal levels in the error correction circuit, greatly relieving the burden on the H.ec loop. In other words, you set the  $V_{as}$  open loop gain as close as possible to the required amplifier closed loop gain. This of course is totally at odds with what you would do for a negative feedback amp. There, you would try to get the highest open loop gain you can get away with, sta-

current for the buffer (I will tell you later which buffer type I used) happens to be about 7 mA. With an R7 value of 220  $\Omega$ , and a current of 14 mA peak-to-peak available, this buffer can handle a little over 3 V peak (about 2  $V_{RMS}$ ) before running out of class-A, which of course is good for linearity. With an amplifier gain of 20 that is enough to deliver 100 W in 8  $\Omega$ .

That same signal current in Q1 and Q3 is mirrored through Q2 and Q4, and flows through R16 to generate the output voltage. As a first approximation, because the same signal current flows through R7 and R16, and the signal across R7 is the same as  $V_{in}$ , the gain (open loop) of

this circuit is simply R16/R7 which is then set to 20. So, this is our  $V_{as}$  stage. But in the discussion in Part 1 we said that the amplifier output stage needs to be driven by a low (and constant) source impedance (ideally zero) for the output stage H.ec to work; so we add a low output impedance emitter follower stage to the basic  $V_{as}$  stage (Q10, Q9). This emitter follower stage is also biased at about 7 mA. Because of D3, the voltage drop across R6 and R8 is about the same, so if we chose  $R6 = R8$ , the same current flowing through Q2 and Q4 will flow through Q10 and Q9. D3 and D4 also provide a measure of temperature stabilization to the emitter follower output stage bias current.

Now that we have the main gain block for the  $V_{as}$ , we enclose it in an error correction loop similarly as we did with the output stage: **Figure 3**. There are a few things to note here. Although both the ec sense and the ec generation resistors are given as 'R', they are not equal. The sense resistance actually is the sum of resistor R plus the output resistance of the  $\beta$ -network ( $R11/R12$ ). It is the total resistance of R plus  $R11/R12$  that determines the error current into the CCII. That same current generates the ec voltage when flowing through the left side R, and these voltages should be equal, so similarly, the left side R is actually the series resistance of the nominal R and the output resistance of whatever will drive the  $V_{as}$ . We'll revert to this issue later. The second thing to note is that the gain of this amp is not strictly  $1/\beta$ . Terminal Y is a virtual earth point. To calculate the exact attenuation from  $V_{out}$  to the node R11, R12 and R, we need to account for the fact that for the attenuation, seen from the  $V_{as}$  output  $V_{drive}$ , R appears in parallel with R12. So, the attenuation, and thus the gain, is slightly higher than  $1/\beta$ . We need to consider both of these issues when we dimension the error correction sense and generation resistors. Just as with the output stage, we will use an AD844 for the ec circuit, while the buffer is used in the amplifier input stage to drive R7. The complete  $V_{as}$  circuit is shown in **Figure 4**. What we haven't mentioned yet are the diodes D9, D12, D13 and

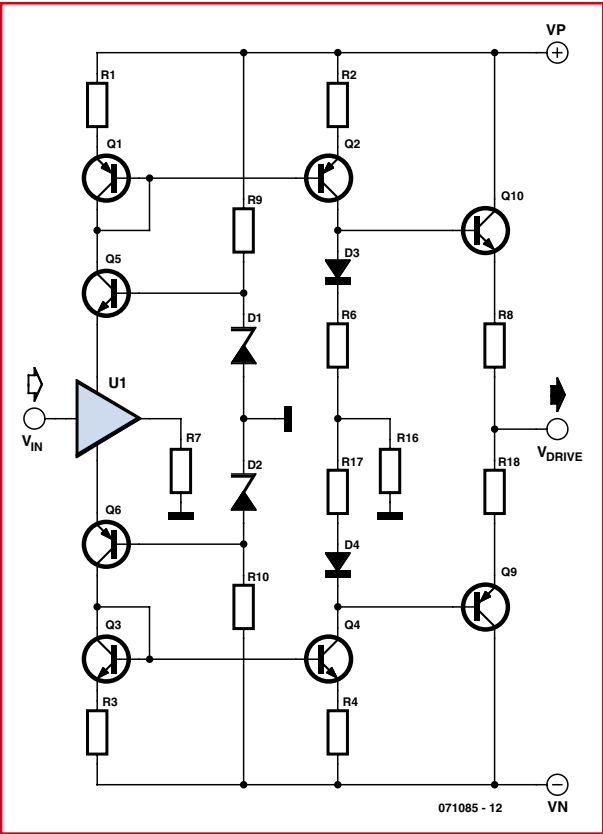


Figure 2.  $V_{as}$  basic circuit.

D14. In Part 1 of this article we have discussed what would happen if we overdrive the amplifier. The positive feedback loop is regenerative and will continue to increase the input signal until stopped by some physical limit like the supply voltage or current or voltage limitations in the circuit. (We also saw in part 1 that, because of the lower open loop gain, overdrive can be expected to be less severe; but we still need to deal with it). In the  $V_{as}$  stage, this is taken care of by the four diodes across the error correction generation resistor R29 (Figure 4). When

the amplifier is overdriven, the error correction current out of pin 5 of the AD844 CCII will increase considerably. This current will start to generate a large correction voltage across R29, to the point that the threshold voltage of the diodes is reached. At that point, the impedance of R29 collapses to just the dynamic diode impedance that is only a few tens of ohms. Further increases in the error correction current will not generate more error correction voltage and the positive feedback loop is broken. This makes the clipping clean, and recovery fast. But we run the risk that the diodes increase the distortion because they may already conduct a small current before the threshold, upsetting the error correction accuracy. It turns out that because of the very small error correction voltages across R29, this can be avoided. In **Figures 6 and 7** you see that if we would use a single pair of soft clipping diodes, the distortion starts to rise before maximum output. With the dual pairs, the difference is very small.

**Figure 8** shows this effect from a different perspective. The soft clipping diodes for the negative signal part have been temporarily removed so only the positive signal is affected. You can see that without the diodes, clipping recovery is delayed (negative part), while with the diodes (positive part) there is only a hint of delay.

Buffer stage and DC offset

All that is needed now for a complete amplifier is the input buffer and the DC offset servo. This is shown in **Figure 5**. Just as with the output stage, we need to drive the  $V_{as}$  input resistor, which develops the ec voltage (R29), with a low impedance source. You guessed it: we will again call upon the open loop buffer in an AD844 to drive the  $V_{as}$  from  $V_{in}$ . The signal enters the buffer in U2 through R51 and R33 at pin 5 and exits at pin 6. The enemy of your loudspeakers (and the amp as well) is DC offset at the output terminal. Most amplifiers have some sort of means to avoid that. In this amplifier, the output stage doesn't need any additional measures: the error correction ideally duplicates the driving voltage (from the  $V_{as}$ )

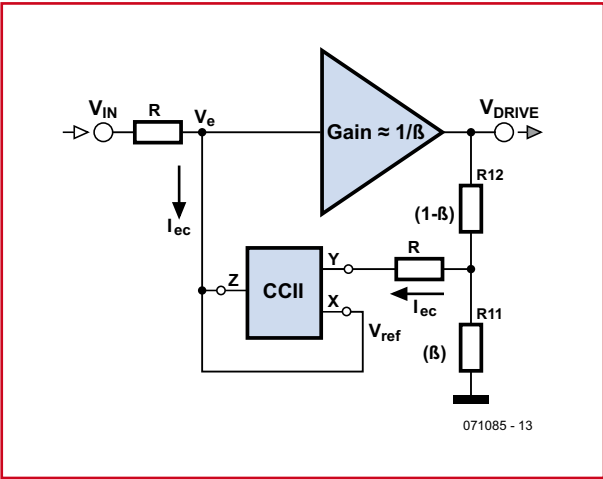


Figure 3. The CCII as the H.ec element for the  $V_{as}$  stage.

to the output terminal, with zero offset, although there will still be some offset from the error-correcting AD844, which will generate a small DC offset of a few millivolts. The only requirement is that the  $V_{as}$  has negligible DC offset. The  $V_{as}$  however has higher gain and will amplify its own AD844 offset with that gain. I decided to implement a DC servo to keep the  $V_{as}$  offset under control. The servo uses a low offset opamp, a TL051CP. We will use the uncommitted current conveyor in that input AD844 (U2, Figure 5) to couple the servo signal to the amplifier.

The way this works is as follows. Remember that whatever current flows in or out of the low impedance input pin 2, also flows (in opposite direction) out of or into pin 5. We also know that the voltage at pins 2 and 3 will track accurately. When we couple the servo signal to the reference input pin 3, it will cause a current in R50 to keep pin 2 at the same level. That same current will flow through R33 in R49 (and R1 if the source is DC coupled), and in this way the offset correction will be added to  $V_{in}$ . R49 assures that this current, which essentially is DC, can flow even if the  $V_{in}$  comes from a coupling capacitor. Finally, this input buffer and servo amp have their own  $\pm 15$  V supply from two zener diodes, D5 and D6. With this circuit, composite offset of the whole amp is just a few millivolts.

## Protection circuitry

There is a separate protection system for this amplifier that protects the speakers against DC output as well as the output devices against overload. It also provides delayed switch-on and immediate switch-off. This is described in a separate article in this issue.

## Power supply

The power supply for this amplifier should deliver about  $2 \times 44 V_{DC}$ . Although the output devices are rated for higher voltages, it is not advisable to increase the supply in trying to get more output power. The allowed dissipation at higher  $V_{ce}$  is much less than the rated DC dissipation due to secondary breakdown limitations of the SOA (Safe Operation Area). With loads that dip substantially below  $4 \Omega$ , even temporarily, the SOA may be exceeded and an output Darlington destroyed (or the protection activated). The supply

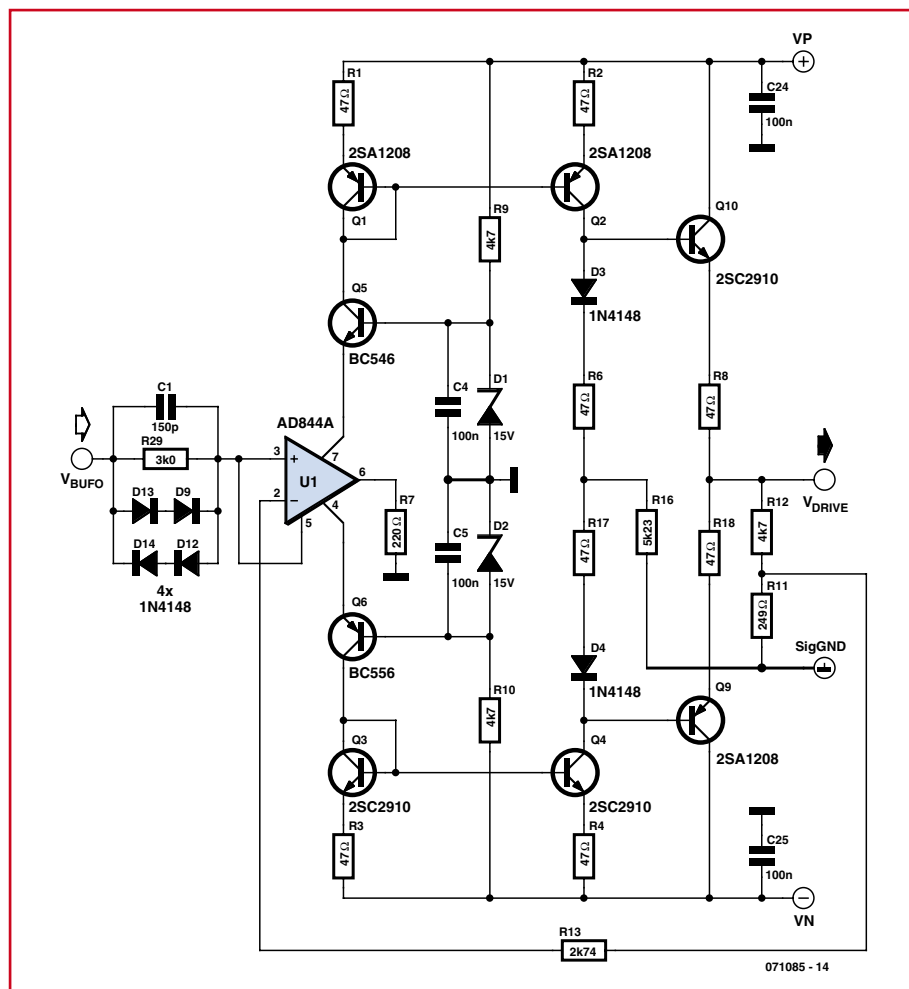


Figure 4. Full circuit of the H.ec  $V_{ds}$  stage.



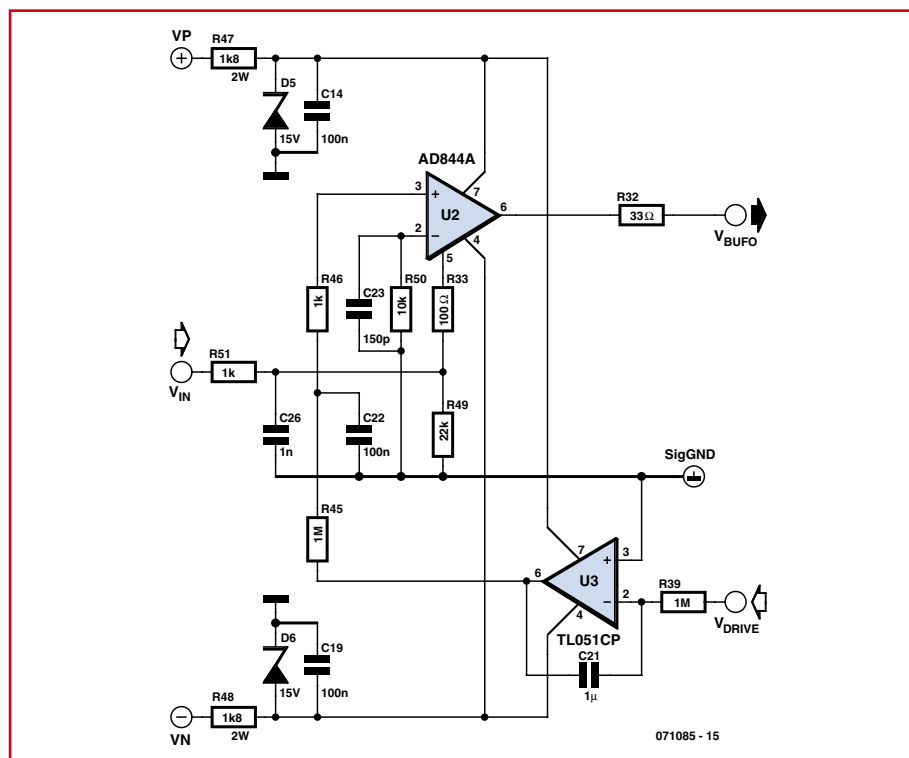


Figure 5. Input buffer and offset servo circuit to drive the  $V_{ds}$  stage.

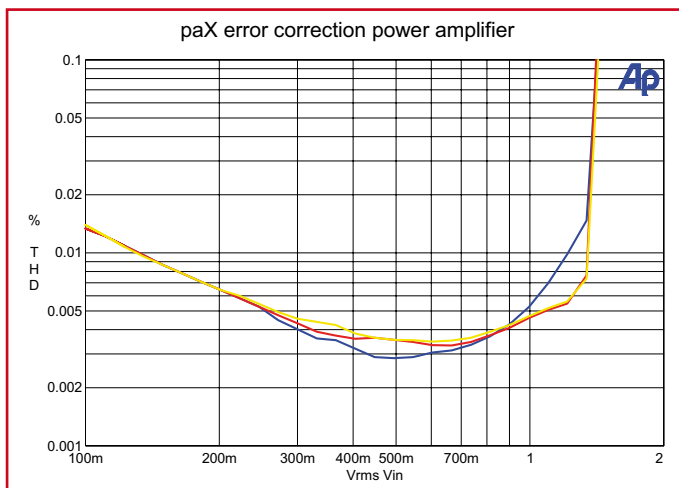

**Figure 6.** Amplifier distortion as a function of output level, with single diode (blue), dual diode (red) and without soft-clipper diodes (yellow).

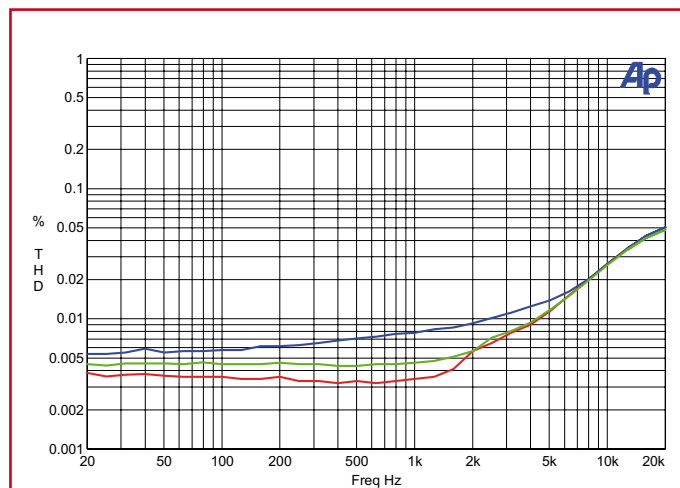

**Figure 7.** Amplifier distortion vs. frequency at 50 W in 8 Ω, with single diode soft clipper (blue), dual diode soft clipper (green), no soft clipper (red).

for the error correction circuit in the output stage is bootstrapped from the output; that part of the circuit can actually drive the output devices beyond the supply voltage. Consequently, it is the  $V_{as}$  that determines how close the output can get to the supply rails. Since the  $V_{as}$  will clip first, there is no clipping overdrive and overdrive delay in the output stage. The output can swing within a few volts of the supply, which is better than in most amplifiers (unless separate, higher voltage,  $V_{as}$  supplies are used).


The power supply for this amplifier is uncritical. The error correction not only corrects internal amplifier non-linearities, but also any power supply ripple or noise that makes it into the circuits. (The supplies for the error correction AD844's is stabilized separately with zener diodes). Therefore, a classic rectifier-and-reservoir capacitor supply delivering  $2 \times 44 V_{DC}$  under load is sufficient for about 100 W in 8 Ω, 200 W in 4 Ω. The power supply circuit details are given in **Figures 9 and 10**. For a stereo version, a 300 or 400 VA transformer should be sufficient; after all, you will not drive both channels at full power for a long period (except maybe on the test bench). You can use the common transformer with a centre-tapped secondary, but other configurations can also be used. One nice option for a stereo amp is to use two completely separated supplies, each with a 250 or 300 VA transformer. That would make

it easier to maintain strict star point grounding.

It is important to get the grounding right. Ground currents back to the supply from the speaker, as well as from the reservoir electrolytics, can be quite large and have all kinds of ripple and noise. Such ground currents generate voltages across the ground return wiring. If the ground for the signal is connected to this ground wire at another point, you have effectively created a small ripple signal that appears in series with the input signal. This may seem far fetched, but with very low distortion and very clean amplifiers, even a few mV of these noise signals can be enough to ruin the linearity and distortion figures of an otherwise very good amplifier. Usually one tries to prevent this by using a star ground: All ground returns come together at a

single point, and no signal return runs through the same ground wire with another return loop. If you look at the amplifier PCB layout you see that the power connections get to a central star point. On the PCB itself, care has been taken to do the same. There are two or three separate traces that bring the returns for the regulator zener diodes and the decoupling capacitors to the same point. The signal returns from the input network, the gain setting resistors R7, R16 and the error attenuation network R11, R12 are also brought to this point separately. All return wires from the supply, the transformer and the speaker are returned to the star ground. The signal grounds in the amplifier are then returned to this point via a low-value resistor R28, which is then by definition the 'clean' ground point (pad J1 on the PCB is the clean ground and should be used as 'ground' for measurements as well). Any error voltages generated by ripple and pulsating currents in the ground wires cannot end up in the signal, except through radiation. This in turn we can minimize by making all high-current wires short and as far away from sensitive signal areas as possible.

Finally, the rectifier diodes should be types that recover quickly from voltage reversal when switching off, and do so 'softly', that is, without very sharp current steps. Diodes that take a long time to reverse themselves and in the process generate sharp current steps may cause high-

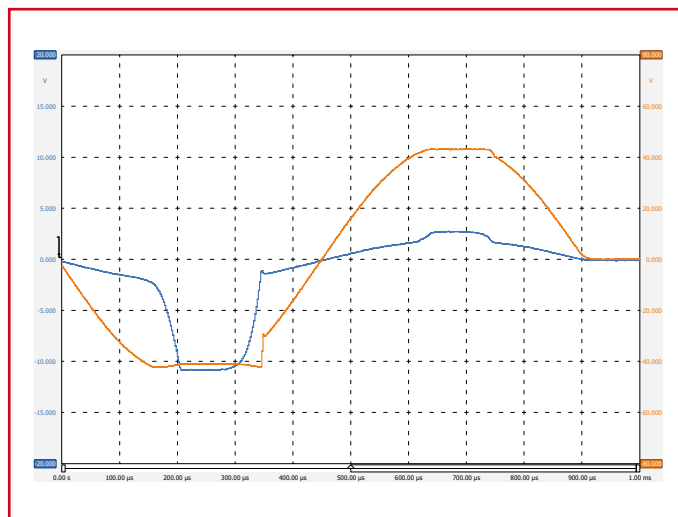

**Figure 8.** Error correction current (blue) and amplifier output clipping (amber) with soft clipper (positive signal) and without soft clipper (negative signal).

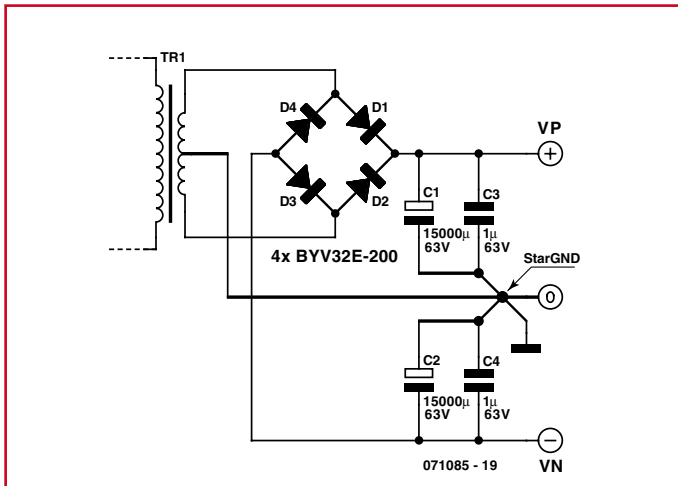


Figure 9. DC power supply. Diodes are paralleled, dual, fast, soft recovery 3-pin TO220 types.

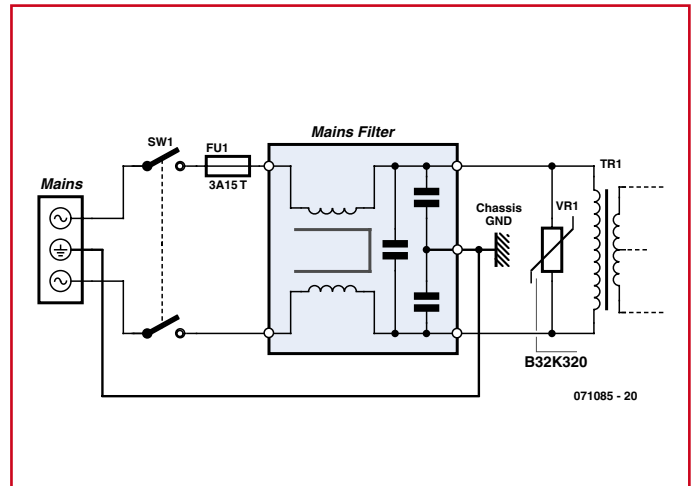


Figure 10. Mains wiring for the power supply, mains filter, overvoltage clamp and fuse.

frequency noise that is difficult to filter out. Fast, soft recovery types don't need capacitors or snubbers; indeed, such capacitors would only increase the transmission of mains-borne noise to the amplifier. My recommendation is to use Philips BYV32E-200 diodes. These are TO220 dual types with a common cathode; the two diodes should be paralleled. They have a relatively low threshold voltage, and are quite inexpensive. They don't need to be heatsinked so they can be put on a PCB in free air. For the reservoir capacitors, a minimum of 15,000  $\mu\text{F}$  should be used per supply polarity. 63 V rating is adequate.

A mains filter as shown in **Figure 10** should be used to keep out high frequency noise and switching pulses riding on the mains. Good mains filters are not cheap but worthwhile; use a type with at least 6 A rating. Ground the filter ground lug as well as the mains safety ground wire to the chas-

sis only. Use a slow-blow fuse of 3.15 A for a stereo version, larger if you use larger reservoir capacitors. A 275 V<sub>AC</sub> varistor clamps any high-level pulses that make it out of the filter.

### Conclusion

So, there you have it, a complete, high quality yet simple error correction power amplifier. The parts list shows all components for one (mono) amplifier. Note that the values of C11, C12, C17 and C18 (output stage) were given as 330  $\mu\text{F}$  in Part I but 470  $\mu\text{F}$  fits on the PCB so these should be used. A separate *Construction Guide* is available as free download from the Elektor website as archive file # **071085-w.zip**.

Although harmonic distortion measurements do not always correlate with sound quality, they do give an indication of linearity and behaviour of an amplifier. Therefore, a few performance curves are given in Figures 6 and 7. If

you work in a step-by-step fashion as described in the Construction Guide, checking your work after each major part, it will help to avoid errors and, if errors are made, to quickly isolate and fix them. Also check on my website for any last-minute information, additions or corrections.

This is not a very difficult project but it provides you with an excellent amplifier, which reproduces your source music faithfully, adding nothing, taking nothing away. This amplifier is stable and will happily drive a wide range of different speakers. In short, an amplifier that will let you enjoy your music for many years to come!

(071085-I)

### Additional information

[www.linearaudio.nl](http://www.linearaudio.nl)

**Availability of construction kits:**  
[www.pilghamaudio.com](http://www.pilghamaudio.com)

— Advertisement

## ElmScan 5 ScanXL

Elmscan 5 is an advanced diagnostic package for use with EOBD compliant vehicles.

- Read and clear trouble codes
- Access up to 192 engine parameters
- Advanced Graphing and Data Logging
- Built-in Dyno and Drag Strip feature
- And much more...

**For under £100!**

[www.scantool.net](http://www.scantool.net) • [sales@scantool.net](mailto:sales@scantool.net)



Order online today!


**ScanTool.net**  
Inexpensive solutions for OBD-II diagnostics

# Protection System for Power Amplifiers

## An indispensable companion for the paX amplifier

Jan Didden

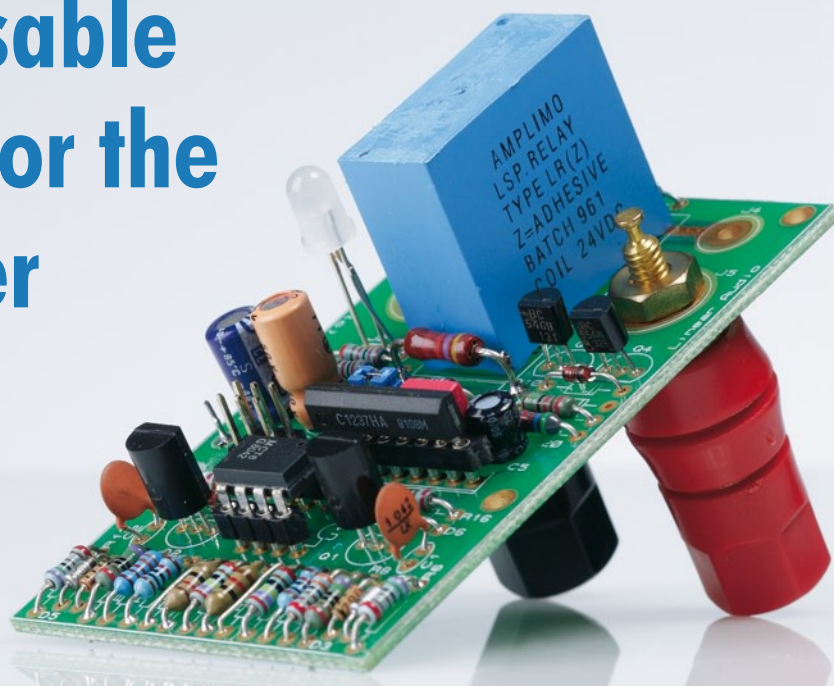**In Part I and part 2 about the paX amplifier we developed a complete error-correction power amplifier. In this accompanying article a protection system is described that's constructed on a separate small circuit board for mounting directly on the speaker binding posts. We will also discuss the Safe Operation Area for the output devices and how it is modelled in the protection system.**



A good protection system for an audio amplifier has two important tasks: speaker protection and amplifier overload protection. Speaker protection concerns a possible excessive DC voltage at the amp output due to either excessive ultra-low frequency signals, or from a circuit failure inside the amp. By the way, you can also get excessive DC output if you have a DC coupled power amp and your preamp gives out DC. If you go on tour with your amp, it would be wise to insert

– even temporarily – some input coupling caps.

There are many convoluted circuits to disconnect the speaker from the amp through a high-power relay in case of significant DC offset at the output. These circuits often do double duty in delaying the closing of the relay until after the turn-on transient, as well as immediately opening the relay when power is switched off – again to avoid transient thumps in the loudspeaker.

I used a low-cost, purpose-designed, but not too well known IC: the uPC1237 from, among others, NEC. The NTE7100 from NTE Electronics, is pin- and functionally compatible. It's an 8-pin single-in-line (SIL) chip with all the functions mentioned above. The datasheet gives the formulas for calculating the component values. It can handle two channels for a stereo amp, but I used one chip per channel to make it easier to construct the amp as dual mono.

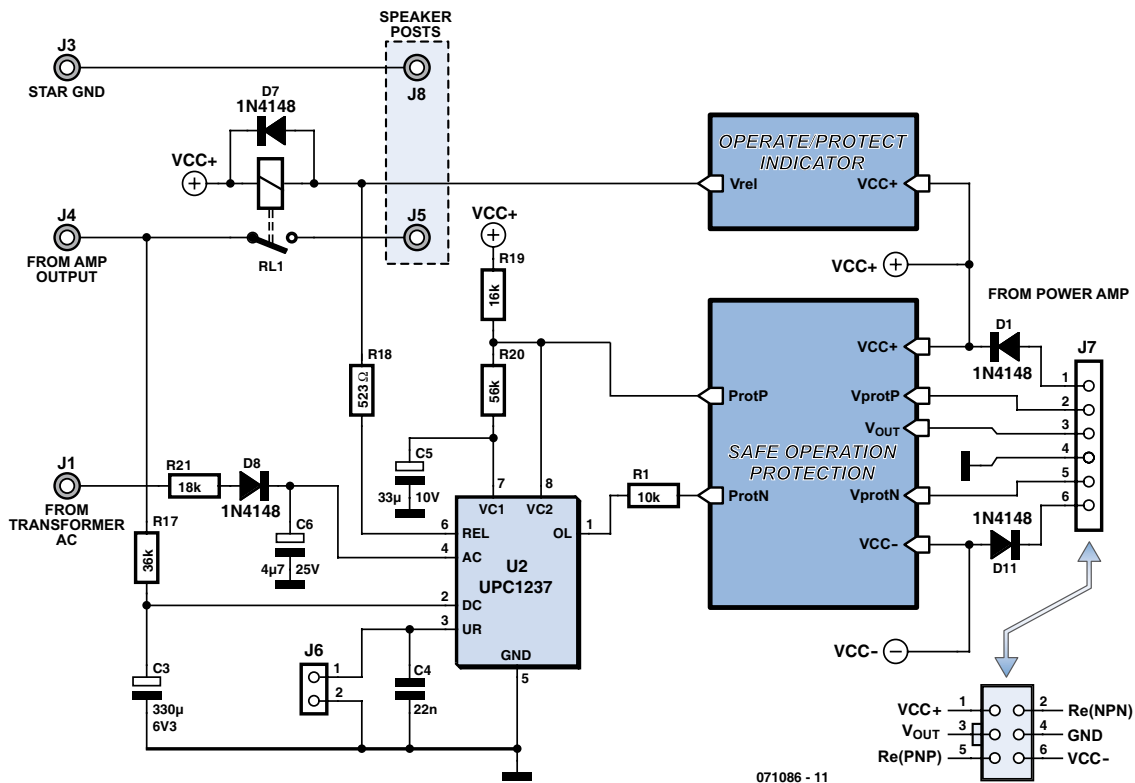


Figure 1. Overall protection system.

For the speaker relay I used a little-known device specially designed for this function and sold by the Dutch company Amplimo. The relay has two parallel tungsten 100 A contact and a smaller gold contact pair. When the relay closes, the tungsten contact closes first, and is then bridged by the gold contact. The reverse takes place when opening the relay.

## Circuit diagrams

The overall protection system is shown in **Figure 1**. The blocks for the Indicator and the Safe Operation Area protection will be described later. The uPC1237 has an internal 3.4 V shunt regulator at pin 8, and the supply current is provided by R19 and R20. The relay switching output (pin 6) drives the relay through R18. Jumper J6 sets the circuit operation. If J6 is closed, the circuit becomes 're-entrant': if there is an error input, the relay falls off, and after a short delay is activated again. If, at that point, the error has disappeared, the relay stays activated, if not, it falls off again and the cycle re-

peats. If J6 is not closed, the relay is deactivated when an error is present and you have to switch the power off and on again to reset the circuit.

### DC offset shut-off

Pin 2 of U2 is the DC offset input. AC on the amplifier output signal is removed by R17-C3 and the DC offset is sensed. Although the uPC1237 only has a unipolar supply (the amplifier's VCC+), pin 2 does accept bipolar signals. The calculations are a bit complex because the internal positive and negative thresholds are not equal. It is all explained in the datasheet. With some care you can set the threshold for positive and negative offset to the same value at  $0.6 V_{DC}$ . These values are set by R17 and C3 as shown in **Figure 1**.

### Switch-on delay

You will also see that a sample of the AC from the supply transformer is connected to the uPC via R21 and D8 to C6. This part of the circuit will delay the loudspeaker switch-on after a power up to make sure the amp has stabilized and there are no switch-on

thumps. When the power is turned off, this signal will disappear immediately, before the supply capacitors have a chance to discharge. This way the speaker relay will be opened before the turn-off thumps occur.

### Safe Operation Area

The second main part of the protection system is to guard the output devices against excessive low impedance loads and short-circuits. Michael Kiwanuka has written a very informative article on Safe Operation Protection in audio power amplifiers [1]. My own protection circuit is different, but was inspired by Mike's design and has many things in common with it. **Figure 2** shows the circuit. The circuit receives two types of information from the power amp: the  $I_c$  in the output devices through  $V_{protP}$  and  $V_{protN}$  (via connector J7 in **Figure 1**): this actually is the voltage across the emitter resistors. Secondly, through the components connected to the supply and  $V_{out}$  a voltage is developed that represents  $V_{ce}$  of the output devices. (There is a separate part to this article that explains the circuit in detail and how

# Calculating and setting up the protection system

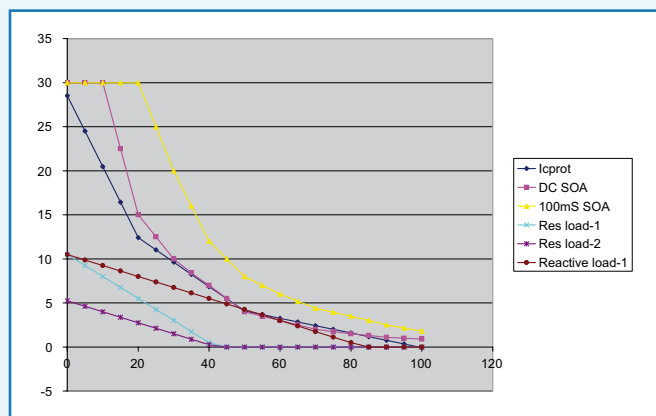


Figure 1. SOA, load lines and protection locus. See text for explanations.

The paX amplifier uses Safe Area Operation (SOA) protection. In this section we will address the specific design equations and how to develop the circuit values for the SOA part.

Figure 1 shows the various curves that we need to develop the SOA protection for two pairs of output devices.  $I_c$  (A) is on the vertical scale,  $V_{ce}$  (V) is on the horizontal scale. When  $V_{ce}$  is zero, it means that  $V_{out}$  is equal to  $V_{supply}$ . In practice, there will always be a few volts  $V_{ce}$  remaining at maximum output, but we will disregard that for the moment. The cyan curve shows the safe combinations of DC  $I_c$  and  $V_{ce}$  for two parallel STD03 Sanken Darlington devices used in this amplifier. The yellow curve shows this for loads lasting no longer than 100 ms. That means that combinations of  $I_c$  and  $V_{ce}$  that fall below and to the left of the curve, are safe, but as soon as the curve is crossed, the protection system should activate. Since music is impulsive and not DC, one could argue that protection for the yellow curve would be sufficient, but if we use the cyan curve we have an additional safety factor and we also are protected against DC shorts.

Figure 1 also shows some load lines, which are combinations of  $I_c$  and  $V_{ce}$  required to drive a (resistive) load, assuming  $\pm 40$  V supplies. The lower one, in pink, is an 8  $\Omega$  load, the light blue one is 4  $\Omega$ . For example, in the 4  $\Omega$  case, we see that when  $V_{ce} = 0$ , the output voltage is the supply voltage (40 V in this case) and thus  $I_{out}$  in 4  $\Omega$  is 10 A. The brown curve is also for 4  $\Omega$  load, but now with a maximum reactive component of 90° phase shift. This is a particularly mean load. At  $V_{ce} = 40$  V we are exactly between the supplies (assuming a  $\pm 40$  V supply) with  $V_{out} = 0$ . With  $V_{ce} = 60$  V,  $V_{out}$  is actually -20 V negative but  $I_c$  is still positive (about 3 A). That means that the upper

transistor (N device) sources current even with a negative  $V_{out}$ ! Under these circumstances (which can happen easily with real speaker/crossover loads) quite high  $V_{ce}$  to  $I_c$  combinations can occur although the device dissipation is very much limited as shown in the SOA curve. For instance, in this example, at  $V_{ce} = 60$  V and  $I_c = 3$  A, allowed dissipation (per device!) is 90 W, although the data sheet calls this a 160 W device.

So, we can put in a simple current limiter that follows, say, the 4  $\Omega$  complex load line. But then we cannot use the large safe area, especially at low  $V_{ce}$  and  $I_c$  between 10 A and 30 A, which may come handy with speaker loads that have low impedance dips. It is clear from Figure 1 that a simple current limiter is not enough. What we want is to 'model' the cyan DC curve in our circuit. This can be done with some non-linear circuit elements, and my target SOA protection curve is shown in dark blue. It has three inflexion points at  $V_{ce} = 20$  V and  $V_{ce} = 50$  V.

The way I implemented this is shown in **Figure 2**, which is the positive half of the full circuit given in Figure 2 of the article about the protection circuit. (The negative part works similarly and will not be discussed). There are 4 distinct points on the blue target curve. The first and last points are defined by  $V_{ce} = 0$  and  $I_c = 0$  respectively. The other breakpoints are at  $V_{ce} = 20$  V and  $V_{ce} = 50$  V. These two breakpoints are caused by diodes D3 (for 20 V/13 A) and D2 (for 50 V/5 A). Remember, all currents are for two parallel devices! At each breakpoint, the diode(s) start to conduct and shunt current away from R14 and R4, so that Q1 conducts later.

To calculate the component values for this rather involved circuit, we start with the simple part: if  $V_{ce} = 0$ , the maximum allowed  $I_c$  is 30 A for two output pairs. Also at this point,  $V_{out} = V_{CC+}$  so there is no current coming from R6/R5. The voltage to turn on Q1 comes exclusively from the voltage drop across the output devices' emitter resistors, through Rs. We need to ensure that at 30 A, the voltage at Q1 (base) is approximately 0.65 V. Although there are two emitter resistors and two Rs resistors in the circuit, they are in effect parallel, so we will use from now on  $R_e = 0.11 \Omega$  and  $R_s = 50 \Omega$ . With 30 A through the parallel value of  $R_e$ ,  $V_{Re} = 3.3$  V, which is attenuated through Rs and R4:  $12/(50+12) \cdot 3.3 = 0.64$  V — close enough.

Now it gets interesting. Lets move to the breakpoint where  $V_{ce} = 20$  V. The allowed  $I_c$  is (cyan curve) about 13 A. We assume some values and then calculate the rest:  $R_s = 100 \Omega$ ,  $R_4 = 12 \Omega$ ; we set R14 to 270  $\Omega$ . Let's disregard D2/R8 and D3/R7 for the moment; we just need to be sure later that that was justified (that the diodes don't conduct at up to  $V_{ce} = 20$  V).  $V_{ce} = 20$  V and  $I_{cmax} = 13$  A gives an effective  $V_s$  of  $V_s = R_4/(R_s+R_4) \cdot (R_e \cdot I_c)$ , which, with the given values, is 0.28 V. We need  $V_b = 0.65$  V, so the current from R5 should gener-

I calculated the various component values).

The purpose of the SOA protection is to limit the combinations of  $V_{ce}$  and  $I_c$  for the power devices to a safe value. Normally, such a protection circuit would be arranged to take away the drive from the output driver transistors to limit the available output current. The protection transistor (Q1 or

Q2, Figure 2) collector would normally be connected to the base of the (pre) driver transistor in the output stage. Q1/Q2 turns on when its  $V_{be}$  exceeds about 0.65 V, shunting driver base signal away. But in my experience, even with a  $V_{be}$  of only a few 100 mV, the protection transistor starts to influence the driver base signal, resulting in increased error correction and increased distortion.

For this reason I decided to make this an on/off protection circuit: the protection transistors drive the 'overload' pin (1) of the uPC1237 through the dual optocoupler U1, an MCT6. If overload occurs, pin 1 of the uPC is set high via R1 (Figure 1) and the uPC opens the speaker relay. I have the uPC set for auto re-entry by jumpering J6: in this mode, the speaker relay will be periodically closed

ate the remaining 0.37 V across R14. So this current needs to be  $I_{R5} = 0.37/270$  or 1.37 mA, which also flows through R6 of course. With a  $V_{ce}$  of 20 V (we disregard the small  $V_{ce}$  loss across  $R_e$ ), that would make  $R5+R6 = (20-0.65)/1.37 = 14.1$  k $\Omega$ . It doesn't really matter how we split up the total value (it does matter for the other values of course, but not for the functioning), so let's make them equal:  $R5 = 7$  k $\Omega$  and  $R6 = 7$  k $\Omega$ .

At this breakpoint,  $V_{ce}=20$  V, diode D3 should be on the verge of conducting, so D3 should be a zener equal to the value of  $V_m$ . Since we have 1.37 mA through R6,  $V_m = 20 - (1.37 \cdot 7) = 10.4$  V, making D3 a 10 V zener.

Now let's move to the next point, 50 V/4 A. Analogous to the 20 V/13 A point, D2 should be on the verge of conducting so we can disregard it, and R8, for now.

As before we calculate the contribution of  $I_c$  at  $V_s$ :  $V_s = 12/(12+50) \cdot (0.11 \cdot 4)$  which is 85 mV, so the  $V_{ce}$ -derived current from R5 and R6 should add  $0.65-0.085 = 0.565$  V at  $V_b$ , therefore

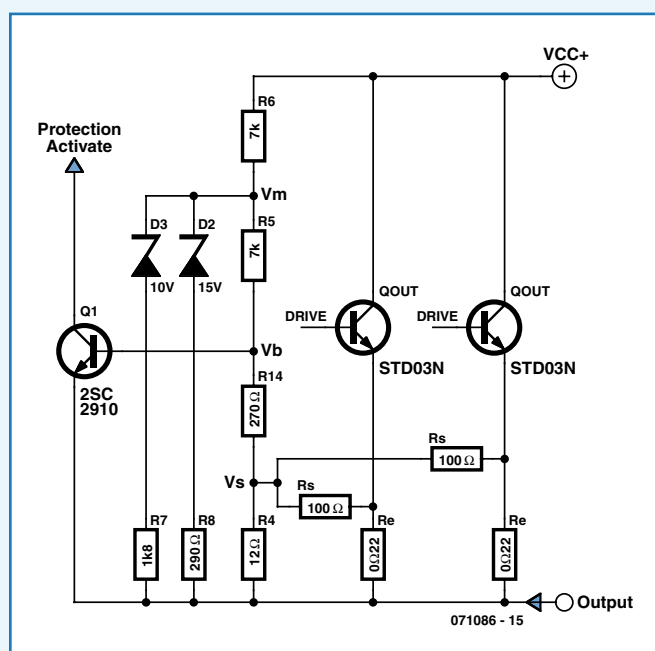


Figure 2. SOA protection circuit.

$I_{R14} = 0.565/270 = 2.1$  mA. This 2.1 mA also flows through R5 and R6, so  $V_m = 0.65 + (2.1 \times 7) = 15.35$  V. (This of course means that D2 should be a 15 V zener, and we will use that later).

With  $V_m = 15.35$  V and D3 a 10 V zener as calculated above, we

have 5.35 V across R7. The voltage across R6 now is  $V_{R6} = 50-15.35 = 34.65$  V, so  $I_{R6} = 34.65/7k = 5$  mA. Since 2.1 mA flows through R5, 2.9 mA must flow through R7 with 5.35 V ( $V_m-10$  V from D3) across R7, so  $R7 = 1.8k\Omega$ .

Moving on now to 100 V/0 A, it gets pretty boring:

$I_c=0$  so there is no contribution from  $R_e$  to  $V_s$ , and the  $V_{be} = 0.65$  has to be generated by the current through R5 and  $R14+R4$ , so  $I_{R14+R4} = 0.65/282 = 2.3$  mA. This current also flows through R5 so  $V_m = 2.3 \cdot 7 + 0.65 = 16.75$  V.

The current through R6 is:  $I_{R6} = (100-16.75)/7 = 12$  mA, so the excess of 12 mA-2.3 mA = 9.7 mA needs to be shunted away through D2/R8 and D3/R7.

$V_{R7} = (16.75-10) = 6.75$  V with R7 at 1.8 k $\Omega$  so  $I_{R7} = 3.75$  mA, which sets  $I_{R8}$  to  $9.7-3.75 = 6$  mA.

$V_{R8} = 16.75-15 = 1.75$  V so  $R8 = 290 \Omega$ .

So, there you have it, but it would be nice if there was some way to verify this before committing solder (and parts). We have disregarded several things, for instance the loss of  $V_{be}$  for  $V_{ce}$  and several roundings in the calculations. I have developed a spreadsheet to try to double check all this (available on [www.linearaudio.nl](http://www.linearaudio.nl) and [www.elektor.com](http://www.elektor.com)). It works backwards from what we just did: using the component values in the circuit, it calculates at each  $V_{ce}$  the  $V_b$  contribution from the current through R5, and then finds the  $I_c$  that would add just enough voltage across  $R_e$  to make  $V_{be} = 0.65$  V. Plotting those pairs of  $V_{ce}$  and  $I_c$  then should give us the actual (blue) SOA curve we wanted in the first place. What we see is that the spreadsheet shows reasonable correspondence to our values, but there are some deviations. The reason is that once I had the spreadsheet, I 'played' with the component values to get the best fit to the SOA curve, or to get 'nice' values for parts. I used a  $V_{CC}$  of 44 V and a  $V_{ce(min)}$  of 2 V in the spreadsheet. Also, manipulating the R5 and R6 ratio lets you home in on standard zener values. The way to do that is to use Excel's solver to find the ratio of R5 to R6 that results in say  $D3 = 12$  V. Some more playing then gets you to  $D2 = 18$  V. In the end, I used the values from the spreadsheet in the actual circuit as given in the main article. Since we stayed on the safe side with the blue protection curve, small deviations won't cause disaster. Just try it, you can't break anything, but don't mess with the formulas unless you know exactly what you're doing!

I developed this spreadsheet for this particular application and did a fair amount of checking, but I cannot guarantee that it is without errors. If you find any, please let me know and I will update it, giving credit where it is due, of course.

It is not so easy to test the accuracy of such a protection system in real world, and mistakes could be expensive. So this double check of calculating the values and then working backwards to verify them is important to gain confidence in the circuit.

to see if the overload still exists, and if so, it is opened again immediately. It can be argued that the protection system should work by limiting the output in case of overload and not by disconnecting the speakers. I would agree that for PA duty this would be preferred, but for home use it is a very minor nuisance, if at all. But doing it this way prevents influencing of the music signal by the circuit

when there is no need for protection activation. Having used this amp for about a year now, I have never seen the protection system disconnect the speakers, except in one case where I had a problem with a balanced cable which put a signal with 2.5  $V_{DC}$  on the amplifier input. I immediately heard the on-off cycling of the amplifier, so I switched it off and managed to find the problem. After solving the

problem all was as it should be. So, for me, this works quite well.

### Status indicator

Then, lastly, there is a small bi-stable circuit that takes the relay drive voltage to drive a bi-colour LED which you can place on the front panel. The LED will be one colour when the amplifier is in turn-on delay or in protection and another colour if the amplifier is oper-

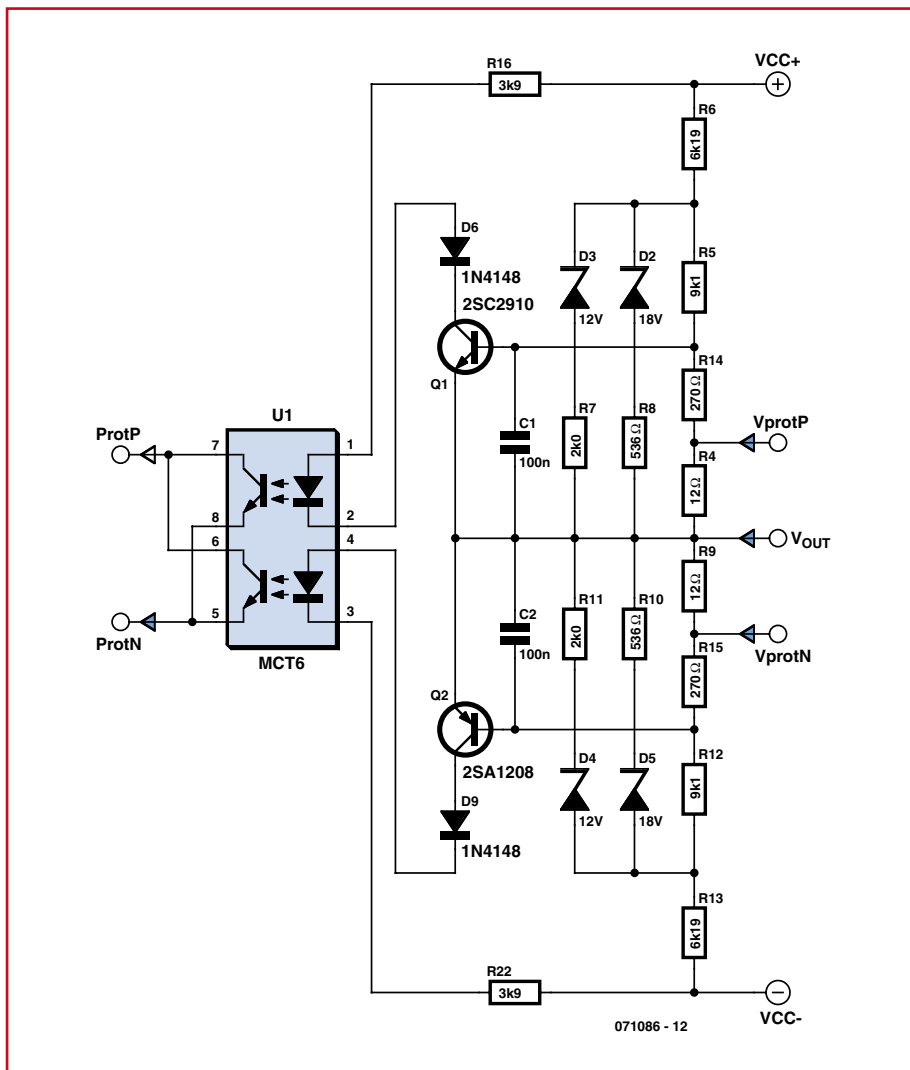


Figure 2. Safe Area Protection system.

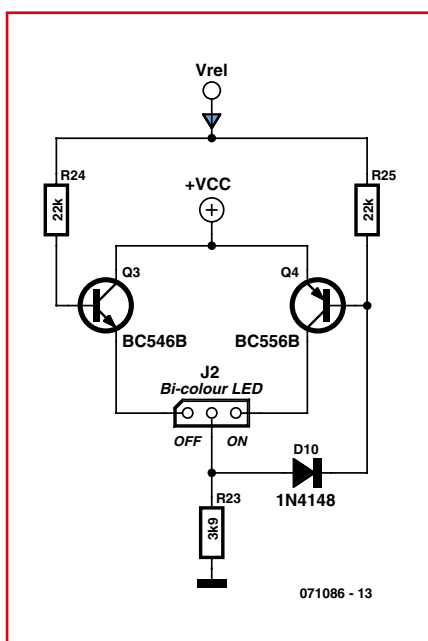


Figure 3. Status indicator.

point) to the protection board at J1 as shown. Don't connect a speaker yet, and don't yet connect the speaker wire from the amp to the protection circuit. Now, when you switch on the amplifier, you should hear the relay pull in after a few seconds. If you find it too fast, you can increase C6 for a longer delay. If you switch off the amp, the relay should immediately open again.

Next we will check the DC offset protection. Temporarily connect a resistor of 100 k $\Omega$  from the positive or the negative supply to the speaker input point on the protection board (J4). The relay should deactivate. Check this with both J6 set and removed to verify correct operation.

Then, install all components for the status indicator in Figure 3.

The PCB has labels 'ON' and 'OFF' at J2. That indicates which pin will be active at which status. If you use a red/green LED you would connect the RED pin to J2/OFF and the GREEN pin to J2/ON. You may want to repeat one of the tests described above to verify the correct operation of the status indicator.

The last part will be to complete the Safe Operation Area (SOA) protection components. Put all remaining parts on the protection board. Connect the flat cable, and connect the speaker output from the amplifier (Amplifier J3 to o/p board J4), as well as the star ground wire (o/p J3 to supply star ground).

ating normally. This circuit is shown in **Figure 3**. All components shown in figures 1, 2 and 3 are on the output/protection (o/p) board shown in **Figure 4**.

## Construction

Before building the o/p board, first complete the amplifier. We need the amplifier to test the o/p board. The o/p board can be populated first with the DC and delay circuitry around U2. Start with the components shown in Figure 1.

Next, construct the 6-wire flatcable as shown in Figure 1 in the Construction Guide. Be sure to orient the notches in the 6-pin headers exactly as shown! Connect the two boards with the flatcable, again noting the header notch position as indicated on the PCB silk screen. Also connect one side of the power transformer secondary (the AC

Switch on the amplifier and verify that it works normally. Then, to simulate an overload situation, connect a resistor of 10 k $\Omega$  between the positive supply and the node Q1(base)/R14/R5/ C1 and verify that the relay falls off. Do the same with the negative supply and the node Q2(base)/R12/R15/C2.

Note: If you do not mount the o/p board directly on the speaker output posts, you can connect the speaker return wire directly from the output post to the supply star ground without going through the o/p board. The loudspeaker's 'hot' connection then goes from the o/p board J8 to the output post.

## Stand-alone!

This article focused on using this o/p board with my 'paX' amplifier. But you can use it with any amplifier, provided you adjust the SOA circuit values as re-

## COMPONENTS LIST

### Resistors

(0.25W metal film)

R1 = 10k $\Omega$   
 R4, R9 = 12 $\Omega$   
 R5, R12 = 8k $\Omega$   
 R6, R13 = 6k $\Omega$   
 R7, R11 = 2k $\Omega$   
 R8, R10 = 560 $\Omega$   
 R14, R15 = 270 $\Omega$   
 R16, R22 = 3k $\Omega$   
 R17 = 36k $\Omega$   
 R18 = 510 $\Omega$   
 R19 = 16k $\Omega$   
 R20 = 56k $\Omega$   
 R21 = 18k $\Omega$   
 R24, R25 = 22k $\Omega$   
 R23 = 3.9k $\Omega$  1W

### Capacitors

C1, C2 = 100nF ceramic  
 C3 = 330 $\mu$ F 6.3V  
 C4 = 22nF ceramic  
 C5 = 33 $\mu$ F 10V

C6 = 4 $\mu$ F 25V

### Semiconductors

D1, D6-D11 = 1N4148  
 D2, D5 = zener diode 18V 0.5W  
 D3, D4 = zener diode 12V 0.5W  
 J2 = dual colour LED  
 Q1 = 2SC2910  
 Q2 = 2SA1208  
 Q3 = BC546B  
 Q4 = BC556B  
 U1 = MCT6 (Fairchild)  
 U2 = UPC1237 (NEC) or NTE7100 (NTE Electronics)

### Miscellaneous

J6 = header 2 x 1 pin  
 J7 = 2 x 3 pin DIL flatcable header  
 RL1 = Amplimo LS relay  
 DIL socket 2 x 4  
 SIL socket 1 x 8 pin  
 PCB, # 071086-1 from the author or [www.thepcbshop.com](http://www.thepcbshop.com)

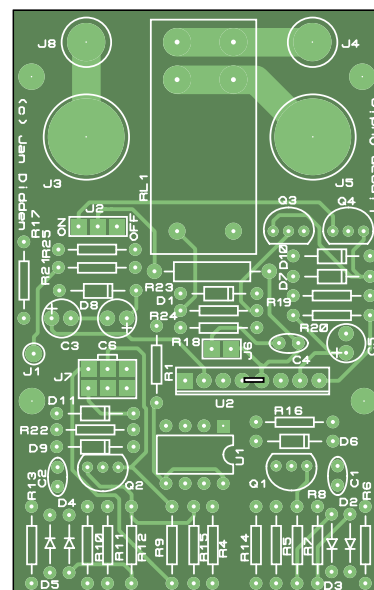



Figure 4. Component placement of the double-sided PCB for the o/p board.

quired, as described separately. The inset in Figure 1 shows the connections you need to make from your amplifier to the o/p board through J7.

(071086-1)
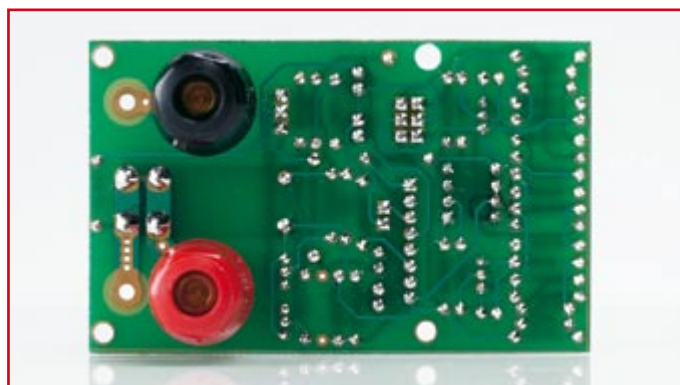
## Literature

[1] Transparent V-I Protection in Audio Power Amplifiers, Michael Kiwanuka. Electronics World, October 2002.



Advertisement

Your price conscious PCB supplier

**EURO**  
CIRCUITS

Online price calculation  
 Online ordering  
 Online order tracking  
 Online 24/24H and 7/7D

Interested? Contact us: +44 2088 167 005

E-mail: [euro@eurocircuits.com](mailto:euro@eurocircuits.com)

[www.eurocircuits.com](http://www.eurocircuits.com)

Verified

- pooling for standard boards
- up to 6 layers
- from 1 to 1000 pieces
- from 3 working days onwards

A la carte

- pooling with more options
- up to 8 layers
- from 1 to 1000 pieces
- from 3 working days onwards

On demand

- your board, our challenge
- up to 16 layers
- from 1 piece onwards
- from 3 working days onwards

# MikroElektronika EasyPIC5 Development System

Jan Buiting

Out of Belgrade comes a vast line of microcontroller development tools and related goodies that's sure to make microcontroller geeks drool and students and other beginners start examining their wallets, savings or budgets — the prices sure are attractive! We examined EasyPIC5, one of the flagship dev kits from MikroElektronika.



Many moons ago, development systems for microcontrollers were supplied by none other than ... the manufacturers of the relevant devices. Alas, these kits were expensive or hard to come by if you were not a journalist/reviewer or a manager commanding 20 or more staff in the product design department. Also, in the early days, manufacturer-specific dev kits, although comprehensive and with technically fine contents, would give you an uneasy feeling of being chained to, again, the microcontroller manufacturer for support and hardware extensions ("sure, that can be done with our product xyz, I'll connect you to sales...").

Today, that's changed a lot and anyone with a reasonably defined target for hardware product development, or an educational interest, should be able to buy microcontroller development systems that can be relied on to give a head start. Although prices generally have come down, the link to the device manufacturer seems inevitable. Or is it?

## Unpacking

The EasyPIC5 box is compact yet sturdy and in general shows good packaging standards applied. The board, measuring 25×21 cms and having rounded corners, struck me as well laid out and extremely solid (it's 3 mm thick). It has lots of useful markings on the silkscreen overlay and, remarkably in this day and age, no SMD parts except one voltage regulator. The general finish of the board is superb — no hand-soldered wires or knifed PCB tracks revealing design errors a.k.a. 'h/w revisions'. A pity, though, some of the jumper setting instructions are obscured when the graphic LCD (GLCD) is installed on the board.

The review board came with the 2×16 character LCD and DS1820 temperature sensor in a separate package — this is an optional add-on costing \$15 extra. MikroElektronika sell a variety of optional add-ons for the board, including a touchpanel and a 128×64 pixel graphic LCD. At \$24 and \$7 respectively these items are good value for money and it seems wise to order them straight away with the EasyPIC5. Other add-ons include CAN, SmartMP3, RS485, Ethernet and IrDA. A remarkable built-in feature of the

board is called MikroICD. This in-circuit debugger allows you to monitor (on your PC), the state of all registers inside the MPU while it executes object code. The associated PC software called PICFlash2 is a free download as well as supplied on CD.

Besides the EasyPIC5 User Manual, the box also contains 'hard copy' i.e. printed documentation of the PICFlash2 and mikroICD utilities — a rare find in this day and age of CD-ROMs and Internet. All printed matter is bright, copiously illustrated and has a consistent layout and use of colours, from the Quick Start leaflet right up to the print on the CD-ROM.

## EasyPIC5 overview

Despite claims in favour of competing devices, Microchip PIC microcontrollers have a leading position in terms

of EasyPIC5 may be found on the CD in the kit.

## POS and NEG

My only criticism of the EasyPIC5 kit proper is that the 2×16 LCD and the DS1820 should have been included in the package instead of supplied as an option at \$15 extra. These add-ons make for a lively start for first time users like myself. I took the DS1820 temperature sensor project as my first attempt to use the board and it was up and running in less than half an hour, including a short experiment with the MikroICD feature.

The kit and the software tools supplied succeed in freeing your mind from hardware intricacies and instead concentrating on software and understanding and optimising the PIC code (in that order). For example, using

MikroBasic it wasn't too much trouble to program three temperature levels at which PIC output lines are activated. When I got the hang of it, cheerfully debugging an

associated indication using the 7-segment LED display, I was told to stop and finish this review.

At \$129 (plus P&P and options) and the dollar in the toilet at the time of writing, EasyPIC5 is good value for money. A wide distributor network is available as well as support, both directly from MikroElektronika themselves and from knowledgeable users in their online Forum, where critical users are not shunned either and all the latest on updates etc. can be found. Further encouraging points to mention are the neatly produced manuals, the non-SMD approach, the wide range of low-cost add-on boards, and a fine selection of get-you-going examples. Users will also appreciate the trial versions of MikroC, MikroPascal and MikroBasic on the CD with the kit. Registration keys for these compilers can be obtained online from MikroElektronika.

(071070-1)

## Web Links

**MikroElektronika:** [www.mikroe.com](http://www.mikroe.com)

**UK distributor:** [www.paltronix.com](http://www.paltronix.com)

**US distributor:** [www.circuit-ed.com](http://www.circuit-ed.com)

---

**At \$129 (plus P&P and options) and the dollar in the toilet at the time of writing, EasyPIC5 is good value for money.**

---


of acceptance among not only enthusiasts and students, but also seasoned workers in the embedded industry. At the heart of the EasyPIC5 board sits a PIC16F877 in its 40-way DIP case. However you can remove it — besides the DIP40 socket, DIP20, DIP18, DIP14 and DIP8 sockets are available on the board to take PICs with fewer pins. The EasyPIC5 documentation tells you which are suitable.

I/O-wise the PIC is totally accessible with all its ports bonded not only to connectors and DIP switch arrays but also LEDs for easy visualisation of logic states as you program along (and make errors!). Input to the digital ports is easy to simulate by means of 36 pushbuttons labelled with port line names. The analogue world is not forgotten either with PIC pins RA0-R5 on pinheaders and two potentiometers on the board to simulate discrete analogue levels between 0 and 5 V.

For higher level connectivity, the board has RS232, PS/2, USB and a 4-digit 7-segment display, not forgetting the USB comprised in the MikroICD of course.

Hardware fans will like to know that the complete schematic and board lay-

# Tiny Counter

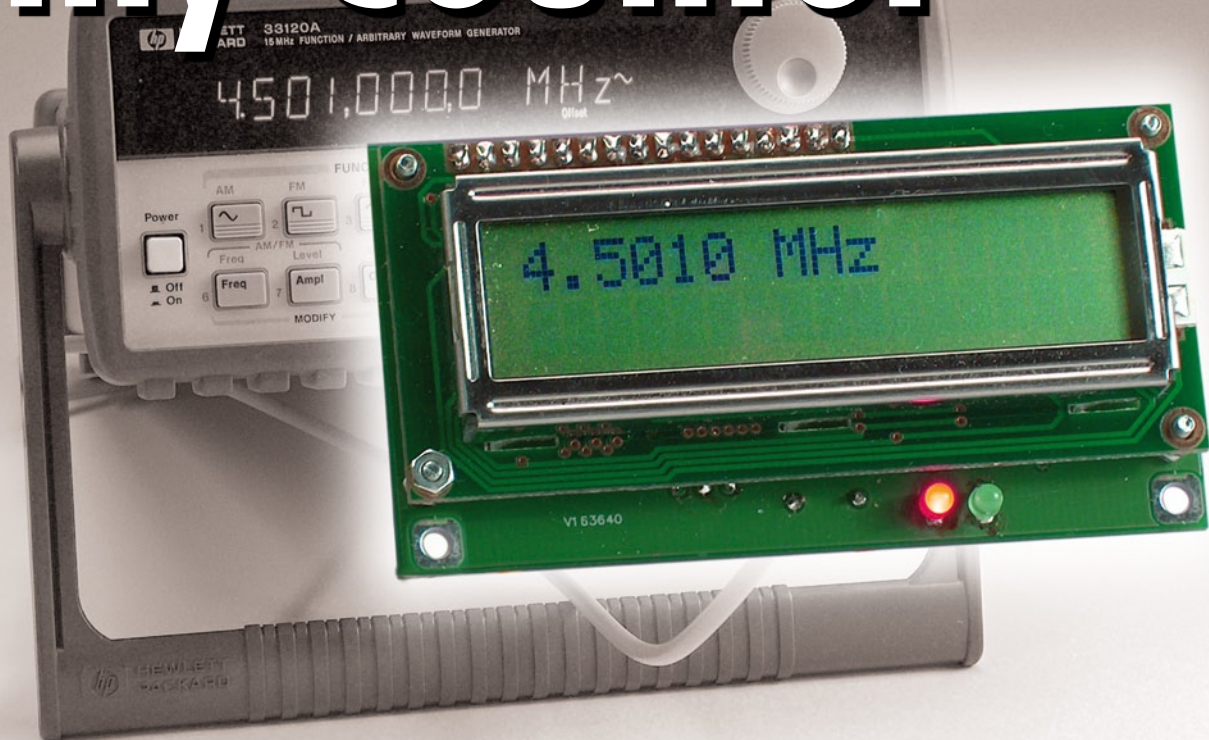

Jochen Brüning

## Frequency counter module using ATtiny2313

**Most small function and signal generators do not have a very accurate frequency control and do not offer a built-in frequency counter. Help is at hand with the tiny frequency counter module described here, which consists essentially of just an ATtiny2313 microcontroller and an LCD panel. The microcontroller is clocked at 20 MHz, and so the counter module can be used at frequencies of up to 5 MHz without the need for a prescaler.**

This counter module is therefore ideal for retrofitting to an existing signal generator or as the main component of a tiny self-contained frequency meter. In the former case it will probably be possible to derive power for the module from the unit's own power supply, and the signal input of the module is best connected to an existing square-wave (5 V level) output. The display ranges from 0 Hz to 5 MHz with automatic selection between units of Hz, kHz and MHz according to the input frequency.

### Mini counter

The starting point for the module described here was the minimalist 1 MHz frequency counter design by Hergen Breitzke described in the July/August 2005 issue of *Elektor Electronics* [1]. That design employed an AT90S2313 programmed using the BASCOM AVR Basic compiler. This version is based on the same principles but uses an ATtiny2313 rather than the AT90S2313. The newer device can be clocked at up to 20 MHz, which allows us to extend

the maximum frequency from 1 MHz to 5 MHz. Fortunately 20 MHz crystals are readily available off-the-shelf. The processor clock speed directly determines the maximum frequency that can be counted: according to the datasheet, the maximum allowable frequency at the counter input pin is one quarter of the processor clock frequency, and this is how the 5 MHz limit arises.

To make the display as easy to read as possible the frequency value is shown in MHz, kHz or Hz as appro-

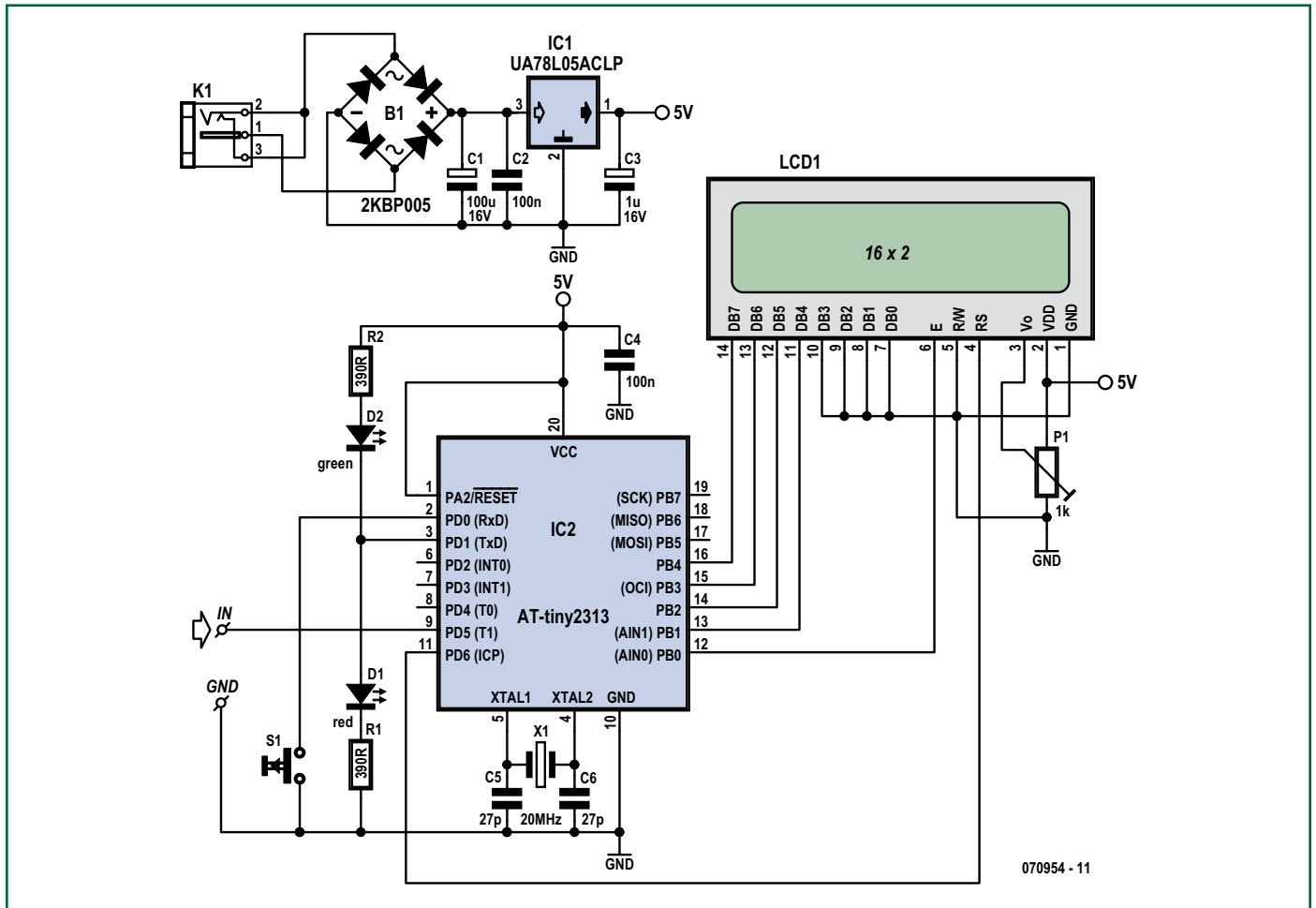


Figure 1. As can be seen from the circuit diagram, the frequency counter consists of just a microcontroller with accompanying voltage regulator and LCD panel.

appropriate, with the decimal point being shifted as needed. The display does not change to and fro rapidly when the unit switches between ranges.

The frequency value is deliberately shown as only five digits. In the highest range (MHz) the 10 Hz and 1 Hz digits are suppressed so that the display is steady and easy to read. If required, the software can easily be modified to show these digits. The hex file and source code for the software are naturally available as a free download from the *Elektor* website.

It is also possible to cause the suppressed digits to appear without modifying the software. The circuit diagram in **Figure 1** shows a button (S1) connected to pin 2 of the microcontroller. When the button is pressed and pin 2 is taken to ground, the counter will show the 10 Hz and 1 Hz digits when in the MHz range. A switch could be used instead of the button or, if this facility is not required, the button could simply be omitted altogether.

## Construction

As can be seen from the circuit diagram in Figure 1, there are no special components in the design and the unit

is very simple, consisting essentially of just the microcontroller, a voltage regulator IC and the LCD panel. Just a few components are required to support the operation of the microcon-

## Features

- Frequency range 0 Hz to 5 MHz
- Accuracy dependent on crystal, typically 50 ppm to 100 ppm
- Display in units of Hz, kHz or MHz with automatic selection
- Stable display even when range changes
- Selectable 5-digit or 7-digit display using pushbutton
- Indication of gate open and display update via red and green LEDs
- Power supply: 5 V DC regulated or 6 V to 9 V AC or 9 V to 12 V DC unregulated
- Current consumption approximately 40 mA (when display specified in parts list is used)
- Simple construction
- No SMDs, no special components
- Printed circuit board and ready-programmed microcontroller available
- Hex file, source code for software and printed circuit board layout available for free download from [www.elektor.com](http://www.elektor.com).

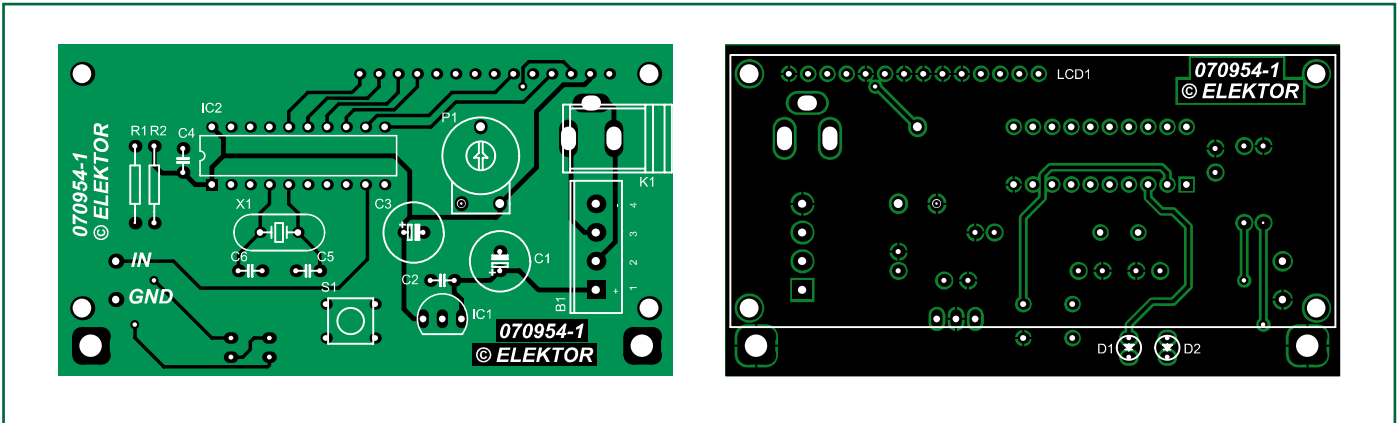


Figure 2. The double-sided printed circuit board for the frequency counter module. There are no SMDs in the design.

Components list

Resistors

R1,R2 = 390Ω  
P1 = 1kΩ preset

Capacitors

C1 = 100μF 25V radial  
C2,C4 = 100nF  
C3 = 1μF 25V radial  
C5,C6 = 27pF

Semiconductors

IC1 = 78L05  
IC2 = ATtiny2313, programmed, Elektor  
Shop # 070954-41  
B1 = 2KBP005  
D1 = LED, 3mm, red  
D2 = LED, 3mm, green

Miscellaneous

LCD1 = LCD module, 2 x 16 characters,  
e.g. Displaytech 162

X1 = 20MHz quartz crystal  
S1 = miniature PCB mount switch  
K1 = mains adapter socket, PCB mount  
14-way pinheader, 1 row, lead pitch 2.54 mm  
2 solder pins  
PCB, ref. 070954-1  
Software and PCB layout, free download  
from www.elektor.com

troller: decoupling capacitor C4, and crystal X1 along with load capacitors C5 and C6. We allow ourselves the luxury of two LEDs connected to a spare processor pin. These light alternately in synchrony with the gate time of the counter (which is fixed at 1 s). The red LED lights when a measurement is taking place, and the green LED lights when the reading is transferred to the display. If the signal source has a very stable frequency, the display will not change from reading to reading, and the LEDs then give comfort that measurements are indeed taking place.

A socket (K1) is provided on the printed circuit board (Figure 2) to connect a mains adaptor. The power supply circuit consists of a bridge rectifier (B1), a smoothing capacitor (C1) and a 5 V regulator (IC1) with a further smoothing capacitor (C3) at its output. The bridge rectifier sug-


gested in the parts list can be replaced by four individual type 1N4001 diodes arranged as shown in the circuit diagram. Because a full-wave rectifier is used, the circuit can be powered from an AC source (6 V to 9 V) or a DC source (9 V to 12 V) of either polarity. Current consumption is only

stalled in a device that already has a regulated 5 V supply, components IC1, C1, C2, B1 and K1 can be omitted and power wired directly to the pin of IC1 connected to the positive side of capacitor C3 and to ground.

The double-sided printed circuit board uses no SMDs and all but three components are mounted on the top side of the board. The LCD panel is mounted on the back of the board, connected using a 14-way header and secured using four screws (see photographs). The two LEDs (D1 and D2) are also mounted on the back of the board so that they face the same way as the LCD.

In operation

Before applying power, check that all the components have been fitted correctly and inspect all the solder joints. When power is applied the two LEDs should flash once

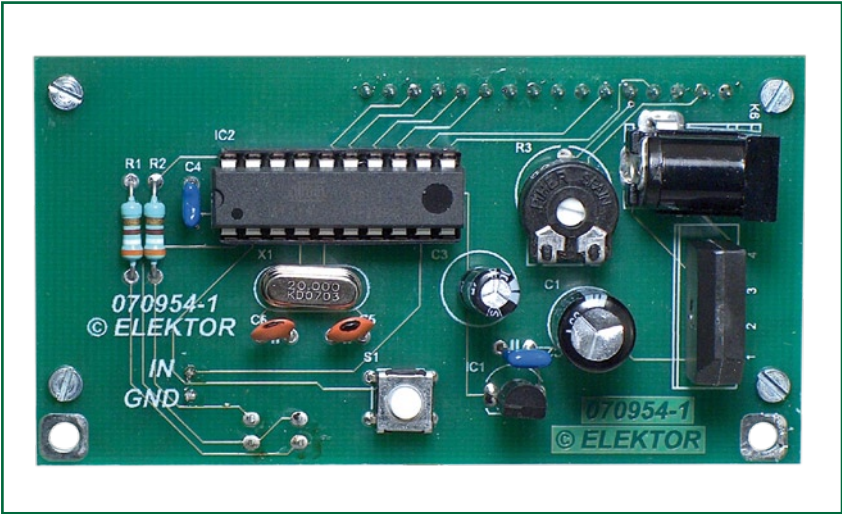

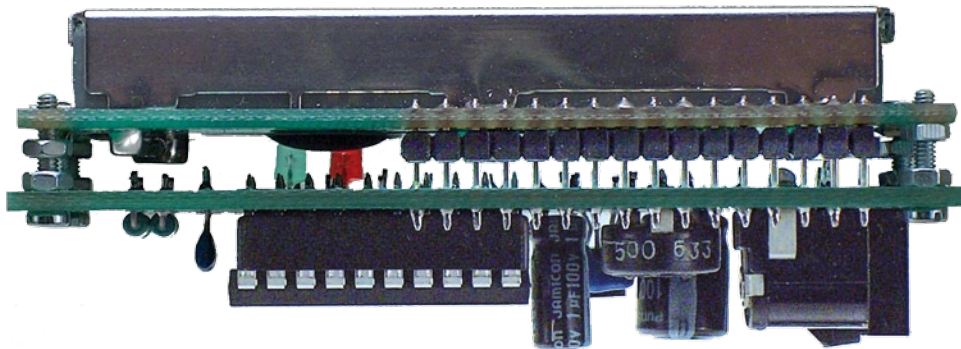


Figure 3. Prototype of the frequency counter module. The two-line LCD panel is mounted on the back of the board using a 14-way pinheader, and is secured using four screws.

per second as described above, and, if the input is shorted to ground, the display should show 0 Hz. If the input is allowed to float it will probably pick up mains hum (a piece of wire can be used as an antenna to help) and the counter will read 50 Hz.

If the display is blank, the problem can most likely be rectified using the only adjustment point on the module: display contrast potentiometer P1.

If a TTL-level square-wave signal with a frequency of at most 5 MHz is now connected to the input its frequency should be displayed. The accuracy of the reading depends on that of the processor clock frequency, which in turn depends on the crystal. An error of 100 ppm in the crystal frequency

Figure 4. The units used for displayed switch automatically between (a) Hz, (b) kHz, and (c) MHz, according to the input frequency.



corresponds to a measurement error of 100 Hz at 1 MHz, and a crystal error of 50 ppm corresponds to 50 Hz at 1 MHz. In the audio frequency range an accu-

racy of better than 1 Hz can be expected.

For applications where a TTL-level signal is not available a small preamplifier is required to produce the necessary square wave. We will be addressing the subject of preamplifiers and prescalers for frequency counters in *Elektor* in the near future.

(070954-1)

## Reference

[1] 1 MHz Frequency Counter, *Elektor Electronics*, July/August 2005, p. 100.

## Where is the counter?

In order to measure frequency the circuit needs a timer to define the gate time and a counter to count the number of pulses that arrive during the gate time. However, there is no counter in the circuit diagram, just a microcontroller IC.

The solution to this puzzle is that the counters are inside the microcontroller. There are two internal hardware counters, one of eight bits and one of 16 bits, which can be configured as timers or as counters at will. In our application the 16-bit counter is configured to count the 5 V (TTL- or CMOS-level) pulses that appear on input pin 9. The maximum value that the counter can store is 65535, and this limit is overcome by arranging for an interrupt to occur each time the counter overflows.

The number of interrupts that occurs is counted in the interrupt service routine (ISR). At the end of the gate time the interrupt count is multiplied by 65536 and added to the current counter value. If the gate time is one second, the result will then be the input frequency in Hz:

$$f = \text{interrupt count} \times 65536 + \text{Timer1 value}$$

The gate time is derived using the 8-bit counter, which is configured as a timer with a divide-by-1024 prescaler. In this way the 20 MHz processor clock is divided down to create a constant gate time of one second.

# Measuring on the PC Display



## Software for measuring purposes

Cris Badea & Thijs Beckers

**Virtually every computer these days is equipped with a reasonably decent sound card. In addition to its audio uses it can also be used for measuring purposes. Install the appropriate software and you have a versatile measuring instrument that can accomplish the most complicated measurements in no time. But which software is the most appropriate? In this article we help you get oriented by giving you an overview of what can be found out there.**

Computers nowadays are fast enough to be useful for making measurements. That is a far cry from 20 years ago when a computer had a 286 processor, 1 MB of memory and a 10 MB hard disc. But now, when we have all those gigabytes and gigahertz at our disposal we can very easily do FFT and other complicated calculations in near 'real-time'. What follows is a selection of software packages that have

been purposely developed for transforming a PC into a test instrument.

### Different purposes

Within this limited group of software applications a further division can be made into three subgroups: software that is

intended for the design of loudspeakers and to make spatial measurements of loudspeakers, software which is designed for general purpose electronic measurements and software intended specifically for audio measurements. There is actually a further subgroup of software that specialises in the acoustic measurement of rooms, but we have included these with the loudspeaker design software.

For this evaluation we used an RME Multiface [1] card. This card is supplied with various drivers such as MME, WDM and ASIO2. The Multiface is capable of sampling 24-bit signals at 96 kHz with a latency of 0.37 ms. This makes this card very interesting for 'fast' measurements such as MLS-measurements (Maximum Length Sequence). The card has 8 analogue inputs and outputs. This makes the card also of interest when more than two channels need to be measured, for example when testing 5.1-configurations, where the perfect position of the loudspeakers needs to be determined for a particular room.

### Loudspeaker design and room simulation

When designing a loudspeaker it is important that the frequency characteristic and the impulse response of the loudspeaker are either known already or can be measured. The impulse response of the room used for the test is also very important, since this affects the acoustics. In recording studios, for example, special attention is paid to the design of the room and what effect this has on the sound.

Measuring the frequency characteristic is very simple in principle. Connect a noise source to the loudspeaker and measure the frequency response with a measuring microphone and a spectrum analyser. It is best to do this in a 'dead room', a room that is virtually free of reflections and rejects practically all sound from the outside. Except that this situation is not very realistic in practice. You don't listen to music at home in a dead room now, do you?

So it is preferable to do the tests in the listening room itself. And if that happens to be your living room than it would be nice if the barking dog next door or the car that happens to drive past are not included in the measurement. The MLS measurement has been invented to allow all disturbing influences from outside the measurement to be excluded. With this measurement technique all parameters are derived from the impulse response.

The Maximum Length Sequence is a periodic pseudo-random binary sequence that functions as the test signal. This signal can be generated using a shift register with feedback. It is possible to mathematically calculate the ratio between the sent and received (measured) signals. The result is a curve with information about the source or the room, depending on what the goal of the measurement was.

### Software for electronic applications

In this category fall the various applications that make it possible to use the PC as, for example, an oscilloscope, spectrum analyser or function generator. Since the signal to be measured has to enter the PC in one way or another, some kind of interface is required. The sound card is the most obvious candidate, because nearly all computers these days are fitted with one.

The quality of the measurement is strongly dependent, of course, on the quality of the sound card. The frequency range also is usually considerably smaller compared with 'dedicated' equipment. A sound card is therefore unsuitable for high frequency applications, but is quite usable at lower frequencies, especially with some of the currently available sound cards that can handle a sampling frequency of

192 kHz at a resolution of 24 bits. Accurate measurements up to 96 kHz belong to the possibilities.

The limitations of a sound card can be overcome with special interface cards, for example from National Instruments or Agilent. These are generally intended for industrial applications and are typically priced accordingly.

### Software for audio measurements

A wide variety of different software packages are available for professional audio applications. The amount on offer is so large that it is impossible to cover all of them here, so we made a selection.


What is typical of this software is that it can be divided into two groups: stand-alone and VST-plugin. VST stands for 'Virtual Studio Technology'. It is a standard that has been developed by Steinberg [2] for virtual musical instruments (VSTi) or effects (VSTfx).

As already mentioned, the amount on offer is huge, but when it comes to features there is remarkable similarity: volume level meters, oscilloscopes, spectrum analysers and correlation measurements. These are, of course, the most frequently used tools when working with audio.

Extensive information about potential measuring techniques can be found on the internet, among those is a document written by Swen Müller and Paulo Massarani [3]. This not only contains information on the 'stepped sine' technique but also MLS and the differences between these two techniques.

## Loudspeaker design and room simulation software

### WinMLS 2004

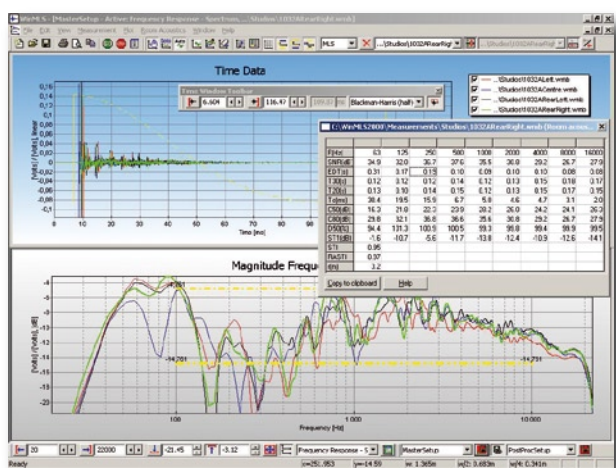

As the name of the program indicates, WinMLS 2004 can be used to make MLS measurements. The program generates a very detailed frequency characteristic. There is a selection of signal sources available. The setting options are nearly endless, which makes this software very comprehensive. Except that how to use it is not always very clear.

The software is very reliable and accurate and optimal for system calibration and spacial measurements, help when designing loudspeakers and is even suitable for resonance measurements of buildings.

The screen shot shows several features such as time- and frequency-windows and room acoustics.

WinMLS is available in various configurations which vary in price from \$ 100 to \$ 1000. The software is only suitable for Windows and can use any sound card that is compatible with Windows. For more information: [www.winmls.com](http://www.winmls.com)


### Praxis

The Praxis software from Liberty Instruments Incorporated is essentially the same as WinMLS. But Praxis has a few extras. For example, an RTA-function (Real Time Analyser). This can be used to make direct ('real-time') measurements. The settings can be stored as presets.

The documentation is quite extensive and there are a large number of wav-files that can be downloaded from Liberty Instruments that can be used to carry out measurements and tests.

On this website you can find many examples and explanations how certain measurements should be made including the required files and descriptions.

For programmers, the manufacturer also has made a Script Designer available online. Script Designer can be used to write applications for Praxis. The script is based on Microsoft Visual Basic and Borland Delphi. It was during our evaluation not at all obvious how the AudPOD interface is circumvented to enable you to use your own microphones, but the website clearly indicates that this should be possible. The accompanying screen shot shows the important win-

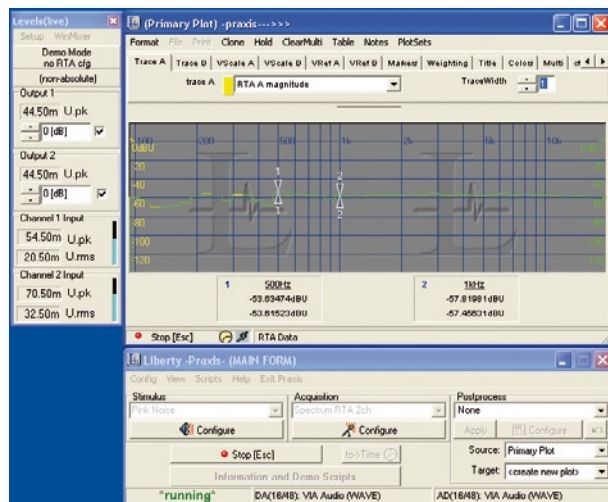


dows of Praxis, which allow most of the settings to be changed and measurements performed. Praxis is clearly a Windows based application. The price amounts to \$ 998. The 'free' version lets you do quite a lot but not all the program's features are available. For more information: [www.libinst.com](http://www.libinst.com).
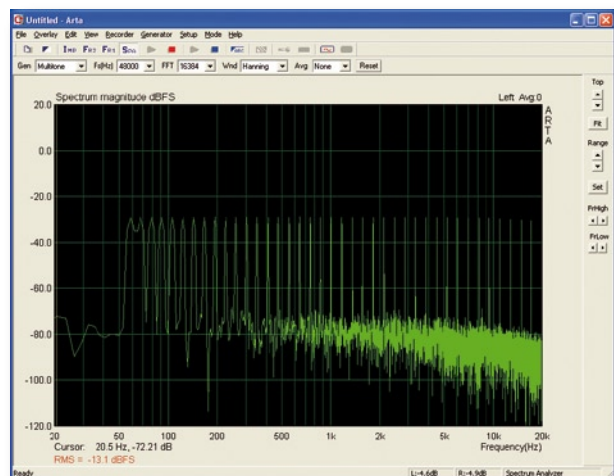
### ARTA, STEPS and LIMP

A fantastic set of programs has been developed at the electronics university in Split in Croatia. The set comprises three applications: ARTA for impulse response measurements, real-time spectrum analysis and frequency analysis, STEPS, which uses 'stepped-sine' excitation for frequency response measurements and LIMP for the measurement of loudspeaker impedance.

ARTA can be used for loudspeaker measurements, room parameters and speech intelligibility analysis. It is very user friendly and well-organised. The software offers various measurement sources which are completely configura-



ble. Among others, you can use white noise, pink noise, MLS, linear/log 'stepped sine' and periodic white and pink noise. The test results are very clearly displayed and further calculations using these results are very easily made.

The manuals are very extensive and easy to follow. There are examples of different configurations, measurements and settings.

A comprehensive procedure for the calibration of the sound card is also available. This calibration is obviously very important when doing these types of tests.

The software is only suitable for Windows and costs from £ 36 (€ 49) to £ 110 (€ 149). The demo version does not allow anything to be saved, but is otherwise fully functional. More information at: [www.fesb.hr/~mateljan/arta](http://www.fesb.hr/~mateljan/arta)


### FuzzMeasure Pro 3

Attention Mac users! This is one of the few applications of this genre for OS X.

FuzzMeasure was originally intended for room measurements, but its application is much broader however. The main purpose of this software is to calibrate rooms such as live podiums, auditoriums, studios, etc. FuzzMeasure is not only suitable for measuring delays and reflections in rooms but can also be used to generate loudspeaker characteristics, for example.

The program uses the swept-sine method, which avoids ambient noise and distortion.

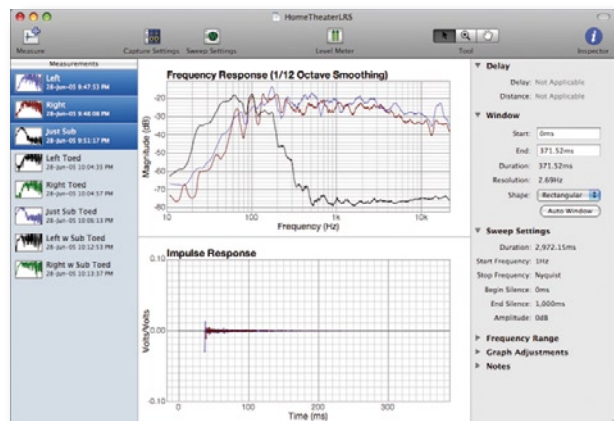The software is only suitable for OS X Leopard and costs \$ 150. At the time of writing the software is up to version 3.0.2, which contains a few bug fixes compared to version 3.0. You can find more information at [www.supermegault-ragroovy.com](http://www.supermegault-ragroovy.com).




## EASERA

EASERA is the most complete software package that we came across. With a price tag varying from \$ 750 to \$ 2250, EASERA has a very big arsenal of measuring features.

What makes the package very interesting is that it still uses a sound card and not an expensive expansion module. EASERA gives the option of choosing between several different drivers, such as the ASIO drivers, which are famous as the fastest drivers for audio processing.

The software consists of four modules: a measurement module, a signal generator, real-time analyser and post-processing module. If this is not enough you can expand the software package with the Time Delay Spectrometry module from Gold Line ([www.gold-line.com](http://www.gold-line.com)).

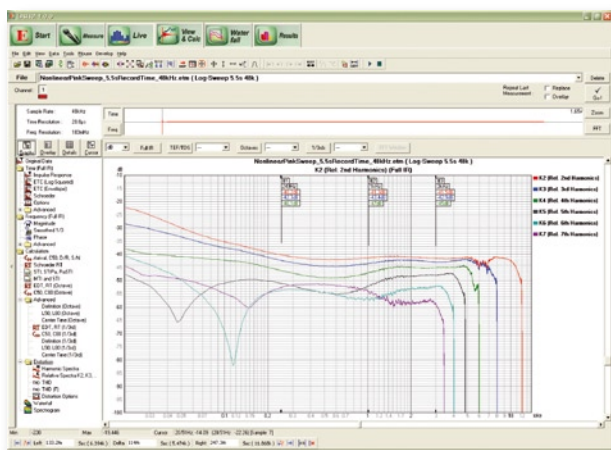EASERA can perform measurements using, among others, swept sine and MLS and with these can take into account the room and different types of background noise. The program can also analyse wav-files and it can use the inputs



of the sound card to record signals.

Calibrating the sound card is simple, provided the card has a synchronisation clock. If the card has multiple inputs or outputs, a second input or output can be used for synchronisation and to determine the delay. All the settings are quite easy to use, despite the large number of options available.

EASERA also has automated functions, such as microphone calibration, adjusting the input sensitivity and compensating for the frequency characteristics of the hardware used. Comprehensive FFT measurements can be made in real-time, volume meters can be consulted and spectrograms can be displayed. Presets can be stored, so that they can be used again or later on during post-processing. The real fun starts at post-processing. Available to you are calculations for Room Acoustics, Electro Acoustics, RMS, noise levels, echo grams, etc. Here it is also possible to manipulate the various signals in both the time and frequency domains.

EASERA can monitor up to 32 inputs with a sampling frequency of 192 kHz, which is also of interest for PA-applications at concerts.

EASERA is the perfect tool for the professional sound engineer. The functionality is practically endless and the reliability is high. More information can be found at [www.sda-software-design.de](http://www.sda-software-design.de) and [www.easera.com](http://www.easera.com).

## Software for electronic applications


### Multi-instrument 3

Multi-Instrument 3 is a very intelligent and functional program. It provides the following measuring instruments:

- a digital oscilloscope with transient recorder, data recorder, voltmeter, Lissajous plotter and digital filter.
- a spectrum analyser with amplitude spectrum analysis, power spectrum analysis, octave analysis, phase spectrum analysis, correlation analysis, frequency response measurements, distortion analysis, noise analysis, dynamic signal analysis, etc.
- a signal generator with a function generator, an arbitrary waveform generator, a burst generator, a white and pink noise generator, a multi-tone generator, an MLS generator, a musical scale generator, DTMF generator, and frequency and amplitude sweep.
- a multimeter with voltage measurement, SPL measurement, frequency measurement, RPM measurement, duty cycle measurement, etc.
- an LCR meter with inductance meter, capacitance meter, resistance meter and impedance meter.

A matching probe makes this software quite unique. The probe has an audio plug which can be connected directly to the input of the sound card. An attenuator is built into the probe which protects the audio inputs of the computer against over-voltages. The probe can be used to safely measure voltages up to  $\pm 24$  V.

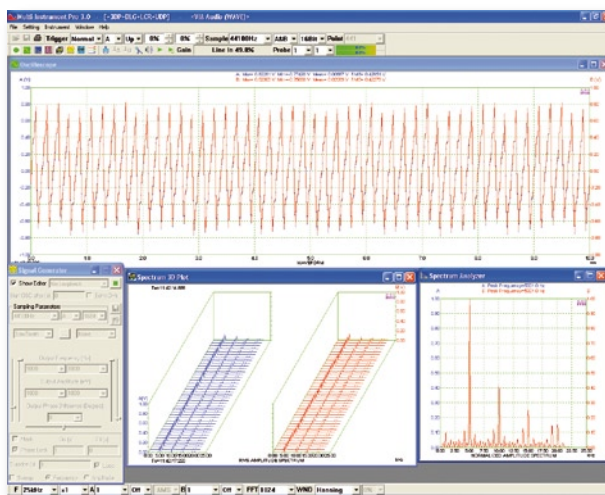
The price of Multi-Instrument is between \$ 50 and \$ 200, depending on which version and options you choose. The probe costs \$ 30. There is also a version intended for Pocket PCs, Pocket Multi Instrument 1.0. This version does however have fewer features compared to its 'big brother'. For more information surf over to: [www.virtins.com](http://www.virtins.com)



### Zelscope


Zelscope turns a PC into a dual-channel storage scope and spectrum analyser. It uses the sound card as A/D-converter and shows in real-time the wave shape and spectrum of the signal.

The program is quite easy to use and reliable. Zelscope costs \$20. For more information surf to [www.zelscope.com](http://www.zelscope.com)

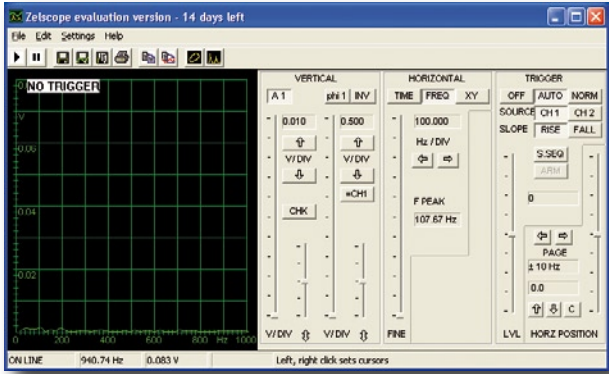

OscilloMeter 6.0


This Russian software is not likely to win a beauty contest, but there are no complaints about its functionality. It is quite comprehensive, but the cluttered design makes it quite hard to use. What is convenient however, is that as soon as you start the software you have four information windows, a dual-channel oscilloscope and spectrum analysis (optionally in 3D) of the left and right channels. Additionally there are extensive generator functions and multimeter options.

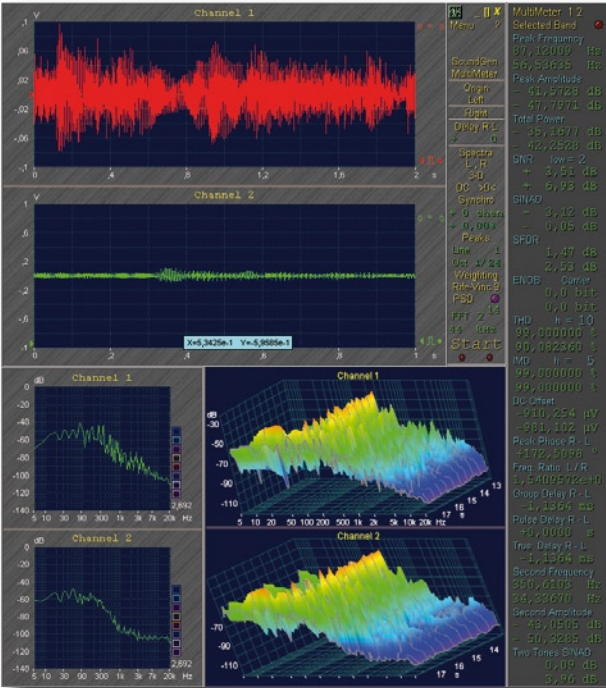

The demo version is restricted to only 15 seconds of unlimited functionality. After this the measurement stops. It does work again when you restart it. To remove this limitation you need to send \$500 to the designer, who will then send you a registration code. More information can be found at <http://shmelyoff.narod.ru>

AudioTester

AudioTester is quite a simple Windows application which consists of an oscilloscope, a spectrum analyser and a signal generator. The signal generator WaveGen is a very comprehensive module that is intuitive to use. It offers various waveforms and step and pulse signals. The design gives the appearance that you're using a physical instrument and not software. You can find more information at [www.sumuller.de/audiotester](http://www.sumuller.de/audiotester)

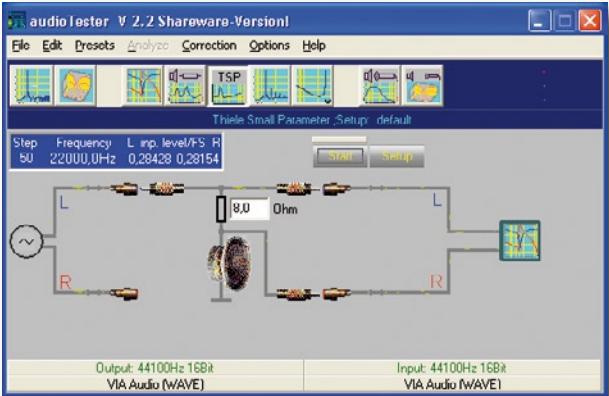

Software for audio measurements

Digicheck - RME

This free software works only with sound cards from RME. It is a very intuitive to use, stand-alone program (only for Windows) with various functions: stereo and multi-channel level



measurements, spectrum analysis, vector audioscope, correlation measurements and bit statistics. The program can record multiple channels simultaneously (Global Record). The picture shows the Totalyser, which shows the spectrum analyser, the level meter and vector audioscope. More info at [www.rme-audio.com](http://www.rme-audio.com)

Spectre

The layout of Spectre is very nice and well-organised. It is set up in modular fashion so that you can arrange your own desktop. The software is very extensive. A few of the test instruments are: level meter, VU-meter, BBC meter (peak meter with BBC scale), oscilloscope, spectrograph, low end



meter, high end meter (separate parts of the audio range), level history meter, waveform meter, spectrogram, Lissajous meter, power balance meter, correlation meter, etc. In addition, spectrum comparison, phase comparison, coherence measurement and playing of sound files also belong to the feature list.


On the website [www.audiofile-engineering.com](http://www.audiofile-engineering.com) you can find more information about Spectre. The software package costs \$ 120 and is only suitable for Mac OS X.

### Electroacoustics Toolbox and SignalScope pro 2.0

These two applications by Faber Acoustical are only suitable for Mac OS X. Electroacoustics Toolbox is a comprehensive package that consists of several modules. There is a Dual FFT analyser which can, among other things, make the following measurements in the frequency domain: amplitude transfer function, phase transfer function, coherence, group delay, signal to noise ratio, etc. In the time domain the following measurements are possible: impulse response, quadratic impulse response and cross-correlation.

There are several other modules available, including an FFT analyser, an octave band analyser, an oscilloscope, a sound level meter, a 3D spectrogram plotter and an X/Y plotter.

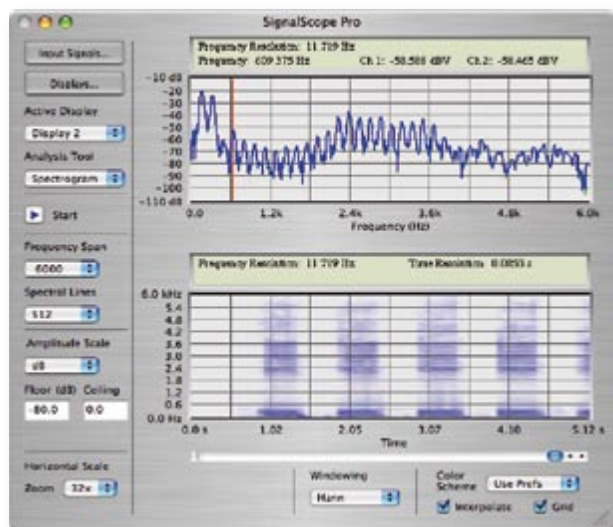SignalScope is a comprehensive oscilloscope with FFT features. Signal scope is really a 'lite' version of Toolbox. It uses a single window where everything is set up and




measured.

Electroacoustics Toolbox costs about £ 370 (€ 500) and can be ordered from the Faber Acoustical website: [www.faberacoustical.com](http://www.faberacoustical.com). SignalScope, which costs about £ 55 (€ 70), is considerably cheaper than Toolbox and can be purchased from the same website.
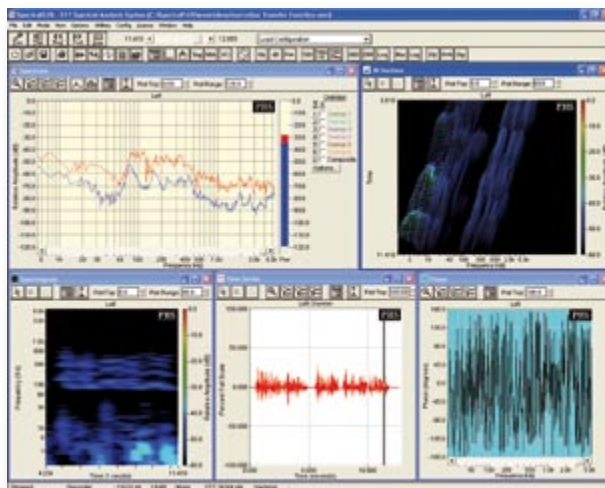
### SpectraPLUS

SpectraPLUS is an audio spectrum analyser which is mainly targeted at real-time measurements. It is only available for Windows and comprises various 'options' (modules), which have to be bought separately. The most important functions are: real-time FFT analysis of the signal at the sound card input, recording and playing of wav-files, displaying the measured signal in the time domain, in the frequency domain and in 2D and 3D spectrograms.

The FFT measurements are very extensive and the resolution is high, 1,048,576 points. The octave analysis can be set



from 1/1 to 1/96. The measurements can be made at up to 24 bit and 200 kHz sampling frequency, depending on the capabilities of the sound card.

Ten different options are available which are suited for different applications. For example, the base package offers you only a mono channel that can be used for measurements, an FFT analysis which is limited to 1/1 and 1/3 octave analysis, phase measurement and microphone compensation.

The base package of SpectraPLUS costs \$ 295. Each additional option or module costs a further \$ 200. There are

Advertisement

### FAST RESPONSE THERMISTOR SENSORS



Semitec the world's most innovative NTC manufacturer, offers a range of novel, fast-acting thermistor sensors for temperature control problems in the electronics industry.

Cost-effective, mini TO-220 style packages with R25s from 1kΩ to 100kΩ can be mounted directly to a P.C.B. or fitted with flying leads. Exposed bead sensors monitor and control rapid air-flow movement and "Soft-touch" sensors operating to 200°C offer time constant as fast as 0.5s.

Our latest NC sensors reacts quickly to I.R. output in non-contact applications where thermopiles would be restricted by high local ambients.

Let us help you solve your temperature control problem, contact us today.

#### ATC Semitec Ltd

Unit 14 Cosgrove Business Park  
Daisy Bank Lane, Anderton,  
Northwich Cheshire, CW9 6FY

Tel: 01606 871680 Fax: 01606 872938


Email: [sales@atcsemitec.co.uk](mailto:sales@atcsemitec.co.uk)

**Web: [www.atcsemitec.co.uk](http://www.atcsemitec.co.uk)**

also bundles for \$ 595 and \$ 795 and the complete package costs \$ 995. You can find more information about SpectraPLUS here: [www.telebyte.com/pioneer/index.html](http://www.telebyte.com/pioneer/index.html)
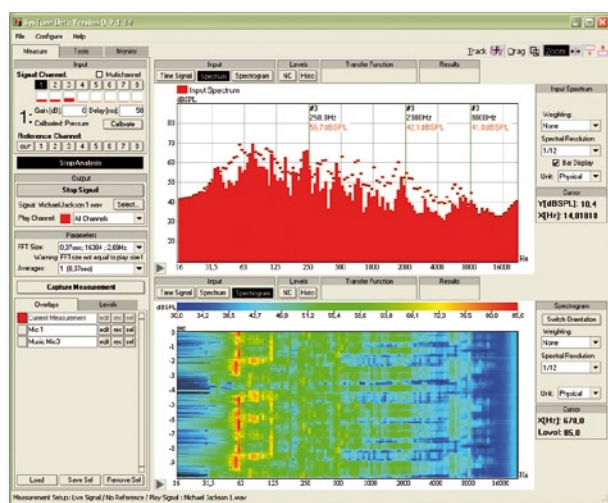
### EASERA SysTune

Most of the description of EASERA also applies to SysTune. It is very comprehensive and reliable, but quite expensive. In addition to the fact that you can use SysTune to measure 8 channels at a sampling frequency of 192 kHz, simultaneously and in real-time, SysTune also offers the following capabilities: the program gives a choice between live input signals or internally generated signals, impulse response measurements, spectrogram measurements, multiple-channel FFT, phase measurements in real-time and much more.



For the price of \$600, SysTune comes as a complete test system, which not only lets you make all kinds of measurements on the incoming signal, but can also do spatial measurements and measurements for the positioning of loudspeakers in studios and auditoriums. More information: [www.easerasystune.com](http://www.easerasystune.com)

### VB Audio

VB Audio is a company who mainly develop VST plugins. They have developed a range of plugins which are intended for audio measurements, for example, Frequencies Analyser, LF Generator and VU Meter. The names already indicate what they do.



What is very interesting, is the stand-alone application FFX16. This application can 'load' several plugins. This transforms the PC into a real-time audio processing and measuring instrument. The 'stacking' of plugins makes it possible to measure several frequency ranges at the same time, by first separating the desired frequencies with band-pass filters.

The Frequencies Analyser has this function built in. In addition to level measurements in the frequency domain the plugins can measure the difference in frequency between left and right channels and display spectrograms.

You can generate various waveforms with the LF Generator. Impulse and sweep modes are also included. The VU Meters is a very stable and accurate meter that is very flexible to use.

On the VB Audio website you can find much more information about these plugins: [www.vb-audio.com](http://www.vb-audio.com).

### Conclusion

With a simple sound card you can quickly measure all kinds of things using a computer. The results of these measurements depend of course on the application for this 'test set-up' and the quality of both the hardware and the software. Cheaper cards often have high latency and a low maximum sampling frequency. This can cause problems when calibrating, which leads to inaccurate measurements.

Software that is much too cheap often means that there is no money and therefore no time for development and testing, so that it is less reliable and the test results may be questionable.

A small step up and still reasonably affordable are for example TiePie [4] and Picotech [5]. The best solution depends on the measurements required and the financial room available.


In conclusion we can state that there are plenty of programs available that are very good at making measurements using the sound card. Obviously, this type of solution cannot compete with professional test instruments from, for example, National Instruments. But then, these cost considerably more.

(071084-1)

### Web Links

- [1] [www.rme-audio.de/en\\_products\\_multiface\\_2.php](http://www.rme-audio.de/en_products_multiface_2.php)
- [2] [www.steinberg.net](http://www.steinberg.net)
- [3] <http://saturn5.com/~jwb/mueller.pdf>
- [4] [www.tiepie.com](http://www.tiepie.com)
- [5] [www.picotech.com](http://www.picotech.com)

Things of the past.

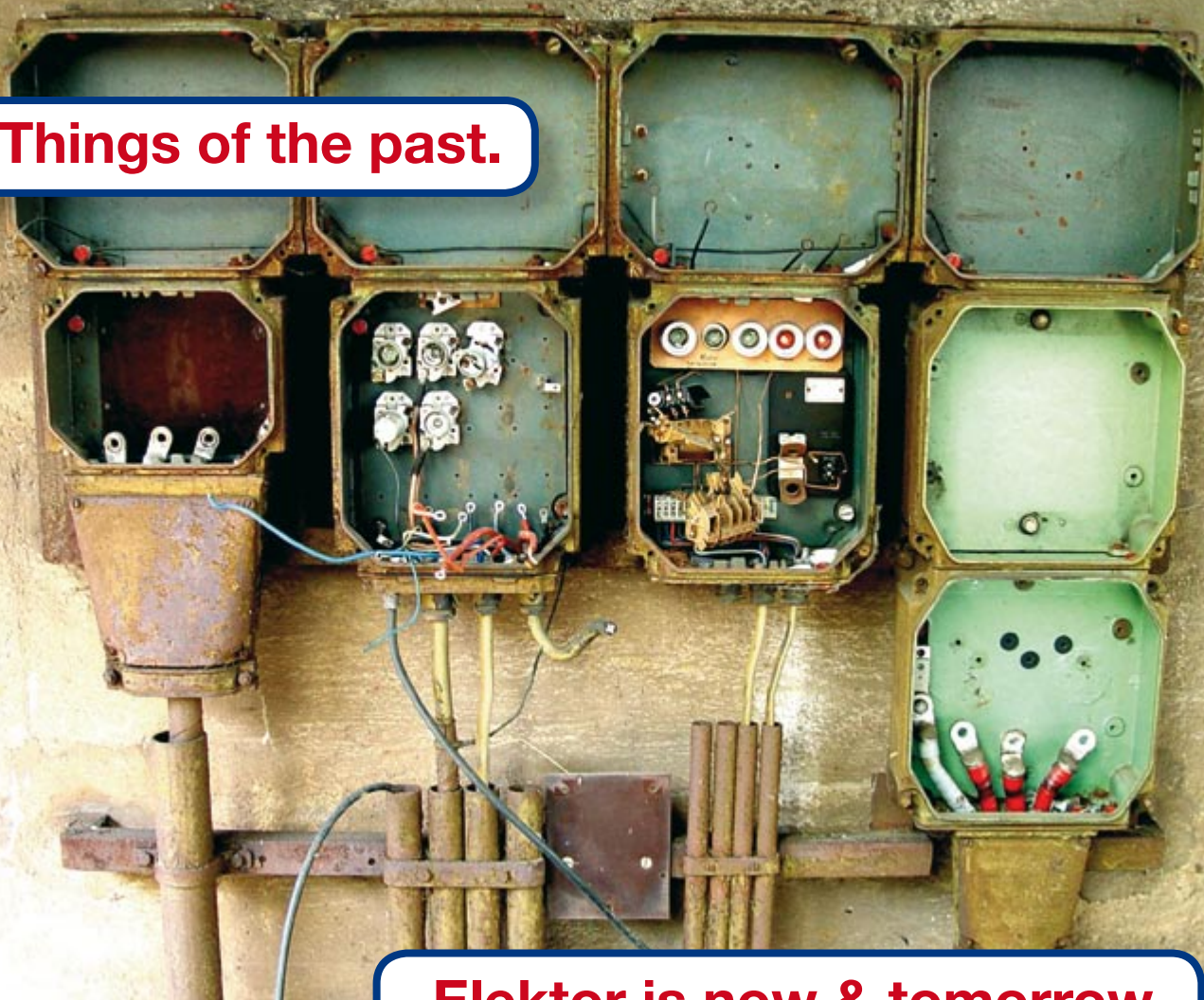

Elektor is now & tomorrow.

Secure a head start in electronics with a subscription!

Advantages to subscribers:

- ✓ Cheaper than 11 issues from the newsstand
- ✓ Subscribers get up to **40% discount** on special Elektor products
- ✓ As a welcome gift you get a free **1GB MP3 player** worth £ 34.50
- ✓ No queues, travelling, parking fees or 'sold out' Elektor is supplied to your doorstep every month
- ✓ Always up to date – read your copy before everyone else



**FREE 3-in-1 welcome gift: 1GB MP3 player, USB Stick and Voice Recorder**

[www.elektor.com/subs](http://www.elektor.com/subs)  
Tel. +44 (0) 20 8261 4509

Or use the subscription order form near the end of the magazine.

**elektor**  
electronics worldwide

# E-blocks: Flowcode Interrupts



## Who's afraid of INT?

Sean King (Matrix Multimedia)

Dear Elektor I am unsure myself of the best use of interrupts in Flowcode so hence the request for guidance. Flowcode is an excellent and fast way to program microcontrollers. Interrupts are such an important part of using a microcontroller I felt I needed to ask for some help, I'm sure that many Flowcode users would also bene t from an article. Thank you for your response.  
Dave Lamer

Here you are, Dave,  
hope you find the article useful.

**Just a mention of the word 'interrupt' makes many novice programmers shiver nervously and state that the use of interrupts is 'far too complicated for them' and that they can 'make do without'. Actually the principles and practical use of interrupts is not that complicated, and in this article we hope to take some of the mystique out of interrupt programming to encourage you to make use of this really useful programming technique.**

A simple programming method used to monitor multiple events within a program, and react accordingly, is to continuously test and react as each event occurs. This methodology is termed 'Polling' and it can be achieved relatively easily and successfully in simple loop program with a series of 'IF' statements and associated subroutines. But as programs become complex the use of subroutines, which may include delays and tests for further external events, means that it is increasingly difficult to guarantee the response of a program to an external event within the required response time. On top of this the use of polling is inefficient as every failed test for an event is a waste of system resources.

To overcome this problem the internal circuitry of micro-controllers is designed to allow programmers to run pre-determined subroutines on the occurrence of an external, or internal, event — separate from the main program. This provides interrupts with two big advantages:

1. the main program does not need to test for the interrupt events, simplifying the program structure;
2. Response to an interrupt event will be quick!

### Examples, please

#### An external digital input interrupt

As an example, consider a domestic burglar alarm: if polling alone was used then it would not be possible for the alarm to be triggered whilst a user was entering a key code to unlock the system: the program would be waiting for the

user to enter a key and could not service the alarm trigger routine. However if the sensor input is connected to an interrupt pin then the programmer can develop a system where the alarm trigger routines are run whatever the rest of the program is doing.

### Internal timer interrupt

An example of an internally generated interrupt is the timer interrupt. Within a microcontroller, a digital counter block, made up from a chain of flip-flops, is connected to the main system clock. The counter block generates an internal interrupt signal each time the counter overflows. The design of the counter block is enhanced so that the effective length of the counter block is determined by the contents of a writable memory register within the chip, allowing the programmer to determine the effective length of the counter. Together this digital block of circuitry and the memory register is called the ‘prescaler’ and it allows programmers to generate an interrupt every, 2, 4, 8, 16, 32, etc. counts, depending on the length of the counter.

The timer interrupt is incredibly useful: if you have a microcontroller clocked with a crystal at 19660800Hz with a 16-bit prescaler counter then it produces an internal interrupt at 19660800/65536: an interrupt 300 times per second. So all you have to do is have a small timer interrupt routine that counts 300 of these and you can accurately produce a clock that shows time passed in seconds. In practice there are many variations of the external digital interrupt and the timer interrupt: external interrupts can be active low or high, some microcontrollers have timer interrupts that can be triggered on an exact count match, etc.

### Other internal interrupts

Most microcontrollers are integrated with a collection of peripheral devices. Each peripheral device contains hardware that is optimised to perform task that would be difficult, time consuming, or even impossible for an unaided microcontroller to undertake. Most of these devices have the ability to generate interrupts when special events occur. Here are just a few more examples:

- UART, SPI, I<sup>2</sup>C: interrupts can be triggered when data is received or a transmission complete.
- A/D converter: interrupt triggered when the A/D conversion is complete and sample available.
- Data EEPROM: interrupt triggered when write operation is completed.
- Comparator: interrupt triggered when the input has changed from previous status.

### Putting it into practice

The example program you can download from the Elektor website (archive # 071069-11.zip) shows how a Flowcode program written for the ATMEGA32 can use two interrupts to create a high speed analogue data logger. Download it, unpack and open it with Flowcode for AVR.

When a microcontroller is powered up, all interrupts are off by default – so the first task a programmer has is to turn them on. The ‘main’ flowchart contains a sequence of three icons which configure the chip to be suitable for our purposes.

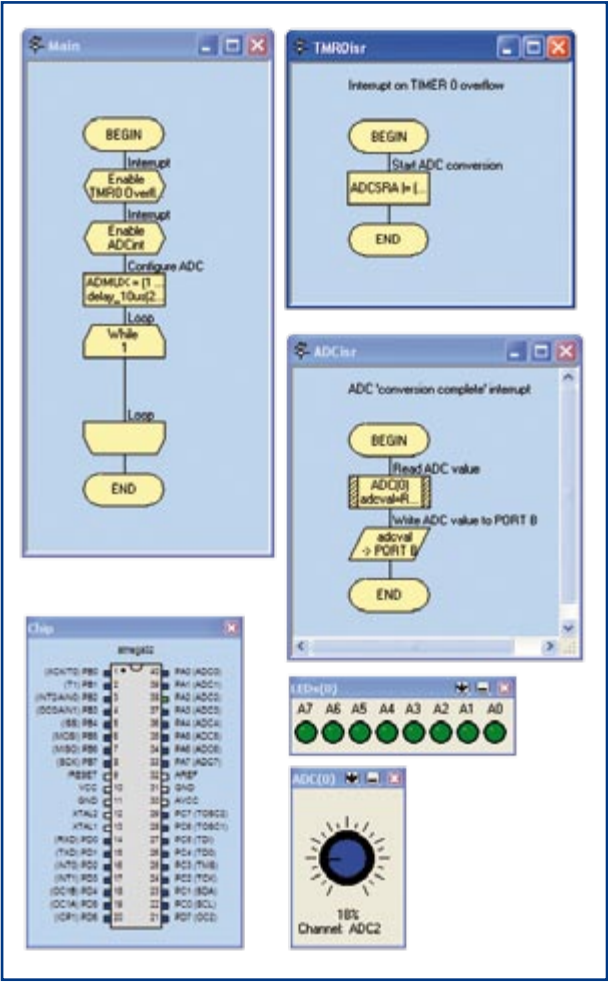


Figure 1.  
A practical example of an interrupt driven program.

Flowcode is supplied with an interrupt function block. You select it from the vertical toolbar at the left of the screen by clicking on the small yellow lozenge with ‘INT’ in it. It provides direct support for several of the more common interrupts. There is also a custom interrupt option that can be used to configure each of the unsupported interrupts offered by the target device.

**The first icon** configures the timer interrupt. Clicking on it results in the dialogue box shown in **Figure 2**. Here you can see that we have selected the TMR0 (TiMeR 0) overflow interrupt to be enabled and that when the timer 0 overflows the macro, or subroutine, in the flowchart TMR0Isr is called. Clicking on the Properties button reveals the screen in **Figure 3** where you can see that the parameters of the timer 0 overflow interrupt can be selected. The interrupt frequency here is 1200 Hz which means that the macro TMR0Isr is called 1200 times a second.

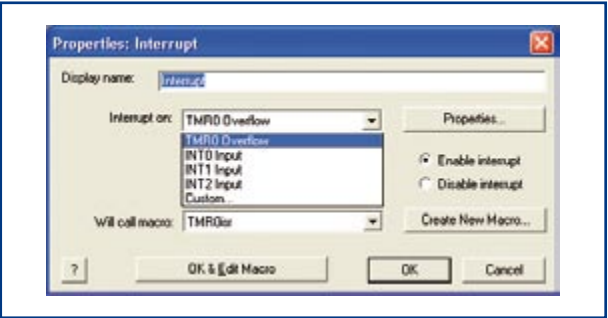


Figure 2.  
First interrupt icon properties.

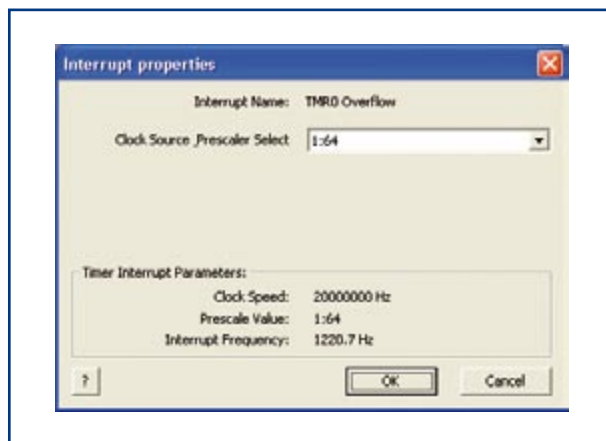


Figure 3.  
The properties of the  
Timer 0 interrupt.

**For those who are curious,  
here is the maths on Figure 3:**

The clock is 20 MHz. The prescaler is 1:64 – effectively a 6 flip flop counter.  $2^6 = 64$ . However the clock feeds into an 8 bit counter before it reaches the prescaler – effectively a 14 bit counter.  $2^{14} = 16384$ . So the actual interrupt frequency is  $20000000/16384 = 1220.703\text{Hz}$ .

In this case the TMR0 interrupt has been configured to generate an interrupt at a frequency of 1220.7Hz (819.2µs), see Figure 3.

From the 'Interrupt on' drop box shown in Figure 2 you can see that other interrupts are available which are as follows:

- INT0: interrupt when a selected transition is detected on the INT0 pin;

- INT1: interrupt when a selected transition is detected on the INT1 pin;
- INT2: interrupt when a selected transition is detected on the INT2 pin.

If you are just starting out with interrupts then use of the timer and INT interrupts will be as far as you want to go for now. Once you have mastered these then you may want to learn a little C code, dig into the datasheets of the microcontroller and you can then take advantage of more advanced interrupts as follows.

**The second icon** in the flowchart configures a second interrupt in the Atmega chip: the A/D Converter Conversion Complete interrupt. Once this is on the flowchart if you click on the icon and select the 'Custom...' option from Figure 2 you will get a new dialogue box as shown in **Figure 4**. Here you need to enter appropriate C code which enables the interrupt by setting the status of the ADCSRA register (ADC Control and Status Register A), and then additional C code which ensures that the selected Flowcode macro is called. Using interrupts like this requires some knowledge of the inner workings of the microcontroller device itself, and a little C code.

**The third icon** in the program sets up several variables for the program. After this we get to the main program loop. As you can see this is a 'loop while 1' pair which simply loops the program round the loop forever. The odd thing about this program is that there are no instructions in the main loop at all!

**The TMR0ISR macro** is called each time a timer-0 interrupt is issued. This macro contains a single C command that initialises the ADC conversion in the Atmega chip. Note that a Flowcode ADC conversion hardware macro is not used here as these require a response from the ADC hardware inside the chip (curiously enough using the Polling technique) suspending operation of the main program until conversion is complete, or a timeout period has elapsed.

## Techtalk 'onINT'

After a Power-On-Reset, interrupts are usually disabled. The microcontroller has several levels of control over its interrupts. A Global Interrupt Enable (GIE) flag is available in one of the system registers to allow the entire interrupt system to be enabled or disabled in a single instruction. Individual interrupt enable flags (e.g. TMR0IE) are contained in various system registers allowing each interrupt to be enabled and disabled independently.

Interrupts will only be generated when they are enabled both individually and globally. When an interrupt is generated it will set a flag in one of the system registers (e.g. TMR0IF). This can be used to confirm the presence of the interrupt request, and should be cleared before returning to the main program.

There are several different requirements for clearing interrupt flags, depending on the interrupt type, device family etc. Reference should be made to the device data sheet.

### Interrupt operation

When an active interrupt condition is detected, the microcontroller completes the machine instruction it is currently executing, saves the address of the next instruction to be

executed in the main program onto the stack, and loads the program counter with an alternative address — similar to a programmed subroutine call. The address loaded into the program counter is that of an interrupt vector. What the microcontroller expects to find at the interrupt vector address depends on the device type.

Two popular devices are the PIC16F877a and the ATMEGA32.

The PIC device has a single interrupt vector and expects to find a sequence of instructions starting at the vector address. One of the first tasks to be carried out is to identify which of the potential sources generated the interrupt, before branching to the appropriate service subroutine.

The ATMEGA32 has a separate interrupt vector for each interrupt source. There is no need to identify the source of the interrupt in this case so the device expects to find the address of the service routine at the vector address.

The outcome of the response to an active Interrupt ReQuest (IRQ) is that the program flow is diverted from the main program and directed to the appropriate Interrupt Service Routine (ISR) that performs the tasks required by the interrupt event, clears the interrupt, re-enables the interrupt system (if necessary), and returns the program counter to the next instruction in the main program.

The **ADCisr** macro is called each time an ADC Conversion Complete interrupt is issued. This macro then reads the sample ADC value and outputs this value onto a bank of LEDs on Port B.

## Back to the program

The entire program is handled by interrupts. The TMRO interrupt generates interrupts at a frequency of 1200.7 Hz. The TMRO interrupt service routine macro (TMROisr) starts the ADC conversion and returns to the main program loop. The ADC Conversion Complete interrupt service routine macro (ADCisr) reads the converted ADC value and writes it to PORT B before returning to the main program loop. Almost any program could be written in place of the main While loop, without affecting the operation or timing of the data logging function. Of course this is not necessarily a practical program, but hopefully it illustrates the use of a simple timer interrupt as well as giving an example of a more complex interrupt and an idea how these are set up.

## Interrupt pitfalls

It is important that interrupt service routines are completed as quickly as possible. Most will transfer small amounts of data, update a variable, or trigger another event. Program loops, macro calls, and complex calculations should be avoided. The delays involved in writing data to the LCD could cause problems in a multi-interrupt application. In this case the interrupt service routine should transfer any necessary data to a suitable location and create an indicator that

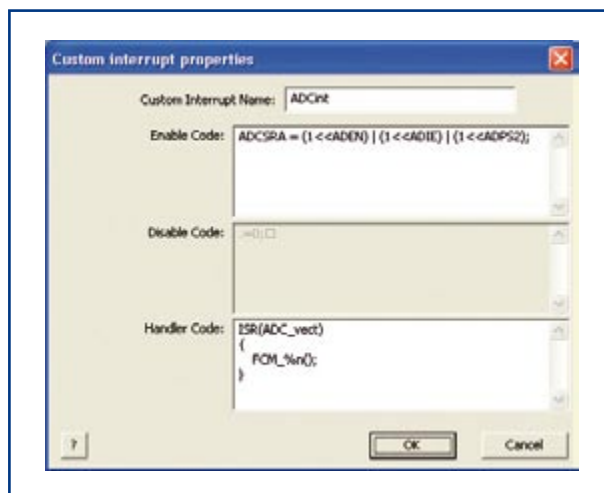


Figure 4.  
The advanced ADC complete code in C.

the main program can use to detect that an interrupt has been serviced and further action is required.

The fact that interrupt response times are down to individual machine instructions can cause problems if an interrupt occurs during a multi-instruction operation, especially if the interrupt service routine modifies a variable that is in the process of being used by the main program. There are many techniques for avoiding this problem, enough to justify another complete article.

(071069-1)

Advertisement

**PCB-POOL®**  
SERVICING YOUR COMPLETE PROTOTYPE NEEDS

**1 EUROCARD**  
(160 x 100 mm)  
+ Tooling  
+ Photoplots  
+ VAT  
**€49**

Price example  
Any size and contour possible!

**Optional:**

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

**DOWNLOAD OUR FREE LAYOUT SOFTWARE!**

**Freephone** **0800-3898560**

Tel.: +353 (0)61 701170  
Fax: +353 (0)61 701165  
pcb-pool@beta-layout.com

**PCB-POOL.COM**

Simply send your files and order ONLINE:

We add value to PCBs when others just sell it.

- One Step Manufacturing Service
- Free Electronics Components
- Free Prototyping Assembly
- Professional Consultant

**EzPCB**


**High Quality Competitive Price**

**www.EzPCB.com**  
**Email: sales@ezpcb.com**

## An SPI-networked Microcontroller
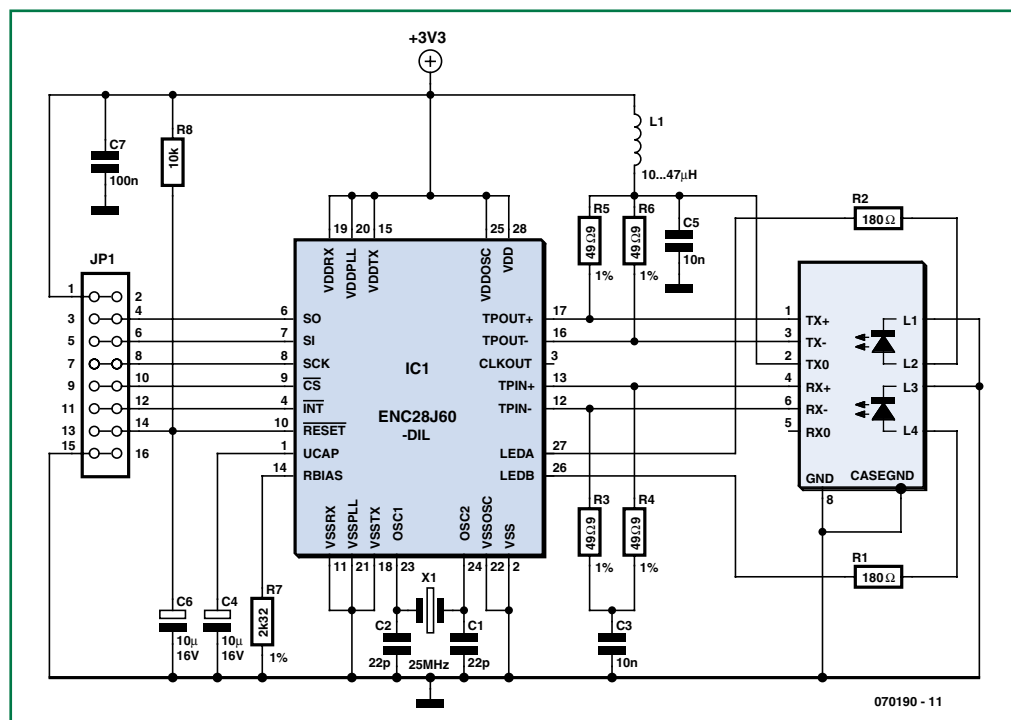
## Dirk Böhm

A little over a year ago Microchip [1] launched the first Ethernet controller with SPI connectivity — and just 28 pins. With the ENC28J60 available also in a solder-friendly DIP version, this makes embedding a microcontroller in a local network particularly simple and attractive. The basic circuit (see diagram) requires only a handful of extra components, enabling the whole affair to be built conveniently on a piece of Veroboard (stripboard) or on a solderless prototyping breadboard. A MagJack integrated module from Belfuse [2] is our choice for the network connector. Apart from this you will need a 25-MHz crystal oscillating at its fundamental or natural frequency. Online suppliers of the microcontroller, connector and crystal include [3] and [4] but you may well know of other firms that are closer to hand. The 1% tolerance resistors, capacitors and coils are available from the usual mail order firms, such as Maplin, Rapid Online and Conrad Direct. Once you have powered up the module you need to apply a frequency of 6.25 MHz on PIN 3 (CLKOUT), otherwise a link will not be established to the network. This 6.25 MHz signal must come from a crystal oscillator operating on its fundamental frequency. If you cannot detect any trace of the 6.25 MHz signal try removing the capacitors experimentally. For your very first trial you should try activating the LEDs connected to the microcontroller. If this works read out



the Revision ID. Should something prevent reading to and from the Register, sending some packets should unblock this. If you don't feel like developing the TCP/IP Stack from scratch you can download an over-ready TCP/IP Stack absolutely gratis from Microchip! For developing network application software we recommend installing the Ethernet network sniffer, downloadable at [5]. This lets you log all the packets passing in broadcast mode or direct to and from the controlling PC. One final tip: it's crucial that you

download the errata and update information relevant to the particular Revision ID of the module you are using [1]!

## SPI in a nutshell

The Serial Peripheral Interface Bus or SPI (often pronounced 'es-p -' or 'spy') bus is a synchronous serial data link standard named by Motorola that operates in full duplex mode. Devices communicate in master/slave mode where the master device initiates the data frame. Multiple slave devices are

allowed with individual slave select (chip select) lines. Definition from Wikipedia [6].

(070190-I)

## Web Links

- [1] [www.microchip.com](http://www.microchip.com)
- [2] [www.belfuse.com](http://www.belfuse.com)
- [3] [www.csd-electronics.de](http://www.csd-electronics.de)
- [4] [www.microcontroller-starterkits.de](http://www.microcontroller-starterkits.de)
- [5] [www.ethereal.com](http://www.ethereal.com)
- [6] [http://en.wikipedia.org/wiki/Serial\\_Peripheral\\_Interface\\_Bus](http://en.wikipedia.org/wiki/Serial_Peripheral_Interface_Bus)

## Symmetrical square wave

## Patrick Knöbel

Just about anyone must be familiar with the NE555 by now. It is one of the most common components in do-it-yourself circuits. This IC, however, was not designed specifically to generate a clock signal, and certainly not one with a duty-cycle of 50%, although it is frequently used for that.

There are of course a number of circuit possibilities that could realise a duty ratio of 50%.

**Figure 1** shows a solution

that uses two diodes. Capacitor C is, via the diodes, always charged and discharged with the same resistor value, so there is no asymmetry and the duty-cycle stays at 50%. We can calculate the (clock) frequency as follows:

$$f = 1.44 / (2RC)$$

where  $R_1 = R_2 = R$ .

It is however not possible to calculate the frequency exactly because the forward voltage drops of the diodes are not known.

This and the fact that six parts are required make it worthwhile to think about another solution. The engineers that STMicroelectronics [11] thought the same.

Their data sheet for the NE555 contains a circuit that, for a clock generator with 50% duty-cycle, requires only three external components (see **Figure 2**).

The amount of time that the output is high ( $t_1$ ), is calculated as follows:

$$t_1 = 0.693 R_1 C$$




The time that the output is low ( $t_2$ ), is a little more complicated:

$$t_2 = (R_1 \times R_2) / (R_1 + R_2) \times C \times \ln((R_2 - 2R_1) / (2R_2 - R_1))$$

For a duty cycle of 50% it is true that  $t_1 = t_2 = t$ . The clock frequency is then:

$$f = 1/2t.$$

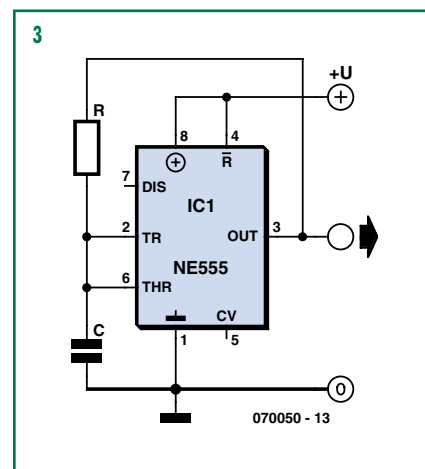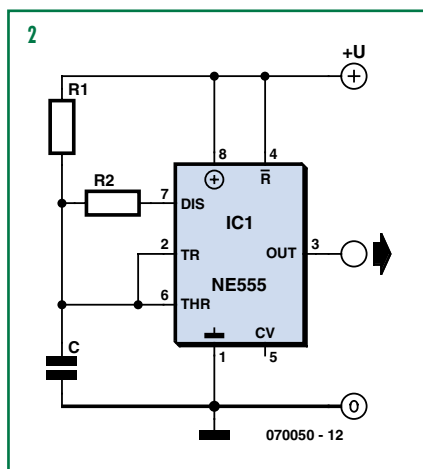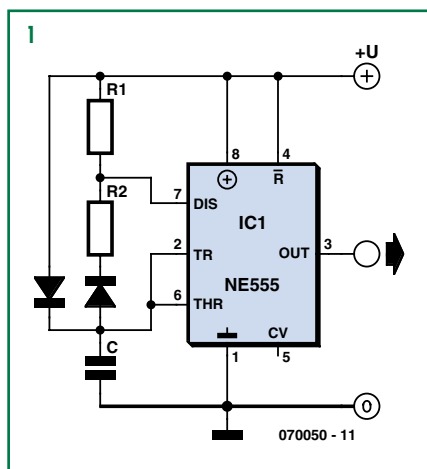The disadvantage of this circuit is that it is not easy to select the values for the components. For example,  $R_2$  may not be greater than  $\frac{1}{2}R_1$ .



So there is an opportunity to do better still. And this is shown in **Figure 3**. This extremely simple schematic shows a clock generator using an NE555 with a 50% duty ratio in its minimal form. It requires only three com-

ponents in total, including the timer IC itself. The frequency can be calculated with this formula:

$$f = 0.72 / RC$$

Where most people would normally use a D-flipflop, we solve that with this circuit using only a capacitor and a resistor. It is not likely to get much simpler than this.

**Links:**

[1] [www.st.com](http://www.st.com)

(070050-1)

Advertisement

**FLYPCB.com**  
*NOTHING IS IMPOSSIBLE*  
**PCB House**  
 FROM CHINA TO WORLDWIDE  
 Start from £30  
 Prototype & Production  
 No Min Order  
 Fast Delivery  
**IMPOSSIBLE IS NOTHING**  
**SALES@FLYPCB.COM**

**ANDRE LAMOTHE'S**  
**XGAMESTATION**  
 LEARN STEP-BY-STEP HOW TO BUILD  
 AND DESIGN YOUR OWN VIDEO GAME CONSOLE!  
 Design inspired by the  
 Atari 800/2600, Sinclair ZX Spectrum,  
 Apple II & Commodore 64!  
 Parallax SX Key Compatible!  
**INCLUDES:**  
 • Tools, Demos & Utilities!  
 • Great for Hobbyists AND Students!  
 • The Fun Way to Learn Embedded Systems!  
 • Fully Assembled XGS Micro Edition Unit!  
 • Complete Software Development Kit!  
 • eBook on Designing the XGS Console!  
 • Cables and Power Supply included!  
**WWW.XGAMESTATION.COM**  
 PH: 512.266.2399 | SUPPORT@NURVE.NET

**PEAK**  
 electronic design ltd

tel. 01298 70012  
 fax. 01298 70046  
[www.peakelec.co.uk](http://www.peakelec.co.uk)  
[sales@peakelec.co.uk](mailto:sales@peakelec.co.uk)

**Handheld Test Gear - Cool, Smart.**

**Atlas DCA** £55

Atlas DCA Model DCA55  
Semiconductor Analyser  
Identifies type and pinout!

**Atlas ESR** £85

**New Low Price!**  
 Atlas ESR Model ESR60  
ESR and Capacitance Meter  
Resolution of 0.01 ohms!

**Atlas LCR** £79

Atlas LCR Model LCR40  
Inductor, Capacitor, Resistor Analyser  
Automatic part identification.

**Atlas SCR** £99

**New Low Price!**  
 Atlas SCR Model SCR100  
Triac and Thyristor Analyser  
Auto gate test current up to 100mA

**UK: Please add £1.00 p&p to your order. Prices include UK VAT. Please see website for overseas pricing.**

# Hexadoku

## Puzzle with an electronics touch

Looking back on the poor weather conditions of the last few months it seems prudent to have a Hexadoku puzzle in stock for yet another a rainy day. If you've not participated before, by all means do so and you may win one of the prizes: an E-blocks Starter Kit Professional and three Elektor Shop vouchers.

The instructions for this puzzle are straightforward.

In the diagram composed of 16 x 16 boxes, enter numbers such that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once only in each row, once in each column and in each of the 4x4 boxes (marked by the thicker black lines).

A number of clues are given in the puzzle and these determine the start situation.

All correct entries received for each month's puzzle go into a draw for a main prize and three lesser prizes. All you need to do is send us the numbers in the grey boxes. The puzzle is also available as a **free download** from our website.

### SOLVE HEXADOKU AND WIN!

Correct solutions received enter a prize draw for an

#### E-blocks Starter Kit Professional

worth **£248.55**

and three **Elektor SHOP Vouchers** worth £35.00 each.



We believe these prizes should encourage all our readers to participate!

The competition is not open to employees of Elektor International Media, its business partners and/or associated publishing houses.

### PARTICIPATE!

Please send your solution (the numbers in the grey boxes) by email to: **editor@elektor.com** - **Subject: hexadoku 5-2008** (please copy exactly).

Include with your solution: **full name and street address.**

Alternatively, by fax or post to: **Elektor Hexadoku**  
**Regus Brentford** - **1000 Great West Road** - **Brentford TW8 9HH**  
**United Kingdom** - **Fax (+44) 208 2614447**

The closing date is **1 June 2008.**

### PRIZE WINNERS

The solution of the March 2008 puzzle is: **C2563**.

The **E-blocks Starter Kit Professional** goes to:  
 Ben Rowles (UK).

An **Elektor SHOP voucher worth £35.00** goes to:

Philip Soper (UK); Silvia Rotondi (I); Sudhir Kumar Gupta (IN).

**Congratulations everybody!**

D					9		7	3				4		B
1	4		3				5			2	C	8		7
		E	F	3			4	8	9	C		D	2	0
8	6	2		E	1		C	4				5	F	3
3	1				E	D	9	2		8	7	4		5
	2		D	C	0	6		1			3	A		B
			A		7	1	B		C	5		3	0	2
5	C				3	F							D	8
	F	B				2	3		1		0			8
2								C	F		9	B	7	D
					F	B		3				0		C
		7	9	D	4			E		6	5			2
	9			B			1		8			E		7
	8	A	7	5	9		F				B			4
	D		2			0	7		5		4			
0	B		4	2				9		A				F

(c) PZZL.com

7	D	1	9	0	8	4	6	3	C	5	B	E	2	F	A
C	2	6	3	D	5	E	A	F	0	4	8	7	9	B	1
F	4	E	8	B	9	7	3	1	6	2	A	5	C	D	0
0	A	B	5	F	1	C	2	D	9	E	7	8	4	6	3
D	8	F	B	A	4	1	0	9	E	3	5	2	6	7	C
6	3	C	E	5	B	9	7	A	2	8	0	D	F	1	4
5	9	2	4	E	3	6	F	7	1	C	D	B	A	0	8
A	7	0	1	C	2	D	8	B	4	6	F	3	E	9	5
8	C	3	A	6	F	0	B	E	D	7	2	1	5	4	9
2	1	5	D	9	A	3	E	0	8	F	4	6	B	C	7
B	F	9	7	4	C	2	5	6	3	A	1	0	8	E	D
E	6	4	0	1	7	8	D	C	5	B	9	F	3	A	2
1	0	A	6	8	D	5	C	2	B	9	E	4	7	3	F
9	5	D	F	3	E	B	4	8	7	1	C	A	0	2	6
4	B	7	C	2	6	A	1	5	F	0	3	9	D	8	E
3	E	8	2	7	0	F	9	4	A	D	6	C	1	5	B

# 'Alibi-Nota' telephone answering machine (1972)

**Peter Beil**

As early as 1972, a telephone answering machine appeared on the market that was second to none: The 'Alibi-Nota FL' with remote listening / erasing functionality. Zettler, a company famous for its pioneering telecomms technology, had succeeded in going round the extremely strict regulations laid down by the German telephone authorities, forbidding private users to send control signals of any kind (be it carriers or dial pulses) over the public telephone system (PTS).

The resultant '0' and '1' code allowed the Alibi-Nota (what's in a name!) to validate the caller/user. The code was programmed using small plug-in boards marked 'yes' and 'no' and inserted into slots marked 1-10 located at the underside of the equipment.



Pulse dialling was the *de facto* standard at the time and DTMF (tone dialling), in its infancy.

The idea of remotely controlling an answerphone machine was ingenious and relied on a 'binary' method: ten short 1-kHz tones played after the welcome message had to be answered or not. In practice, callers had to blow into the mouthpiece or say a word out loud in response to two text-announced tones, or muffle the mouthpiece in response to two other tones.

Pitfalls — sure! 'Static on the line' — quite normal at the time — would have upset the operation of the Alibi-Nota machine as it was unable to discern between 'yes' and 'no'. As part of the

dialogue, further check tones had to be 'answered' correctly, if not, the machine would stop the playback and disconnect. To use the remote erase function, you had to respond to the last tone prompt as well (the last tone naturally was within the call you were making).

Alibi-Nota was a full-fledged tape recorder recording at 2.4 cm/s — fully adequate for



the limited frequency response of analogue phone lines. It was fitted with a call counter, a ring pulse counter and adjustable recording length. For each key, the control buttons could be

locked in any position. The front side had a replaceable cassette for the fixed message. Inside we find an endless tape with a clearance in it for on/off switching and switching over.

Sporting a microphone, foot-switch and fast tape rewind the machine was also suitable for use as a Dictaphone. The complete Alibi-Nota weighs 15 kgs. The tape recorder proper is quite conventional, but the remote control unit is a masterpiece of engineering. Removing the one kilogramme steel cover of the encoder bay reveals a large vertically mounted board that can be hinged out. The relays allow the equipment to be controlled 'in parallel' and the logic circuits used are now long forgotten types from Siemens & Halske like the FLH131, FLJ121 and FLK101.

To date this answerphone is fully functional on the analogue phone system. In 1972 it would have set you back the equivalent of about a month's wages.

(071073-1)

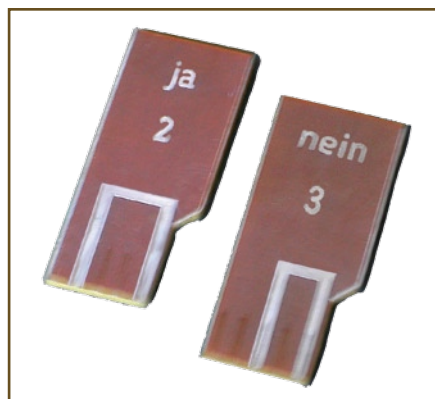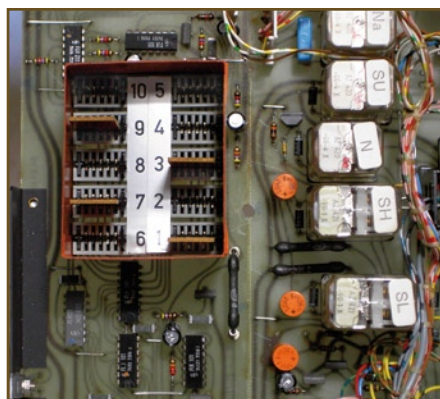

# ELEKTOR SHOWCASE

To book your showcase space contact Huson International Media

Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

## ATC SEMITEC LTD

[www.atcsemitec.co.uk](http://www.atcsemitec.co.uk)

Thermal and current-sensitive components for temperature control and circuit protection;

- NTC Thermistors
- Current Diodes
- Thermostats
- Re-settable Fuses
- Thermal Fuses
- Temperature Sensors

Call today for free samples and pricing

Tel: 01606 871680 Fax: 01606 872938

## AVIT RESEARCH

[www.avitresearch.co.uk](http://www.avitresearch.co.uk)

USB has never been so simple...

with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232 interfaces.



See our webpage for more details. From £10.00.

## BETA LAYOUT

[www.pcb-pool.com](http://www.pcb-pool.com)

Beta layout Ltd Award-winning site in both English and German

offers prototype

PCBs at a fraction of the cost of the usual manufacturer's prices.



## BOWOOD ELECTRONICS LTD

[www.bowood-electronics.co.uk](http://www.bowood-electronics.co.uk)

Suppliers of Electronic Components

- Semiconductors
- Opto Electronics
- Passives
- Enclosures
- Switches
- Stripboard
- PCB Materials
- Popular Special Offer Packs

Online Store, all major cards

Same day despatch upto 3.00pm

Personal Service [sales@bowood-electronics.co.uk](mailto:sales@bowood-electronics.co.uk)

## BYVAC ELECTRONICS

[www.byvac.co.uk](http://www.byvac.co.uk)

32Bit ARM

Microcontroller, USB, built in RTC with its own operating system,

no complex

tools, just a

terminal emulator, start writing programs in 20 minutes. Complete with CD-ROM, Software and 100 Page Foundation book



## DECIBIT CO.LTD.

[www.decibit.com](http://www.decibit.com)

Smallest 2.4 GHz ISM band MCU

embedded transceiver modules. Complete tiny solution, ready to transmit RF data by only attaching as example a CR2032 coin cell to it.



## COMPONENTBIN.COM

[www.componentbin.com](http://www.componentbin.com)

Kickstart your development with modules and parts from componentbin.com

- ARM7 modules
- Ethernet modules
- Superb Graphic LCD displays (all with example software)

and much much more...

Online ordering and great prices!



## DESIGNER SYSTEMS

<http://www.designersystems.co.uk>

Professional product development services.

- Marine (Security, Tracking, Monitoring & control)
- Automotive (AV, Tracking, Gadget, Monitoring & control)
- Industrial (Safety systems, Monitoring over Ethernet)
- Telecoms (PSTN handsets, GSM/GPRS)
- AudioVisual ((HD)DVD accessories & controllers)

Tel: +44 (0)1872 223306



## EASYDAQ

[www.easydaq.biz](http://www.easydaq.biz)

- USB powered, 4 relays + 4 DIO channels
- Will switch 240VAC @ 10 amps
- Screw terminal access
- LabVIEW, VB, VC
- Free shipping
- From £38

Design & supply of USB, USB Wireless, Ethernet & Serial, DAQ, Relay & DIO card products.



## EASYSYNC

<http://www.easysync.co.uk>

EasySync Ltd sells a wide range of single and multi-port USB to RS232/RS422 and RS485 converters at competitive prices.



## ELNEC

[www.elnec.com](http://www.elnec.com)

- device programmer manufacturer
- selling through contracted distributors all over the world
- universal and dedicated device programmers
- excellent support and after sale support
- free SW updates
- reliable HW
- once a months new SW release
- three years warranty for most programmers



## YOUR ELECTRONICS OPEN SOURCE

<http://dev.emcelettronica.com>

Website full of Projects and Resources for Electronics Engineers and DIY.

- Tutorial
- Hardware (Schematic & Gerber)
- Firmware (Asm & C)
- Reference Design

Everyone can submit a story as a useful source! 'Share for life'



## FIRST TECHNOLOGY TRANSFER LTD.

<http://www.ftt.co.uk/PICProTrng.html>

Microchip Professional C and Assembly

Programming Courses.

The future is embedded.

Microchip Consultant / Training Partner developed courses:

- Distance learning / instructor led
- Assembly / C-Programming of PIC16, PIC18, PIC24, dsPIC microcontrollers
- Foundation / Intermediate



## FLEXIPANEL LTD

[www.flexipanel.com](http://www.flexipanel.com)

TEAclippers - the smallest PIC programmers in the world, from £20 each:

- Per-copy firmware sales
- Firmware programming & archiving
- In-the-field firmware updates
- Protection from design theft by subcontractors



## FUTURE TECHNOLOGY DEVICES

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers, these devices simplify the task of designing or upgrading peripherals to USB



## FUTURLEC

<http://www.futurlec.com>

Save up to 60% on

- Electronic Components
- Microcontrollers, PIC, Atmel
- Development Boards, Programmers

Huge range of products available on-line for immediate delivery, at very competitive prices.



## ILP ELECTRONICS LTD

[www.ilpelectronics.com](http://www.ilpelectronics.com)

Tel +441233750481

Fax +441233750578

ILP have been manufacturing audio modules since 1971 and apart from our standard range we also offer a custom design service for the OEM market.



## LONDON ELECTRONICS COLLEGE

<http://www.lec.org.uk>

Vocational training and education for national qualifications in Electronics Engineering and Information Technology (BTEC First National, Higher National NVQs, GCSEs and GCEs). Also Technical Management and Languages.



# products and services directory

## MARCHAND ELECTRONICS INC.

[www.marchandelec.com](http://www.marchandelec.com)

- power amplifier modules
- electronic crossovers solid state / valve / passive
- valve amplifiers
- phono preamps
- handheld sinewave generator
- kits or assembled
- software electronic instruments
- custom design services



## MQP ELECTRONICS

[www.mqp.com](http://www.mqp.com)

- Low cost USB Bus Analysers
- High, Full or Low speed captures
- Graphical analysis and filtering
- Automatic speed detection
- Bus powered from high speed PC
- Capture buttons and feature connector
- Optional analysis classes



## NEW WAVE CONCEPTS

[www.new-wave-concepts.com](http://www.new-wave-concepts.com)

Software for Hobbyists:

- Livewire - circuit simulation software, only £34.99
  - PCB Wizard - PCB design software, only £34.99
  - Circuit Wizard - circuit, PCB and breadboard design software, only £59.99
- Available from all Maplin Electronics stores and [www.maplin.co.uk](http://www.maplin.co.uk)



## OBD2CABLES.COM

<http://www.obd2cables.com>

- Thousands of OBD cables and connectors in stock
  - Custom cable design and manufacturing
  - OBD breakout boxes and simulators
  - Guaranteed lowest prices
  - Single quantity orders
  - Convenient online ordering
  - Fast shipping
- Visit our website, or email us at: [sales@obd2cables.com](mailto:sales@obd2cables.com)



## ROBOT ELECTRONICS

<http://www.robot-electronics.co.uk>

Advanced Sensors and Electronics for Robotics

- Ultrasonic Range Finders
- Compass modules
- Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- Wireless Telemetry Links
- Embedded Controllers



## ROBOTIQ

<http://www.robotiq.co.uk>

Build your own Robot!

- Fun for the whole family!
- MeccanoTM Compatible
- Computer Control
- Radio Control
- Tank Treads
- Hydraulics

Internet Technical Bookshop,  
1-3 Fairlands House, North Street, Carshalton,  
Surrey SM5 2HW  
email: [sales@robotiq.co.uk](mailto:sales@robotiq.co.uk) Tel: 020 8669 0769



## RADIOMETRIX

[www.radiometrix.com](http://www.radiometrix.com)

The leading global developer of ISM band, low power radio modules for wireless data transmission:

- Transmitters • Receivers • Transceivers
- RF modems • Evaluation Kits



## SCANTOOL.NET

<http://www.scantool.net>

Scantool.net offers a complete line of PC-based scantools for under £50.

- 1 year unconditional warranty
  - 90 day money back guarantee
  - For use with EOBD compliant vehicles
  - Fast shipping
  - Compatible with a wide range of diagnostic software
- Visit our website, or email us at: [sales@scantool.net](mailto:sales@scantool.net)



## USB INSTRUMENTS

<http://www.usb-instruments.com>

USB Instruments specialises in PC based instrumentation products and software such as Oscilloscopes, Data Loggers, Logic Analysers which interface to your PC via USB.



## VIRTINS TECHNOLOGY

[www.virtins.com](http://www.virtins.com)

PC and Pocket PC based virtual instrument such as sound card real time oscilloscope, spectrum analyzer, signal generator, multimeter, sound meter, distortion analyzer, LCR meter. Free to download and try.



## SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £220 + VAT (£20 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description
- For £330 + VAT for the year (£30 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour

image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So-please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for £220 + VAT
- Text and photo for £330 + VAT

NAME: ..... ORGANISATION: .....

JOB TITLE: .....

ADDRESS: .....

..... TEL: .....

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998

COMPANY NAME .....

WEB ADDRESS .....

30-WORD DESCRIPTION .....

.....


.....

.....

.....
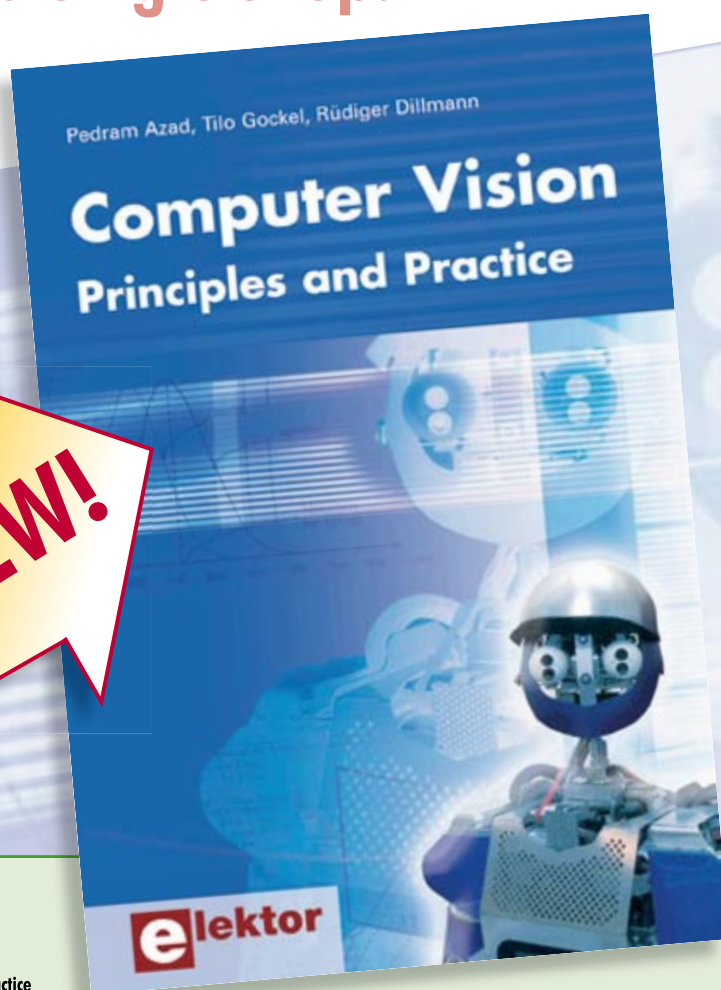
# Going Strong

A world of electronics  
from a single shop!



**NEW!**

Principles and Practice

## Computer Vision

Computer vision is probably the most exciting branch of image processing, and the number of applications in robotics, automation technology and quality control is constantly increasing. Unfortunately entering this research area is, as yet, not simple. Those who are interested must first go through a lot of books, publications and software libraries. With this book, however, the first step is easy. The theoretically founded content is understandable and is supplemented by many practical examples. Among other subjects, the following are dealt with in the fundamentals section of the book: Lighting, optics, camera technology, transfer standards, camera calibration, image enhancement, segmentation, filters, correlation and stereo vision. The practical section provides the efficient implementation of the algorithms, followed by many interesting applications such as interior surveillance, bar code scanning, object recognition, 3-D scanning, 3-D tracking, a stereo camera system and much more.

Approx. 320 pages • ISBN 978-0-905705-71-2 • £32.00 • US\$ 64.00




Silent alarm, poetry box, night buzzer and more!
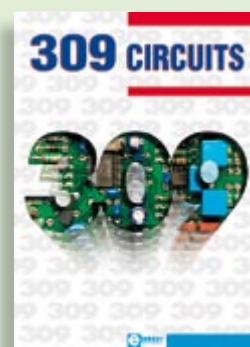
## PIC Microcontrollers

This hands-on book covers a series of exciting and fun projects with PIC microcontrollers. You can build more than 50 projects for your own use. The clear explanations, schematics, and pictures of each project on a breadboard make this a fun activity. You can also use it as a study guide. The technical background information in each project explains why the project is set up the way it is, including the use of datasheets. Even after you've built all the projects it will still be a valuable reference guide to keep next to your PC.

446 pages • ISBN 978-0-905705-70-5  
£27.00 • US\$ 54.00



Fully elaborated electronics projects

## 309 Circuits

The present tenth edition of the popular '30x Circuits' series of books once again contains a comprehensive variety of circuits, sub-circuits, tips and tricks and design ideas for electronics. Among many other inspiring topics, the following categories are well presented in this book: test & measurement; RF (radio); computers and peripherals; audio & video; hobby and modelling; microcontrollers; home & garden; power supplies & battery chargers; etcetera.

432 pages • ISBN 978-0-905705-69-9  
£19.95 • US\$ 39.95




All articles published in 2007
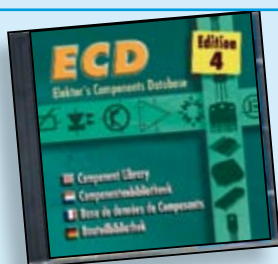
## Elektor 2007

This CD-ROM contains all articles published in Elektor Volume 2007. Using the supplied Adobe Reader program, articles are presented in the same layout as originally found in the magazine. An extensive search machine is available to locate keywords in any article. The installation program now allows Elektor year volume CD-ROMs you have available to be copied to hard disk, so you do not have to eject and insert your CDs when searching in another year volume. With this CD-ROM you can produce hard copy of PCB layouts at printer resolution, adapt PCB layouts using your favourite graphics program, zoom in / out on selected PCB areas and export circuit diagrams and illustrations to other programs.

ISBN 978-90-5381-218-1 • £16.90 • US\$ 33.80



More than 68,000 components

## ECD 4

The program package consists of eight databanks covering ICs, germanium and silicon transistors, FETs, diodes, thyristors, triacs and optocouplers. A further eleven applications cover the calculation of, for example, LED series droppers, zener diode series resistors, voltage regulators and AMVs. A colour band decoder is included for determining resistor and inductor values. ECD 4 gives instant access to data on more than 68,000 components. All databank applications are fully interactive, allowing the user to add, edit and complete component data. This CD-ROM is a must-have for all electronics enthusiasts.

ISBN 978-90-5381-159-7 • £15.90 • US\$ 31.80



## DigiButler

(May & April 2008)

A low-cost home automation server based on a Freescale Coldfire 32-bit microcontroller. The project has been designed with open source in mind and doubles as a powerful Coldfire development system using free CodeWarrior software from Freescale. DigiButler activates electrical appliances in and around the home, accepting on/off commands from a WAP phone, through an Ethernet network or via a webpage at an allocated IP address and with full access security.

*Kit of parts including SMD-stuffed PCB, programmed microcontroller, all leaded parts and CD-ROM containing CodeWarrior, TBLCF documentation, datasheets, application notes and source code files.*

Art.# 071102-71 • £29.00 • US\$ 58.00



## Elektor Internet Radio

(April 2008)

In the good old days, you had to modulate audio signals onto an RF carrier so they could be received and demodulated to produce something more or less audible. Nowadays you can access every Internet radio programme in the world by receiving, buffering and decompressing IP packages. This is all very easy with the Elektor Internet Radio. All open-source!

*PCB, SMD-populated*

Art.# 071081-71 • £115.00 • US\$ 230.00



**Bestseller!**

## Datalogger "deLuxe"

(March 2008)

We have had the pleasure of proposing various data acquisition units over the last few years. This Datalogger "deLuxe" is a nice exercise in product development. It actually utilises an SD card as the media for data storage. The hardware design is compact and that makes the firmware and software features even more interesting.

*Kit of parts incl. PCB, programmed controller and display*

Art.# 070745-71 • £71.75 • US\$ 143.50

More information on the  
Elektor Website:

**www.elektor.com**

**Elektor**

**Regus Brentford**

**1000 Great West Road**

**Brentford**

**TW8 9HH**

**United Kingdom**

**Tel.: +44 20 8261 4509**

**Fax: +44 20 8261 4447**

**Email: sales@elektor.com**

**elektor**  
SHOP

May 2008 (No. 377)

£ US\$

**Two-wire LCD**

071035-93 .... SMD-populated board with all parts and pinheaders ..... 12.70 ..... 25.40

**Display Computer**

070827-91 .... Populated PCB in enclosure ..... 78.80 ..... 157.60

**DigiButler (2)**

071102-1 .... PCB with SMDs premounted; empty microcontroller ..... 18.00 ..... 36.00

071102-71 .... Kit of parts incl. CD-ROM, PCB with SMDs premounted; programmed microcontroller ..... 29.00 ..... 58.00

071102-81 .... Software on CD-ROM (project software and CodeWarrior 6.3) ..... 5.20 ..... 10.40

**Elektor AVRprog**

080083-71 .... SMD-populated board with all cables ..... 23.50 ..... 47.00

**Tiny Counter**

070954-1 .... PCB, bare ..... 11.50 ..... 23.00

070954-41 .... Programmed controller ..... 7.50 ..... 15.00

April 2008 (No. 376)

**Elektor Internet Radio (EIR)**

071081-71 .... PCB, SMD-populated ..... 115.00 ..... 230.00

**CC2-AVR-Board 1**

071035-91 .... PCB, partly populated, ATM18 Controller module ..... 7.30 ..... 14.60

071035-92 .... PCB, partly populated ATM18-Testboard ..... 27.00 ..... 54.00

**Frequency Response Sweep Oscillator**

070951-41 .... Programmed controller ..... 5.40 ..... 10.80

March 2008 (No. 375)

**Data Logger "deLuxe"**

070745-1 .... PCB, bare ..... 16.30 ..... 32.60

070745-41 .... Programmed controller ..... 19.90 ..... 39.80

070745-71 .... Kit of parts (PCB, programmed controller and display) ..... 71.75 ..... 143.50

**The Secrets of I2C**

070600-1 .... PCB, bare ..... 13.60 ..... 32.60

070600-41 .... Programmed controller ..... 19.90 ..... 39.80

**Cylon Voice**

070859-41 .... Programmed controller ..... 4.70 ..... 9.40

**ECIO PLC**

070786-1 .... PCB, bare ..... 16.30 ..... 32.60

070786-71 .... Kit of parts (PCB, ECIO-module, all other components) ..... 76.00 ..... 152.00

February 2008 (No. 374)

**LEDBUS System**

070459-1 .... PCB, power module ..... www.thePCBshop.com

070459-2 .... PCB, central ..... www.thePCBshop.com

070459-41 .... PIC12F638-I/SN, programmed (power module) ..... 3.10 ..... 6.20

070459-42 .... ATmega32-16PC, programmed (central) ..... 13.80 ..... 27.60

**RGB LED Mood Lighting**

070892-1 .... PCB, bare ..... www.thePCBshop.com

070892-2 .... PCB, bare ..... www.thePCBshop.com

070892-3 .... PCB, bare ..... www.thePCBshop.com

**Surround Light for PC Monitor**

070491-1 .... PCB, bare ..... 21.50 ..... 43.00

070491-2 .... PCB, bare ..... 5.00 ..... 10.00

**LED Ringflash**

070612-1 .... PCB, bare ..... www.thePCBshop.com

070612-41 .... PIC16F628, programmed ..... 10.50 ..... 21.00

070612-81 .... Software on CD-ROM ..... 5.20 ..... 10.40

**TV Surround Light**

070487-1 .... PCB, bare ..... 21.50 ..... 43.00

070487-41 .... Programmed controller ..... 12.70 ..... 25.40

070487-42 .... Programmed controller ..... 10.50 ..... 21.00

070487-81 .... Software on CD-ROM ..... 5.20 ..... 10.40

**CAN Explorer**

060201-1 .... PCB, MCP2515 and MCP2551SN ..... www.thePCBshop.com

060201-W .... Testing & Error Sources Manual ..... www.elektor.com

# Bestsellers

Books

**1 ➡ PIC Microcontrollers**  
ISBN 978-0-905705-70-5 ..... £27.00 ..... US\$ 54.00

**2 ➡ 309 Circuits**  
ISBN 978-0-905705-69-9 ..... £19.95 ..... US\$ 39.95

**3 ➡ Visual Basic for Electronics Engineering Applications**  
ISBN 978-0-905705-68-2 ..... £29.00 ..... US\$ 58.00

**4 ➡ Microcontroller Basics**  
ISBN 978-0-905705-67-5 ..... £19.50 ..... US\$ 39.00

**5 ➡ PC Interfaces under Windows**  
ISBN 978-0-905705-65-1 ..... £27.25 ..... US\$ 54.50

CD-ROMs

**1 ➡ FPGA Course**  
ISBN 978-90-5381-225-9 ..... £14.50 ..... US\$ 29.00

**2 ➡ Elektor 2007**  
ISBN 978-90-5381-218-1 ..... £16.90 ..... US\$ 33.80

**3 ➡ ECD 4**  
ISBN 978-90-5381-159-7 ..... £15.90 ..... US\$ 31.80

**4 ➡ USB Toolbox**  
ISBN 978-90-5381-212-9 ..... £19.90 ..... US\$ 39.80

**5 ➡ Ethernet Toolbox**  
ISBN 978-90-5381-214-3 ..... £18.90 ..... US\$ 37.90

Kits & Modules

**1 ➡ Datalogger "deLuxe"**  
Art. # 070745-71 ..... £71.75 ..... US\$ 143.50

**2 ➡ CO<sub>2</sub> Measurement**  
Art. # 070802-71 ..... £107.50 ..... US\$ 215.00

**3 ➡ ECIO PLC**  
Art. # 070786-71 ..... £76.00 ..... US\$ 152.00

**4 ➡ Elektor Internet Radio**  
Art. # 071081-71 ..... £115.00 ..... US\$ 230.00

**5 ➡ USB Flash Board**  
Art. # 070125-71 ..... £36.20 ..... US\$ 72.40

Order quickly and safe through  
**www.elektor.com/shop**  
or use the Order Form near the end  
of the magazine!

**elektor**  
SHOP

Elektor  
Regus Brentford  
1000 Great West Road  
Brentford TW8 9HH • United Kingdom  
Tel. +44 20 8261 4509  
Fax +44 20 8261 4447  
Email: sales@elektor.com

**NEW**

# i-TRIXX

**Electronics inside out!**


**The free e-magazine about internet, computers, hacking, tweaking, modding, gadgets, geekstuff, gaming and DIY electronics. The e-zine you have to check out now!**



Receive i-TRIXX in your mailbox  
**FOR FREE !**  
each Wednesday !
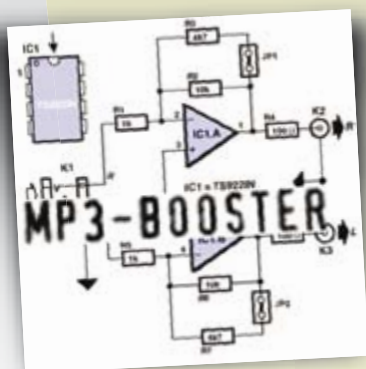
## Play the i-TRIXX Quiz and win!

Test your knowledge about internet, computers and electronics. Take your chance now and play the i-TRIXX Quiz. There are great prizes to win!



**From the Elektor labs:**  
Simple, useful and fun electronic circuits!

Check **i-TRIXX.com** and subscribe now!

Powered by



## on the testbench: PC soundcards

All PCs are now sold with a plug-in soundcard or equivalent on-board circuitry for processing audio signals. To electronics designers, the soundcard doubles as a fine instrument to do (low-frequency) measurements, effectively turning the PC into an analyser or an oscilloscope.

Sufficient resolution of the soundcard is perhaps the single most important condition for accurate measurement results. Hence we ran laboratory tests on a number of soundcards on the market with different price tags. The results are presented in the June 2008 issue.



## Colourful Computer Light

We live in a colourful environment these days. Everything is in colour: TV, advertising billboards, mobile phone displays and LEDs. Philips added a further dimension to all this with their Ambilight, Wake-up Light and Living Colors lamp. We will work with the latter in this Modding & Tweaking article. The wireless remote control offers interesting possibilities once the protocol has been cracked...

## Switch-mode audio power supply

Lots of electronic equipment is powered by a switch-mode power supply (SMPSU) because it's light, efficient and compact. Alas, SMPSUs suitable for use with audio power amplifiers are rare finds. That's going to change with SAPS-400, a module with an adjustable output voltage to  $\pm 60$  V and good for a whopping 400 watts of output power. SAPS weighs just 500 g and is a little larger than two cigarette packs.



### RESERVE YOUR COPY NOW!

UK mainland subscribers will receive the magazine between 16 and 19 May 2008.

The June 2008 issue goes on sale on Thursday 22 May 2008 (UK distribution only).

Article titles and magazine contents subject to change, please check [www.elektor.com](http://www.elektor.com).

## NEWSAGENTS ORDER FORM

### SHOP SAVE / HOME DELIVERY

Please save / deliver one copy of *Elektor* magazine for me each month

Name: .....  
 Address: .....  
 Post code: .....  
 Telephone: .....  
 Date: .....  
 Signature: .....



Please cut out or photocopy this form, complete details and hand to your newsagent.

Elektor is published on the third Thursday of each month, except in July.

Distribution S.O.R. by Seymour (NS).

[www.elektor.com](http://www.elektor.com) [www.elektor.com](http://www.elektor.com) [www.elektor.com](http://www.elektor.com) [www.elektor.com](http://www.elektor.com) [www.elektor.com](http://www.elektor.com)

## Elektor on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Shop you'll find all other products sold by the publishers, like CD-ROMs, kits and books. A powerful search function allows you to search for items and references across the entire website.

### Also on the Elektor website:

- Electronics news and Elektor announcements
- Readers Forum
- PCB, software and e-magazine downloads
- Surveys and polls
- FAQ, Author Guidelines and Contact



**METHOD OF PAYMENT**  
(see reverse before ticking as appropriate)

- ☐ **Bank transfer**
- ☐ **Cheque**  
(UK-resident customers ONLY)

#### **Giro transfer**

[illegible]

Expiry date: \_\_\_\_\_

Verification code:

Please send this order form to\*  
(see reverse for conditions)

## Elektor

Regus Brentford  
1000 Great West Road  
Brentford TW8 9HH  
United Kingdom

Tel.: +44 20 8261 4509  
Fax: +44 20 8261 4447  
[www.elektor.com](http://www.elektor.com)  
[sales@elektor.com](mailto:sales@elektor.com)

\*USA and Canada residents may  
(but are not obliged to)  
use \$ prices, and send the order form to:  
Old Colony Sound Lab  
P.O. Box 876, Peterborough  
NH 03458-0876. Tel. (603) 924-6371, 924-6526,  
Fax: (603) 924-9467  
Email: [custserv@audioXpress.com](mailto:custserv@audioXpress.com)

**I would like:**

☐ **Standard Subscription (11 issues)**

☐ **Subscription-Plus**  
**(11 issues plus the Elektor Volume 2008 CD-ROM)**

\* Offer available to Subscribers who have not held a subscription to *Elektor* during the last 12 months. Offer subject to availability. See reverse for rates and conditions.

Name		
<hr/>		
Address + Post code		
<hr/>		
<hr/>		
<hr/>		
Tel.		Email
Date	-	Signature
		<hr/>

**METHOD OF PAYMENT**  
(see reverse before ticking as appropriate)

- ☐ **Bank transfer**
- ☐ **Cheque**  
(UK-resident customers ONLY)

#### **Giro transfer**

[illegible]

Expiry date: \_\_\_\_\_

Verification code: \_\_\_\_\_

Please send this order form to

## Elektor

Regus Brentford  
1000 Great West Road  
Brentford TW8 9HH  
United Kingdom

Tel.: +44 20 8261 4509  
Fax: +44 20 8261 4447  
[www.elektor.com](http://www.elektor.com)  
[subscriptions@elektor.com](mailto:subscriptions@elektor.com)

## ORDERING INSTRUCTIONS, P&P CHARGES

Except in the USA and Canada, all orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. Online ordering: [www.elektor.com/shop](http://www.elektor.com/shop)

**Readers in the USA and Canada** may (but are not obliged to) send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Old Colony Sound for applicable P&P charges. Please allow 4-6 weeks for delivery.

**Orders placed on our Brentford office** must include P&P charges (Priority or Standard) as follows: Europe: £6.00 (Standard) or £7.00 (Priority) Outside Europe: £9.00 (Standard) or £11.00 (Priority)

## HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

**Bank transfer** into account no. 40209520 held by Elektor Electronics with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

**Cheque** sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

**Giro transfer** into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

**Credit card** VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

## COMPONENTS

Components for projects appearing in Elektor are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

## TERMS OF BUSINESS

**Delivery** Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. **Returns** Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. **Damaged goods** Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). **Cancelled orders** All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5.00. **Patents** Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor does not accept responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor other than to supply goods as described or, at the option of Elektor, to refund the purchaser any money paid in respect of the goods. **Law** Any question relating to the supply of goods and services by Elektor shall be determined in all respects by the laws of England.

September 2007

## SUBSCRIPTION RATES FOR ANNUAL SUBSCRIPTION

	Standard	Plus
United Kingdom	£42.00	£49.00
Surface Mail		
Rest of the World	£56.00	£63.00
Airmail		
Rest of the World	£71.00	£78.00
USA & Canada For US\$-prices please check <a href="http://www.elektor.com">www.elektor.com</a>		

## HOW TO PAY

**Bank transfer** into account no. 40209520 held by Elektor Electronics. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

**Cheque** sent by post, made payable to Elektor Electronics. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

**Giro transfer** into account no. 34-152-3801, held by Elektor Electronics. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

**Credit card** VISA and MasterCard can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

## SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of student-ship signed by the head of the college, school or university faculty. A standard Student Subscription costs £33.60, a Student Subscription-Plus costs £39.20 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twenty-five per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subscriptions cannot be cancelled after they have run for six months or more.

January 2008



## Take out a free subscription to E-weekly now

Do you want to stay up to date with electronics and computer technology? Always looking for useful hints, tips and interesting offers? Subscribe now to E-weekly, the free Elektor Newsletter.

### Your benefits:

- The latest news on electronics in your own mailbox each friday
- Free access to the News Archive on the Elektor website
- You're authorized to post replies and new topics in our forum



Register today on [www.elektor.com/newsletter](http://www.elektor.com/newsletter)

# www. elektor. com

**PCBs in 24 hours from £30.00**

**PCBTrain.com**

Tel: 01635 40347  
Fax: 01635 36143  
e-mail: [clmufa@newburyteam.co.uk](mailto:clmufa@newburyteam.co.uk)

Newbury Electronics Ltd  
Forday Road, Newbury, Berkshire RG14 2AD  
[www.newburyelectronics.co.uk](http://www.newburyelectronics.co.uk)

**NE**  
Approved ISO 9001

## INDEX OF ADVERTISERS

Allendale Electronics Ltd	<a href="http://www.pcb-soldering.co.uk">www.pcb-soldering.co.uk</a>	36	Marchand Electronics Inc, Showcase	<a href="http://www.marchandelec.com">www.marchandelec.com</a>	79
ATC Semitec Ltd, Showcase	<a href="http://www.atcsemitec.co.uk">www.atcsemitec.co.uk</a>	67, 78	Microchip	<a href="http://www.microchip.com">www.microchip.com</a>	17
Avit Research, Showcase	<a href="http://www.avitresearch.co.uk">www.avitresearch.co.uk</a>	78	MikroElektronika	<a href="http://www.mikroe.com">www.mikroe.com</a>	11
Beijing Draco	<a href="http://www.ezpcb.com">www.ezpcb.com</a>	73	MQP Electronics, Showcase	<a href="http://www.mqp.com">www.mqp.com</a>	79
Beta Layout, Showcase	<a href="http://www.pcb-pool.com">www.pcb-pool.com</a>	73, 78	New Wave Concepts, Showcase	<a href="http://www.new-wave-concepts.com">www.new-wave-concepts.com</a>	79
Bitscope Designs	<a href="http://www.bitscope.com">www.bitscope.com</a>	3	Newbury Electronics	<a href="http://www.newburyelectronics.co.uk">www.newburyelectronics.co.uk</a>	87
Bowood Electronics Ltd, Showcase	<a href="http://www.bowood-electronics.co.uk">www.bowood-electronics.co.uk</a>	78	Nurve Networks	<a href="http://www.xgamestation.com">www.xgamestation.com</a>	75
Byvac Electronics, Showcase	<a href="http://www.byvac.co.uk">www.byvac.co.uk</a>	78	Paltronix	<a href="http://www.paltronix.com">www.paltronix.com</a>	13
Decibit Co. Ltd, Showcase	<a href="http://www.decibit.com">www.decibit.com</a>	78	Peak Electronic Design	<a href="http://www.peakelec.co.uk">www.peakelec.co.uk</a>	75
Designer Systems, Showcase	<a href="http://www.designersystems.co.uk">www.designersystems.co.uk</a>	78	Pico	<a href="http://www.picotech.com">www.picotech.com</a>	15
EasyDAQ, Showcase	<a href="http://www.easydaq.biz">www.easydaq.biz</a>	78	Quasar Electronics	<a href="http://www.quasarelectronics.com">www.quasarelectronics.com</a>	37
Easysync, Showcase	<a href="http://www.easysync.co.uk">www.easysync.co.uk</a>	78	Radiometrix, Showcase	<a href="http://www.radiometrix.com">www.radiometrix.com</a>	79
Eltec, Showcase	<a href="http://www.eltec.com">www.eltec.com</a>	78	Robot Electronics, Showcase	<a href="http://www.robot-electronics.co.uk">www.robot-electronics.co.uk</a>	79
EMCelettronica Srl, Showcase	<a href="http://www.emcelettronica.com">www.emcelettronica.com</a>	78	Robotiq, Showcase	<a href="http://www.robotiq.co.uk">www.robotiq.co.uk</a>	79
Eurocircuits	<a href="http://www.eurocircuits.com">www.eurocircuits.com</a>	55	ScanTool, Showcase	<a href="http://www.obd2cables.com">www.obd2cables.com</a> , <a href="http://www.scantool.net">www.scantool.net</a>	79
First Technology Transfer Ltd, Showcase	<a href="http://www.ftt.co.uk">www.ftt.co.uk</a>	78	Showcase		78, 79
FlexiPanel Ltd, Showcase	<a href="http://www.flexipanel.com">www.flexipanel.com</a>	78	Tsien (UK) Ltd, Showcase	<a href="http://www.componentbin.com">www.componentbin.com</a>	78
FLYPCB	<a href="http://www.flypcb.com">www.flypcb.com</a>	75	USB Instruments, Showcase	<a href="http://www.usb-instruments.com">www.usb-instruments.com</a>	79
Future Technology Devices, Showcase	<a href="http://www.ftdichip.com">www.ftdichip.com</a>	78	Virtins Technology, Showcase	<a href="http://www.virtins.com">www.virtins.com</a>	79
Futurlec, Showcase	<a href="http://www.futurlec.com">www.futurlec.com</a>	78			
Hammond Electronics	<a href="http://www.hammondmfg.com/uk">www.hammondmfg.com/uk</a>	35			
ILP Electronics Ltd, Showcase	<a href="http://www.ilpelectronics.com">www.ilpelectronics.com</a>	78			
Jaycar Electronics	<a href="http://www.jaycarelectronics.co.uk">www.jaycarelectronics.co.uk</a>	2			
Labcenter	<a href="http://www.labcenter.com">www.labcenter.com</a>	88			
Lascar	<a href="http://www.lascarelectronics.com">www.lascarelectronics.com</a>	41			
London Electronics College, Showcase	<a href="http://www.lec.org.uk">www.lec.org.uk</a>	78			

**Advertising space for the issue of 23 June 2008  
may be reserved not later than 27 May 2008**

with Huson International Media – Cambridge House – Gogmore Lane –  
Chertsey, Surrey KT16 9AP – England – Telephone 01932 564 999 –  
Fax 01932 564998 – e-mail: [p.brady@husonmedia.com](mailto:p.brady@husonmedia.com) to whom all  
correspondence, copy instructions and artwork should be addressed.

# The Proteus Design Suite

## Celebrating 20 Years of Innovation



- ↓ **1988** Labcenter commences trading with PC-B for DOS
- ↓ **1989.** First integrated autorouter added for PCB Design.
- ↓ **1990** Schematic Capture added to PCB Layout package
- ↓ **1991. World First** Schematic Capture for Windows™.
- ↓ **1992.** Topological route editing for easier PCB layout.
- ↓ **1993. Proteus** offers fully integrated circuit simulation.
- ↓ **1994.** Autorouter enhanced with Rip-Up and Retry algorithm.
- ↓ **1995** Gridless, shape based power plane support
- ↓ **1996.** True, mixed mode SPICE simulation introduced.
- ↓ **1997.** Interactive simulation - ideal for educational users.
- ↓ **1998.** PIC microcontroller simulation technology developed.
- ↓ **1999.** 8051 microcontroller simulation technology developed.
- ↓ **2000** World First Interactive MCU co-simulation (VSM)
- ↓ **2001.** High level language support added for MCU simulation.
- ↓ **2002.** ELECTRA adaptive shape based router interface added.
- ↓ **2003. World First** 32 bit MCU simulation support with ARM7.
- ↓ **2004.** Integration between Proteus VSM and MPLAB™.
- ↓ **2005** Redesigned GUI across the Proteus Design Suite
- ↓ **2006.** 3D visualisation engine integrated with ARES PCB Design.
- ↓ **2007. World First** USB schematic based USB Simulation.
- ↓ **2008** Coming Soon: Introduction of HDL support in simulation, ODB++ manufacturing output, improved core SPICE simulation algorithms, enhanced live DRC error checking and much more.

### LABCENTER ELECTRONICS LTD

A technology pioneer in the EDA Industry since 1988  
 Technical Support direct from the program authors  
 Flexible packages and pricing tailored to customer requirements.

**labcenter**  **www.labcenter.com**  
**Electronics**



Labcenter Electronics Ltd. 53-55 Main Street, Grassington,  
 North Yorks. BD23 5AA. Registered in England 4692454  
 Tel: +44 (0)1756 753440, Email: info@labcenter.com